

Lab Report 6

Name: Sricharan Vinoth Kumar

Roll no: 2024112022

Group no: 10

Experiment 1:-



- Objective:

To create a S-R Latch using NOR gates and observe its function.

- Electronic Components Required:

- 7402 2-input NOR gate IC
- Digital Test Kit

- Reference Circuit:-

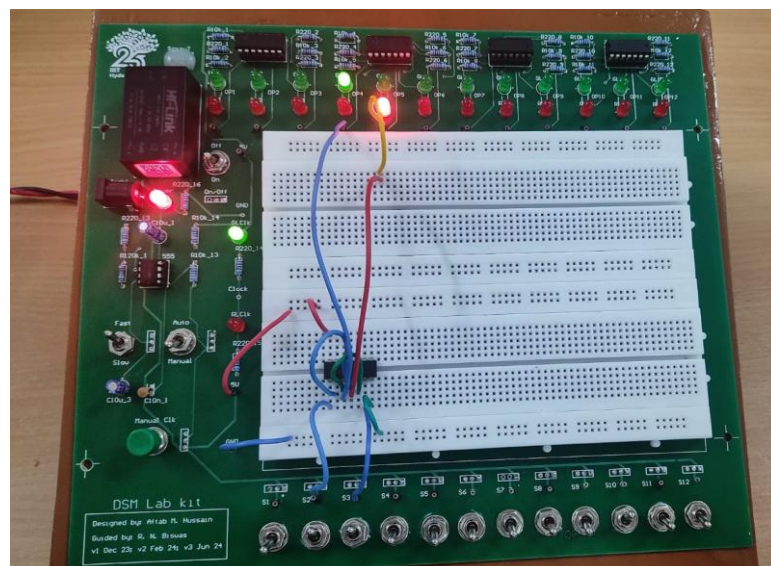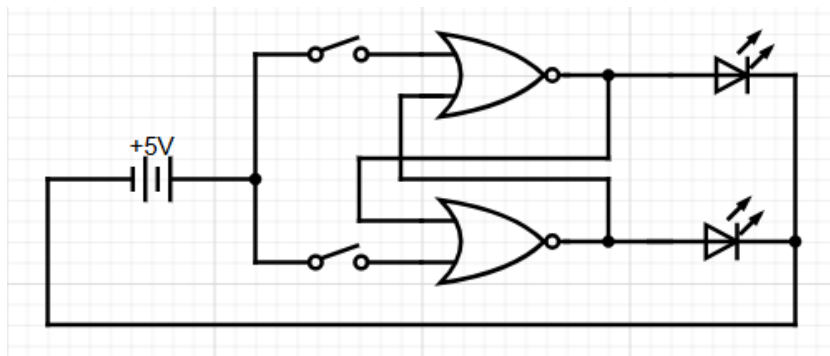

- Procedure:-

1. Ensure that the input pins IP1-12 and output LEDs LG1-12 and LR1-12 are working.
2. Using a 2-input NOR gate IC, assemble an SR latch as shown in the circuit diagram.
3. Apply all possible inputs of R and S to the latch and observe the outputs in each case.
4. Tabulate the observations and verify the function of the S-R latch.

- Observation:-

Function table of the circuit,

S	R	Q(t+1)
0	0	Q(t) (Memory state)
0	1	0 (Reset)
1	0	1 (Set)
1	1	Forbidden

- Conclusion:-

An S-R latch using NOR gates has been assembled and its function has been observed.

- TinkerCAD Simulation:-

https://www.tinkercad.com/things/5X1xLI4e2QS-dsm-lab-6-exp-1?sharecode=LkADH9MJCZeNb_d3srh3YiamyXwN9jUDJuAE9Fspz9Q

Experiment 2:-



- Objective:-

To create a J-K Flip Flop and observe its function.

- Electronic Components Required:-

1. 7420 4-input NAND gate IC
2. 7400 2-input NAND gate IC
3. 7402 2-input NOR gate IC
4. Digital Test Kit

- Reference Circuit:-

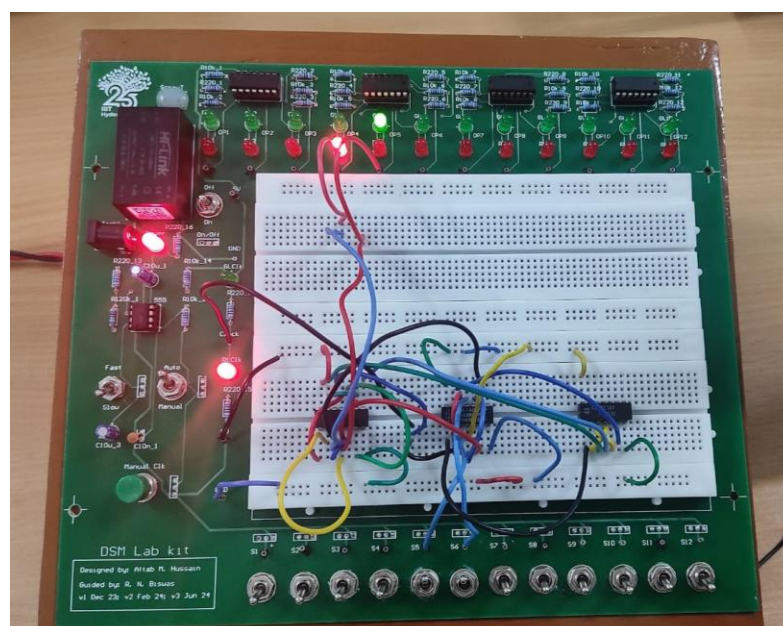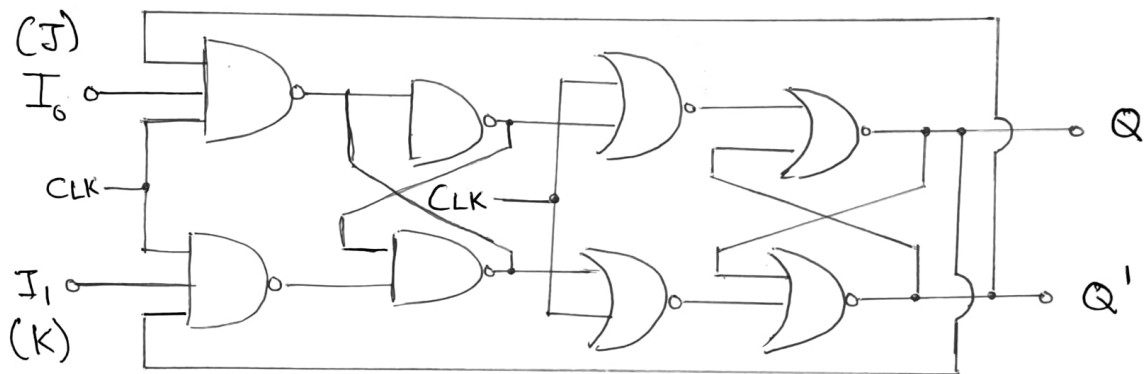

- Procedure:-

1. Ensure that the input pins IP1-12 and output LEDs LG1-12 and LR1-12 are working.
2. Set the CLOCK of the kit to SLOW mode or Manual mode.
3. Using the above-mentioned ICs, assemble the circuit as per the given circuit diagram.
4. Apply all possible combinations of J and K and observe the outputs.
5. Tabulate the observations and verify the function of the J-K Flip flop.

- Observation:-

Observed characteristic table of the circuit,

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

- Conclusion:-

A J-K Flip flop has been assembled and its function has been observed.

- TinkerCAD Simulation:-

https://www.tinkercad.com/things/cCOD9E9mK0A-dsm-lab-6-exp-2?sharecode=zKHdZXtSTKf0m-X_W_gAmhNmPn6RYiz2QeUedzCtbU

Experiment 3:-



- Objective:-

To design a 4 – bit binary counter using Arduino

- Electronic Components Required:-

- Arduino Uno
- Digital Test Kit

- Reference Circuit:-

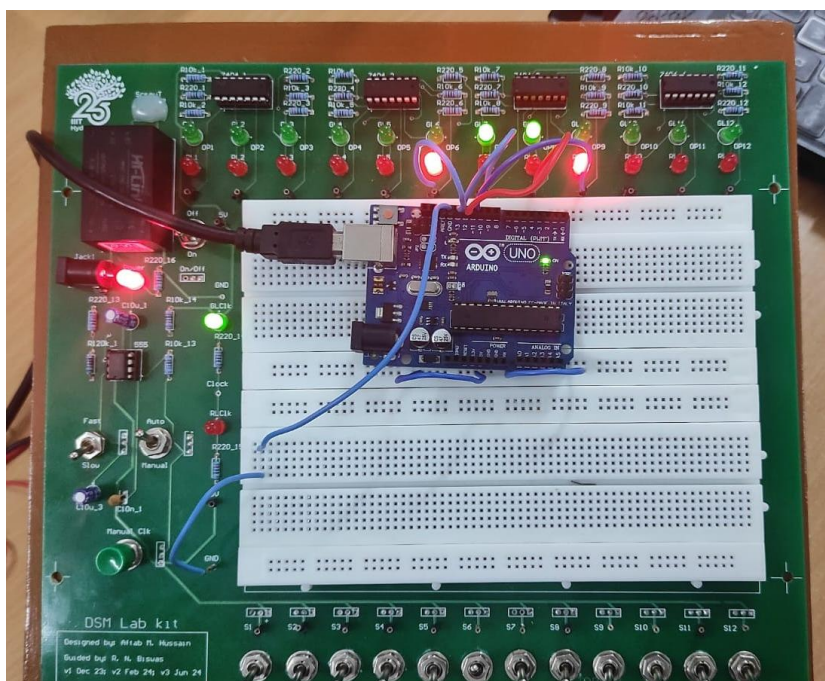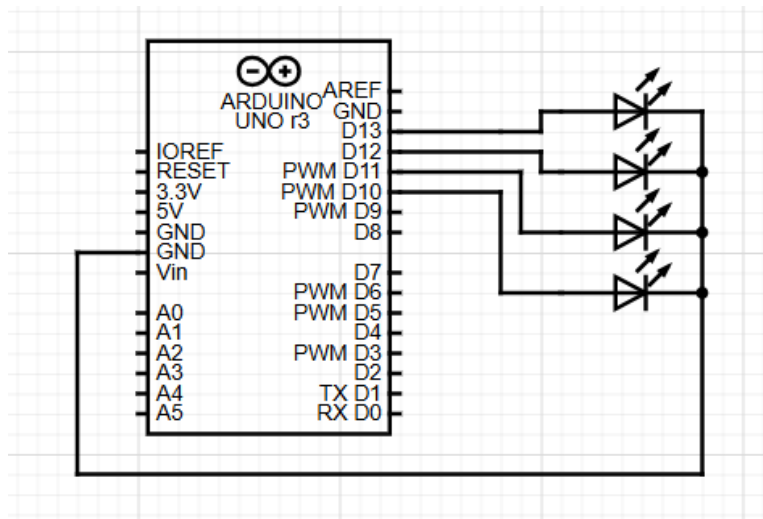

- Procedure:-

1. Connect the Arduino to 4 output LEDs as per the given circuit diagrams.
2. Write a program to oscillate the output level of the pins, such that each pin has twice the time period of its adjacent pin.
3. Upload the code and observe the output

- Observation:-

Code of the program,

```
#include "Timer.h"

Timer t;

int pin1 = 7;
int pin2 = 6;
int pin3 = 5;
int pin4 = 4;

void setup() {
    pinMode(pin1, OUTPUT);
    pinMode(pin2, OUTPUT);
    pinMode(pin3, OUTPUT);
    pinMode(pin4, OUTPUT);

    t.oscillate(pin1, 8000, LOW);
    t.oscillate(pin2, 4000, LOW);
    t.oscillate(pin3, 2000, LOW);
    t.oscillate(pin4, 1000, LOW);
}

void loop() {
    t.update();
}
```

- Conclusion:-

A 4-bit counter has been successfully assembled using the Arduino.

- TinkerCAD Simulation:-

TinkerCAD does not support the Timer.h library used in the program.

Therefore, the code used in the simulation is different. But the basic idea is the same.

<https://www.tinkercad.com/things/ca3EYNGTRjL-dsm-lab-6-exp-3?sharecode=EKSB2RT2Bv1hWBuRSv4DTtsvnatSO2Al-Q6kosErUPE>