

Lab Report 8

Name: Sricharan Vinoth Kumar

Roll no: 2024112022

Group no: 10


- Objective:


To simulate the working of RAM by building a binary cell circuit.

- Electronic Components Required:-

- 7402 2-input NOR IC
- 7411 3-input AND IC
- 7404 NOT IC
- Digital Test Kit

- Reference Circuit:-

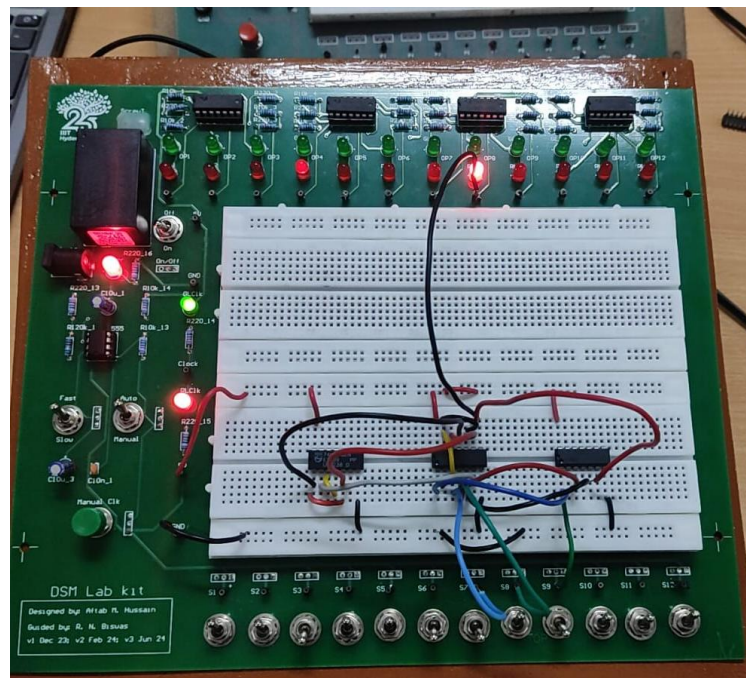

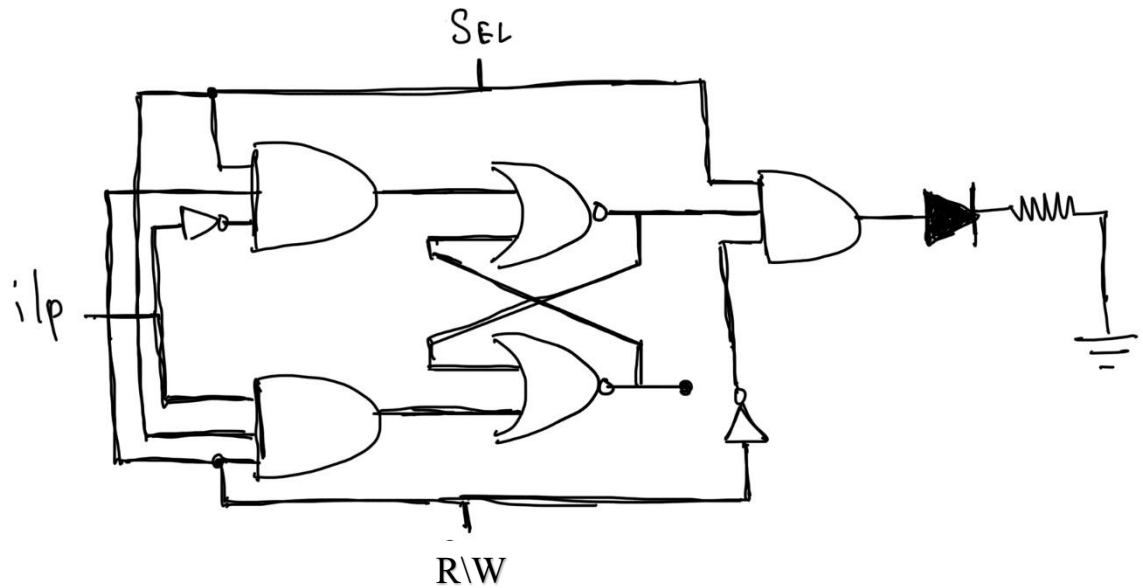

- Procedure:

1. Ensure that the input pins IP1-12 and output LEDs LG1-12 and LR1-12 are working.
2. Assemble the circuit as per the given circuit diagram.
3. Give all possible combinations of inputs to the Input, Select and R/W pins and observe the outputs.
4. Verify the working and the functions of the circuit.

- Observation:

The function table of the circuit is:

<u>Select</u>	<u>Read/Write</u>	<u>Function</u>
0	X	0
1	0	Retains the previous output
1	1	Follows the input

- Conclusion:

The binary cell circuit has been assembled and its working has been analyzed.

- TinkerCAD Simulation:

https://www.tinkercad.com/things/8r1jbnDYzYz-dsm-lab-8?sharecode=5niQHlrQpLhAuHNuhbLKkAQfob_OeXhgNv0VL1mx1Ms