

## **Instructions:**


1. Systematically record all your observations in the lab book ([mandatory](#))
2. Save results in USB or take pictures
3. Make meaningful tables to summarize your findings and show it to the instructor(s) during the lab session only
4. Bring your calculators and DMM (if available)
5. Handle equipment carefully and report in case of any incidence
6. Enjoy your time in lab and strengthen your understanding about circuits

## Experiment-7 Common Source Amplifier

### 1. Effect of Body effect on gain of CS amplifier

Fig. 21 shows a CS amplifier using an NMOS (CD4007BE). Realize the circuit on breadboard and connect the body terminal ( $V_{SS}$ ) to ground.

It is given that  $V_{DD} = 5V$ ,  $V_{BIAS} = 2.5V$ ,  $V_T = 1.8V$ ,  $R_L = 4.7k\Omega$ .

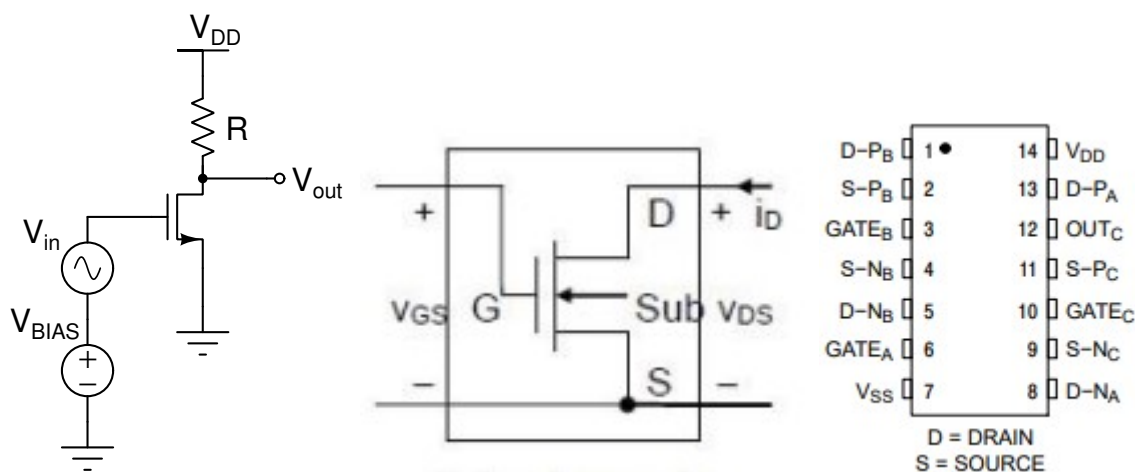

**Figure 21:** Common source NMOS based amplifier with resistive load

- (a) Measure the DC value of  $V_{DS}$ . Find drain current  $I_{DS} = \frac{V_{DD} - V_{DS}}{R_L}$  and using saturation region drain current equation find  $\mu_n C_{ox} \frac{W}{L}$  for the given transistor. Also calculate  $g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$ .
- (b) Apply an ac signal ( $v_{in}$  with  $50 mV_{pp}$  amplitude and 1 kHz frequency). Report gain ( $A_v = \frac{v_{out}}{v_{in}} = g_m \times R_L$ ) and calculate  $g_m$  (*effective*) (does it match closely with the value obtained in previous step?).

- (c) In order to see the body effect, connect  $V_{SS}$  to a DC supply. (Caution: Before connecting to the supply, ensure that the voltage is near 0 V). As shown in table 14, use given values of  $V_{SS}$  and report the corresponding amplitude of  $v_{out}$ , gain and  $g_m$  (effective). Note that due to the body effect,  $g_m$  (effective) =  $g_m + g_{mb}$ . Comment on the effect of body-effect over gain.

Body Voltage ( $V_{SS}$ )	$v_{out}$	Gain	$g_m$ (effective)
0			
0.4			
-0.4			

Table 12

## 2. Effect of BIAS points on Gain of common source amplifier

- (a) For different values of input BIAS voltage and a fixed small signal input voltage ( $v_{in}$  with  $100\text{ mV}_{pp}$  amplitude and 1 kHz frequency),  $V_{DD} = 5\text{ V}$ , plot the output and find the gain for each value of  $V_{BIAS}$ .
- (b) Calculate the value of  $g_m$  for each value of  $V_{BIAS}$  from gain ( $gain = -g_m R_L$ ), where  $R_L = 4.7\text{ k}\Omega$ .
- (c) Using the measured values, plot  $g_m$  vs  $V_{GS}$  (BIAS) in your notebook.
- (d) Tabulate the corresponding values of  $V_{out}$  for each value of  $V_{BIAS}$

$V_{BIAS}$ (V)	$V_{out}$	Gain	$g_m$
1.5			
1.8			
2.5			
3.1			
4			

Table 13


## 3. Effect of small signal input swing on gain of common source amplifier

- (a) For a  $V_{BIAS} = 2.5\text{ V}$ , apply the input signal ( $100\text{ mV}$ ) with step size of  $100\text{ mV}$  between the different inputs until clipping can be observed. Find the output swing and the corresponding gain value.
- (b) Tabulate the corresponding values of gain and output swing for each  $v_{in}$ .
- (c) Explain the reason of clipping and trend of gain values.

$V_{input\ ac}$	$V_{output\ ac}$	Gain	$g_m$

Table 14

#### 4. CS amplifier with external coupling

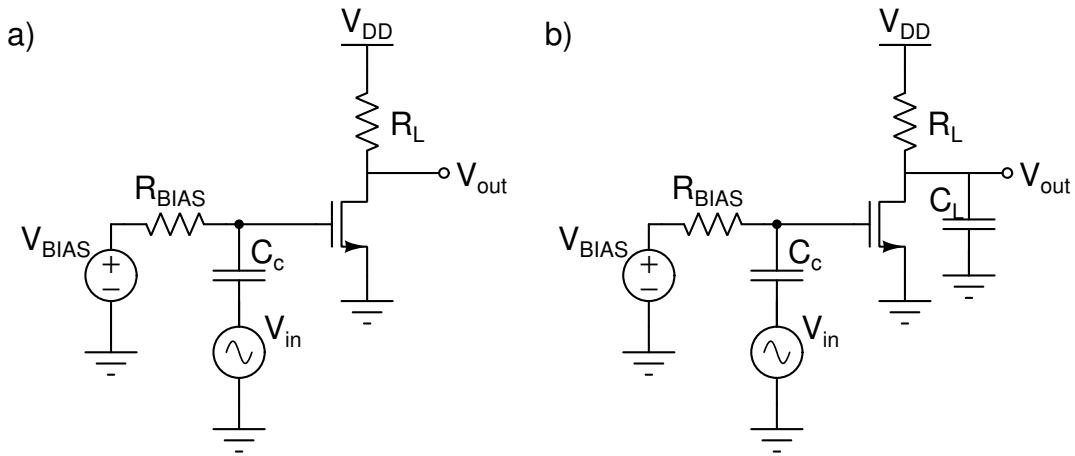

**Figure 22:** CS amplifier with external coupling capacitance and resistor

- (a) To the CS amplifier as in figure.21 instead of giving a sinusoidal signal with a DC offset we bias the amplifier with external DC source. We connect an external coupling capacitance  $C_c$  of value around  $10\ \mu\text{F}$  in series with  $V_{in}$  and a bias resistor  $R_{BIAS}$  of value around few  $100\ \Omega$  in series with  $V_{BIAS}$  as shown in figure.22.
- (b) We give a sinusoidal input signal  $v_{in}$  of amplitude  $100\ \text{mV}$   $V_{p-p}$ ,  $V_{BIAS}$  of value  $2.5\ \text{V}$  and load resistance  $R_L$  of value  $4.7\ \text{K}\Omega$  for supply voltage ( $V_{DD}$ ) of  $5\ \text{V}$ . Measure the value of gain ( $\frac{V_{out}}{V_{in}}$ ) and from gain calculate the value of  $g_m$ . Do you observe any difference in the values of gain and  $g_m$  from the values you obtained from previous results.
- (c) Measure the value of  $V_{DS}$  and determine the value of  $I_{DS}$  and  $\mu C_{ox} \frac{W}{L}$ .
- (d) As shown in Fig. 22(b), connect a load capacitor  $C_L = 470\ \text{pF}$  and plot the frequency response of the amplifier gain. Find the 3-dB bandwidth from measured plots and verify it with the estimated pole of the transfer function ( $\frac{v_{out}}{v_{in}}(s)$ ). (hint: To plot, use analyze option in DSO, in frequency response analysis chart, set start frequency as  $100\ \text{Hz}$ , stop frequency as  $20\ \text{MHz}$ , Amplitude as  $10\ \text{mV}$ , Output load as High-Z and points as 50. Select the gain channel and move the marker to get the readings)