

Prof: Abhishek Srivastava , CVEST

23 lectures

- 30 hours

Grading :

Assignment (3/4) : 10 %.

Course Project : 20 %.

Quiz : 10 % + 10 %.

Midsem : 20 %.

Endsem : 30 %.

VLSI Design

Assignment Deadline: 6pm

VLSI Design

→ Topics:-

1) Intro to VLSI Design

2) CMOS Inverter

3) Multi-stage logic Design and Optimization

4) Other logic styles


5) Intro. to HDL System Design.

• SCL - Semiconductor Complex Limited. Only fabrication facility in India. Can do upto 180 nm CMOS. Located in Mohali.
↳ Considered a very old technology.

• We will be using 180 nm technology in this course, since it is now open-source.

→ High impedance state :-

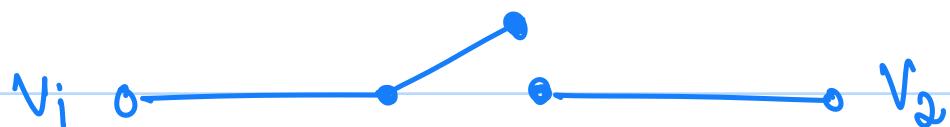• When a node is not connected to any well defined voltage, it is said to be existing in a high impedance state.




V_2 is in a high impedance state.

(Refer Weste & Harris MOS T Physics for
today's lecture)

5/8/25

→ Inverter :-

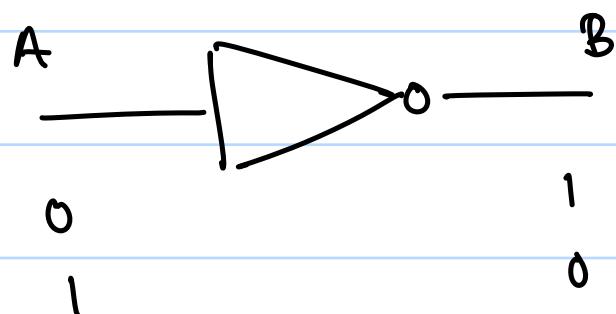

A	B
0	1
1	0


- 1 and 0 correspond to 2 different voltage levels.

• Ideally,




The above plot is termed as a VTC plot (Voltage Transfer Characteristics).

1)

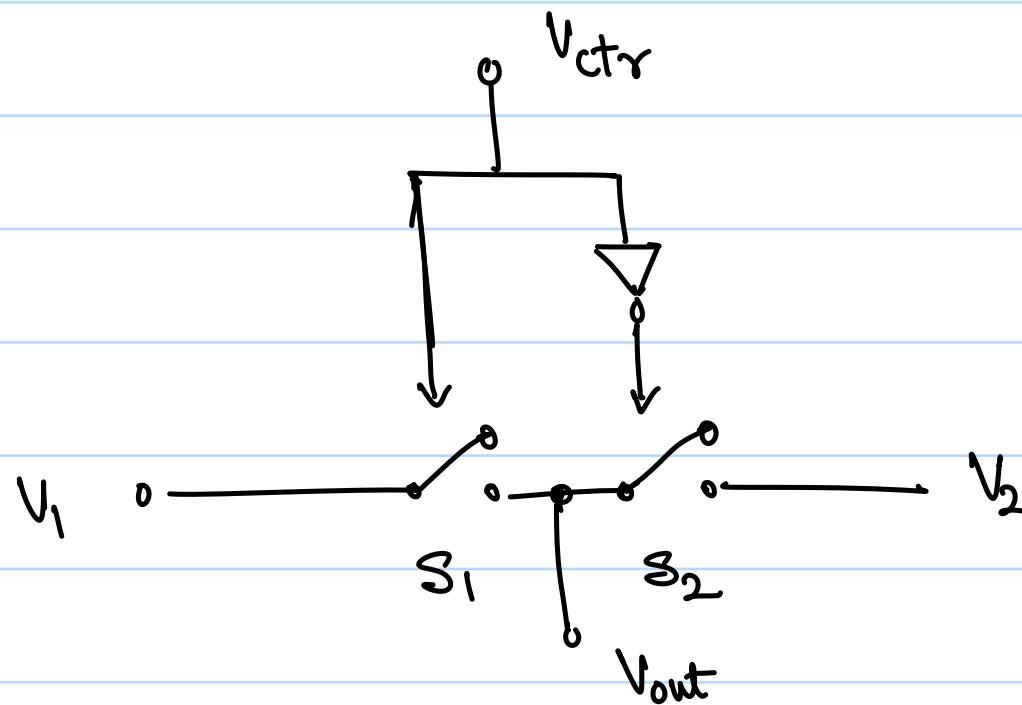Truth Table:

V_{ctr}	V_{out}
0	V_2
1	V_1


2)

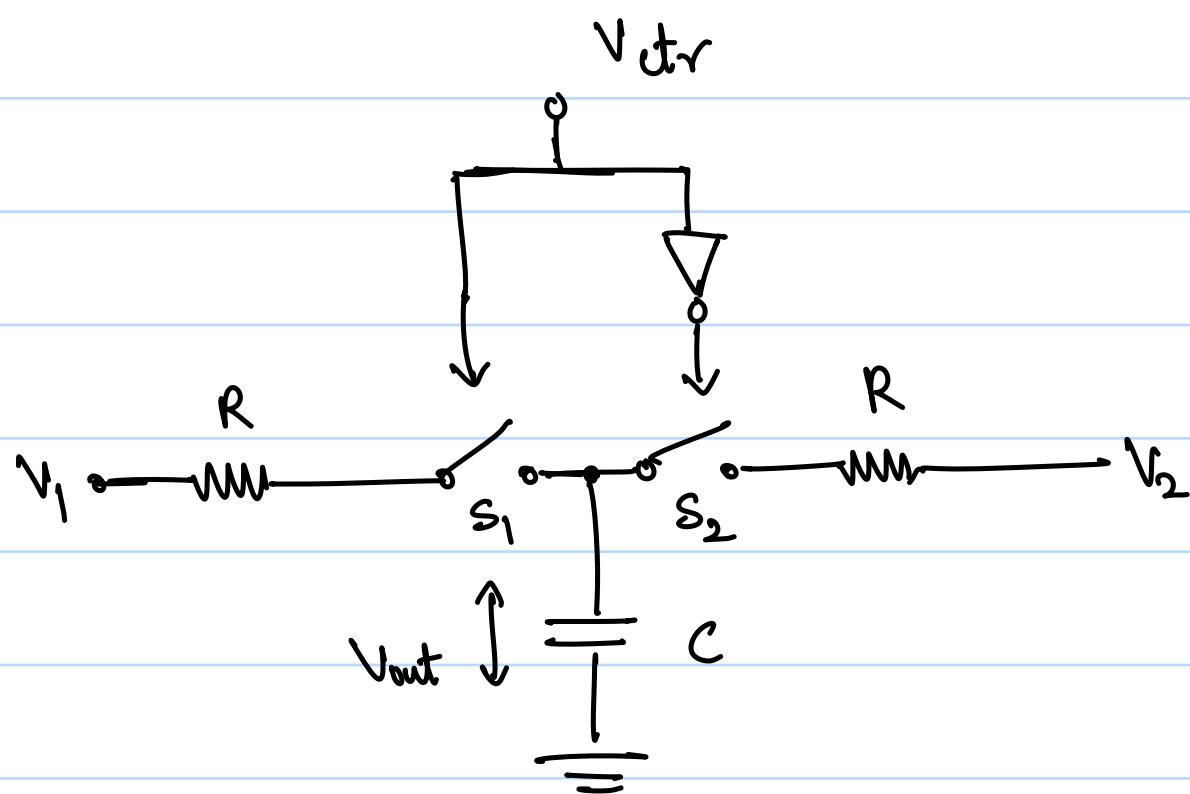



Here, $V_{out} = \begin{cases} V_2(1 - e^{-t/RC}), & V_{ctr} = 0 \\ V_1(1 - e^{-t/RC}), & V_{ctr} = 1 \end{cases}$

If there is no resistance involved, the current through the capacitor will be a Dirac impulse, infinite for an infinitesimal time.

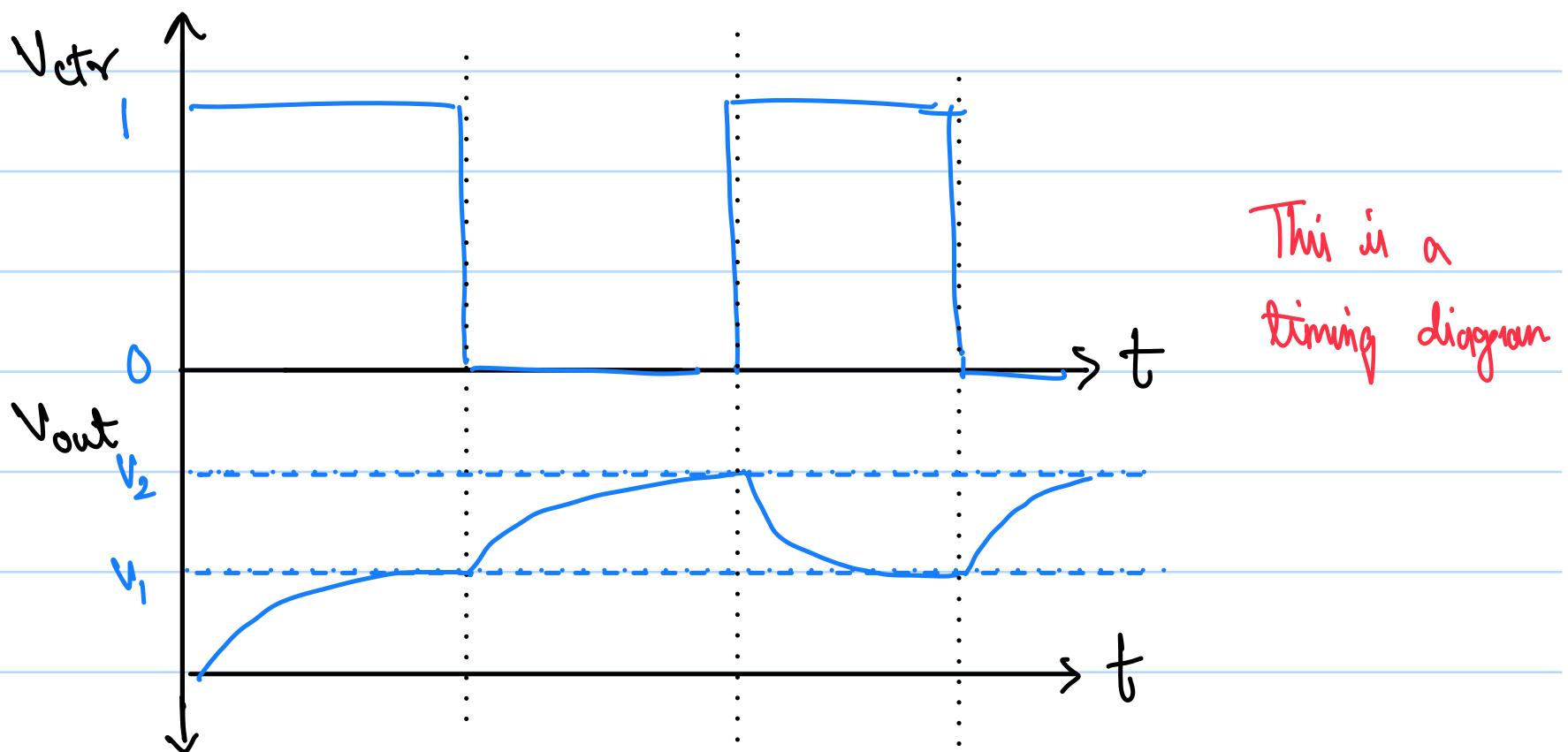($i = C \frac{dV}{dt}$, dt is very small)




3)

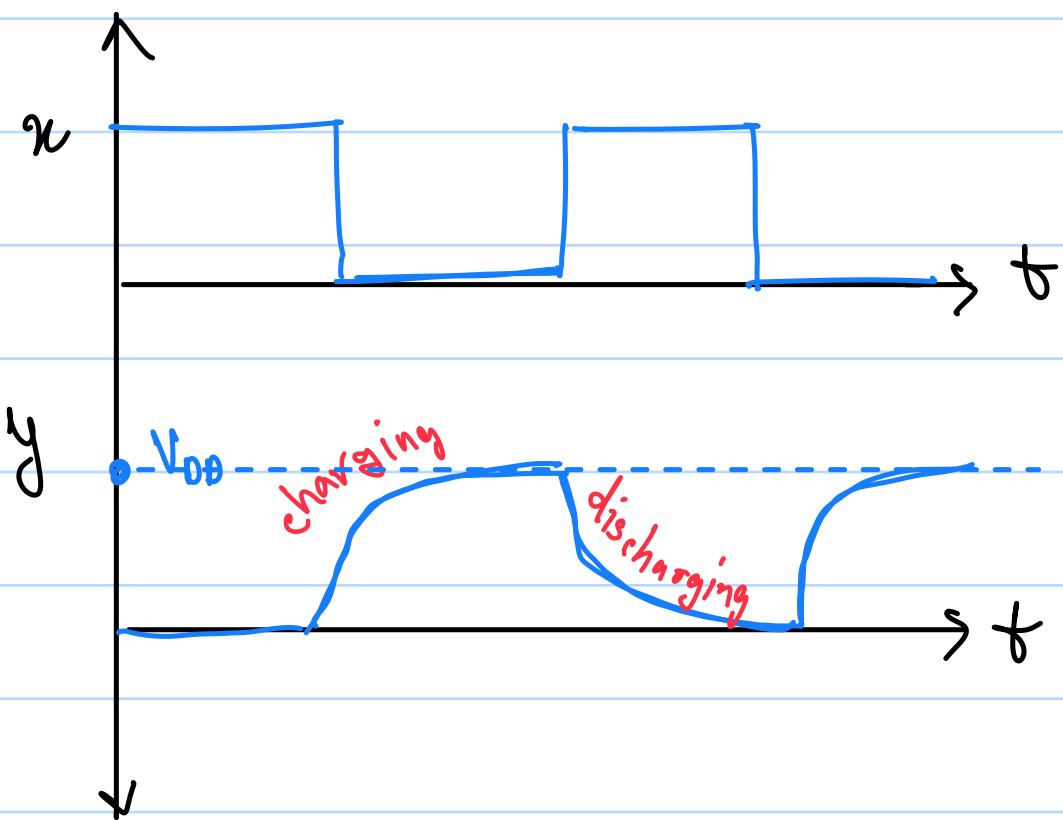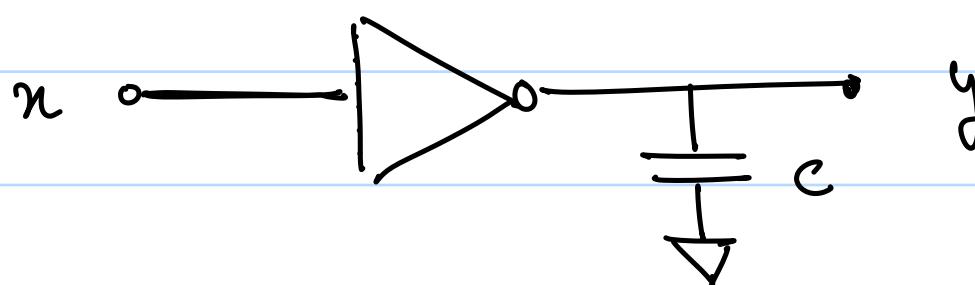


- The charging and discharging speeds of the capacitor are dependent on the RC / time constants of the circuit.

If RC is very large,

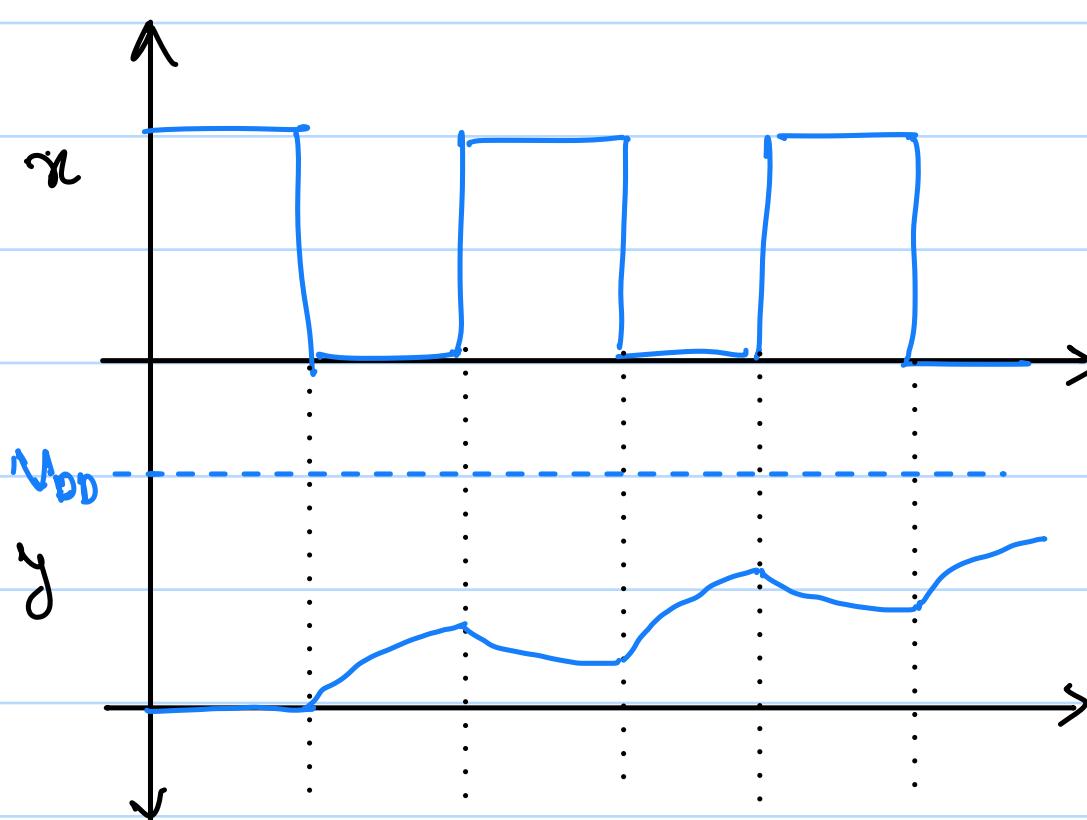

The capacitor is not fast enough to reach V_{DD} and zero, so information is lost.

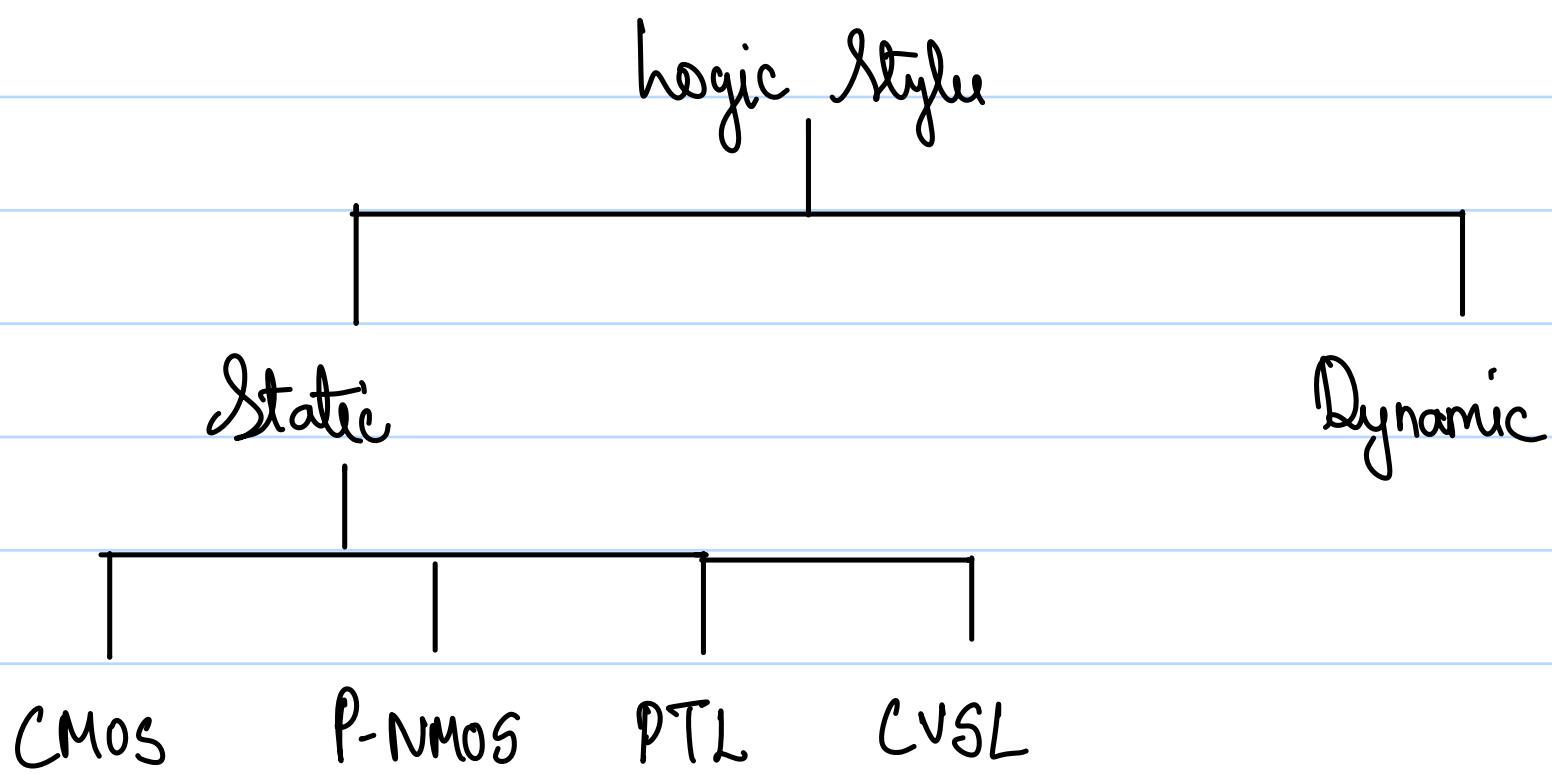
- Because of this, the RC parameters of the circuit must be fast enough to handle the input speed/frequency.



Circuit Design

Combinational Sequential Memory


4)

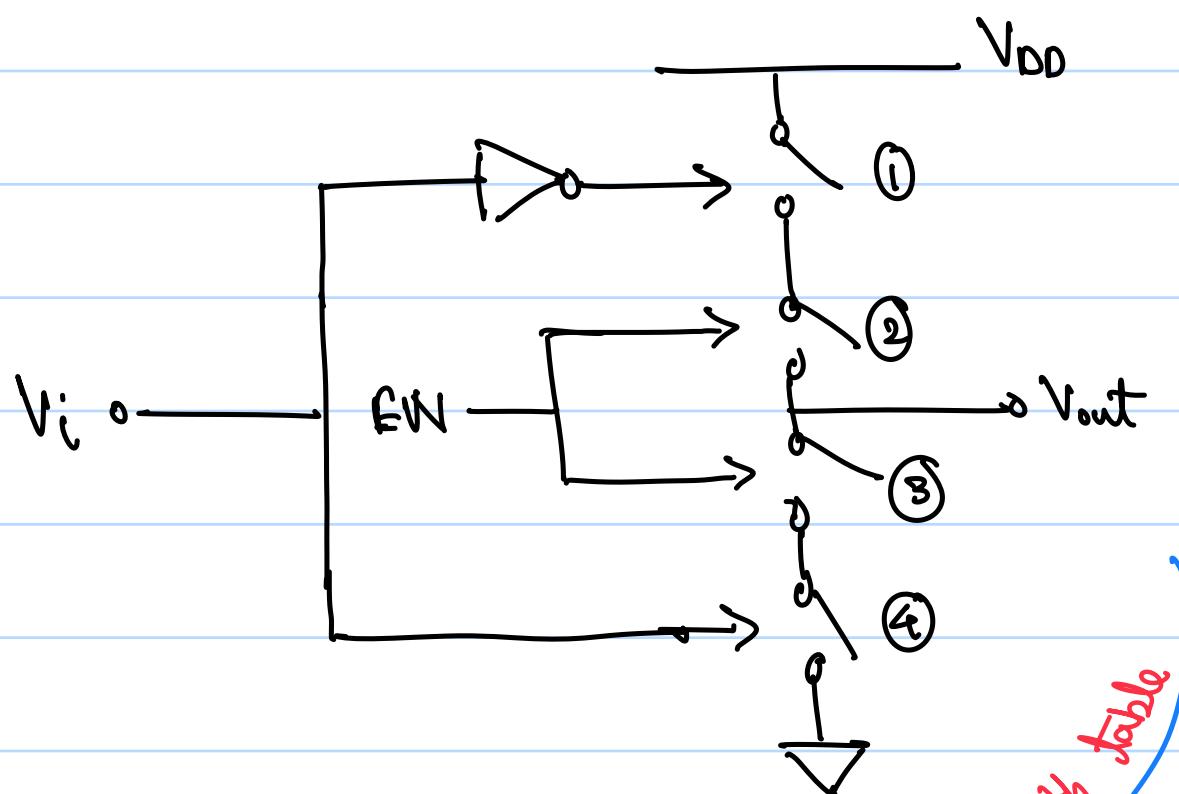


truth table

EN	V _i	V _o
0	0	Z
0	1	Z
1	0	V _{DD}
1	1	0

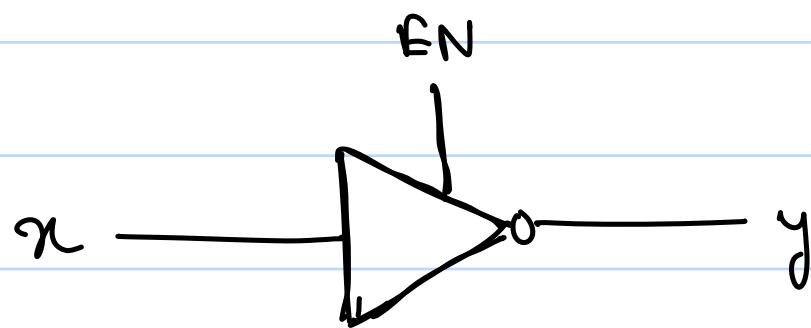The above device acts like an inverter if $EN = 1$. This is the design of a tri-state inverter.




5)

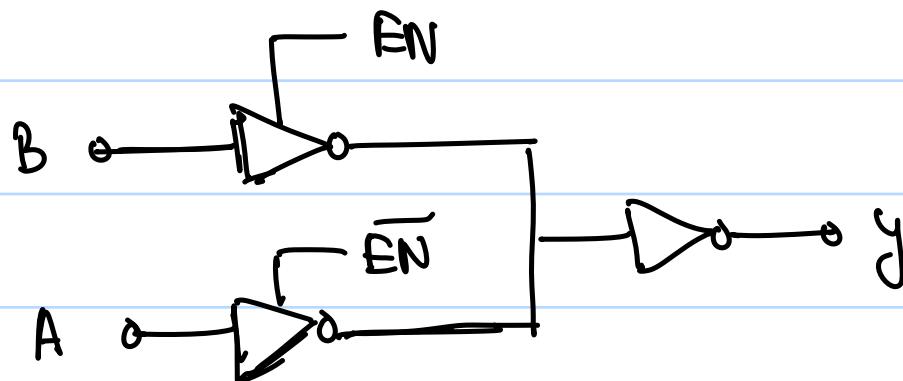

Truth Table:


EN	Y
0	A
1	B

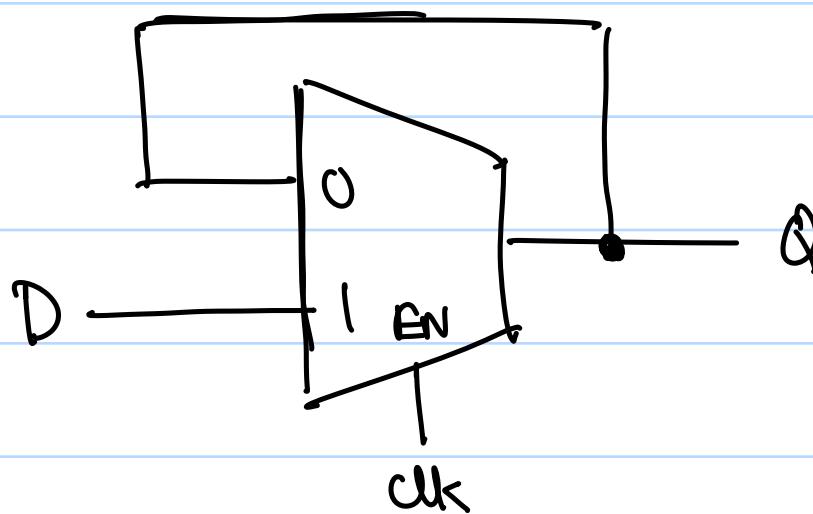- Due to the high impedance, the output of one tri-state inverter will not be affected by the other, since one output is always z .
- The above device will act as a 2×1 MUX, which can be used to design devices like gates and latches.



Level Triggered D-Latch


→ SPICE :-

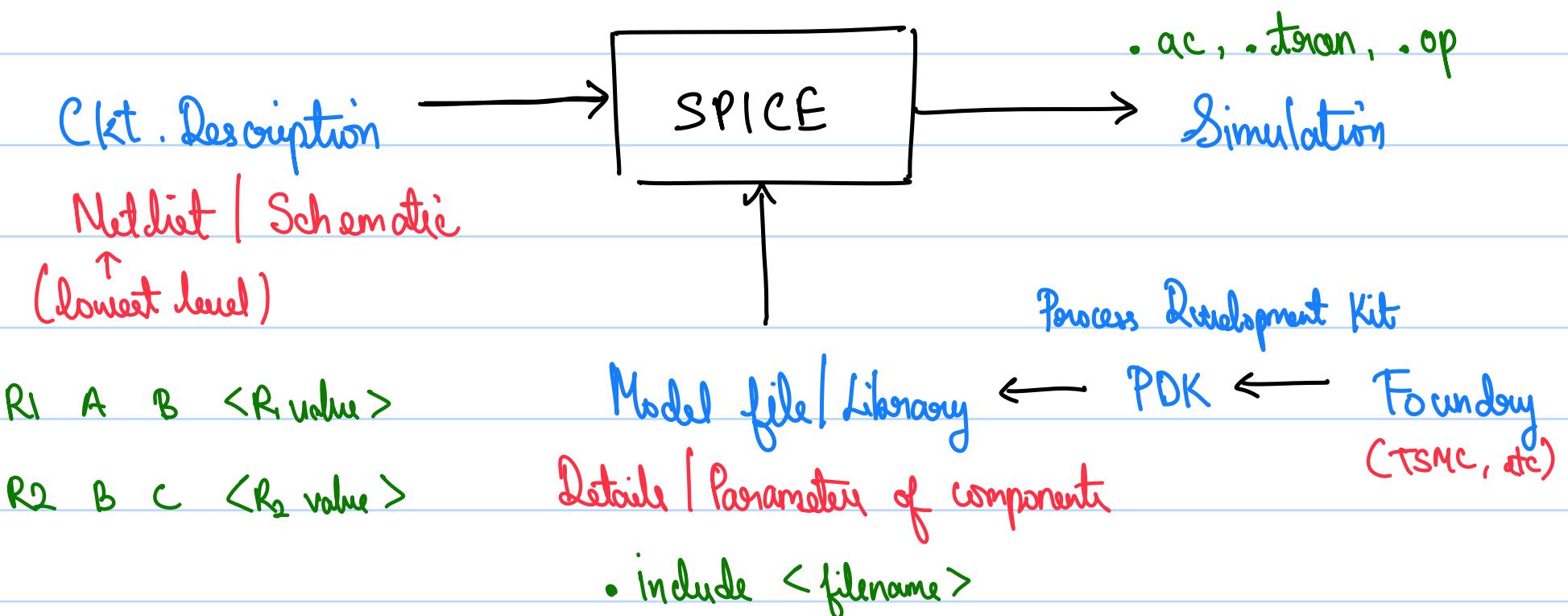

→ Technology Node:

- To make a semiconductor chipset on a substrate, we use a "stencil" of the circuit layout.
- In the chipset, there are multiple metal layers on top of the substrate, to provide the interconnection between the MOSFETs.
- Within the MOSFETs, there are multiple dimensions that vary between them, depending on the usage of that MOSFET
- The minimum of those dimensions, ie, minimum feature length among the MOSFETs is deemed as the "technology node" of that MOSFET. Usually minimum channel length.
- 3nm (N3) node - Retail products released
- 2nm (N2) node - Will release early next year.

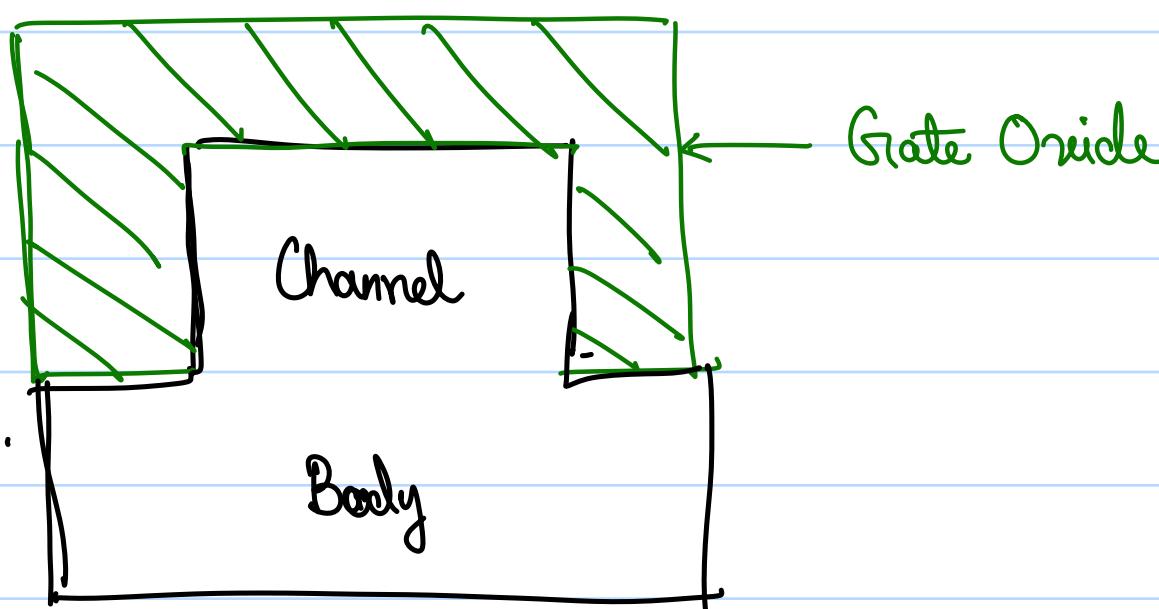- < 22nm - FinFETs are used instead of MOSFETs.



View of FinFET through Source/Drain

In FinFETs, the oxide wraps around the channel, enabling better inversion at a lower gate potential, better than MOSFETs.

- A14 - 1.4nm node } In development.
- A7 - 0.7nm node }

- 180nm is still widely used, in devices that do not require extremely high competition.

- Lower transistor size \Rightarrow lower cost per transistor.

- Clock Speed:

- Recently the clock speed of processes has saturated.

- Since the packing density has increased by a lot, the heat and leakage of the transistors have increased by a lot.

- These factors made it difficult for clock speed to improve as fast as the technology node.

→ Shannon's Expansion :-


- For any function $f(x_1, x_2, x_3 \dots x_n)$,

$$f(x_1, x_2, x_3 \dots x_n) = x_1 f(1, x_2, x_3 \dots x_n) + \bar{x}_1 f(0, x_2, x_3 \dots x_n)$$

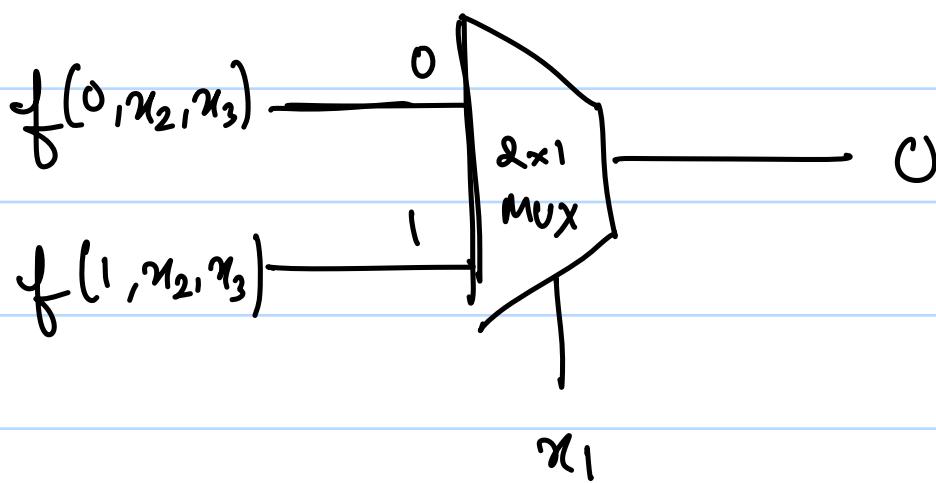Example: Expand $f(x_1, x_2, x_3) = \bar{x}_1 \bar{x}_3 + x_1 x_2 + x_1 x_3$. w.r.t x_1

$$\Rightarrow f(x_1, x_2, x_3) = x_1 (x_2 + x_3) + \bar{x}_1 (\bar{x}_3)$$


- If we expand the function in this way, we can use a 2×1 MUX to implement the function, using x_1 as the selection variable.



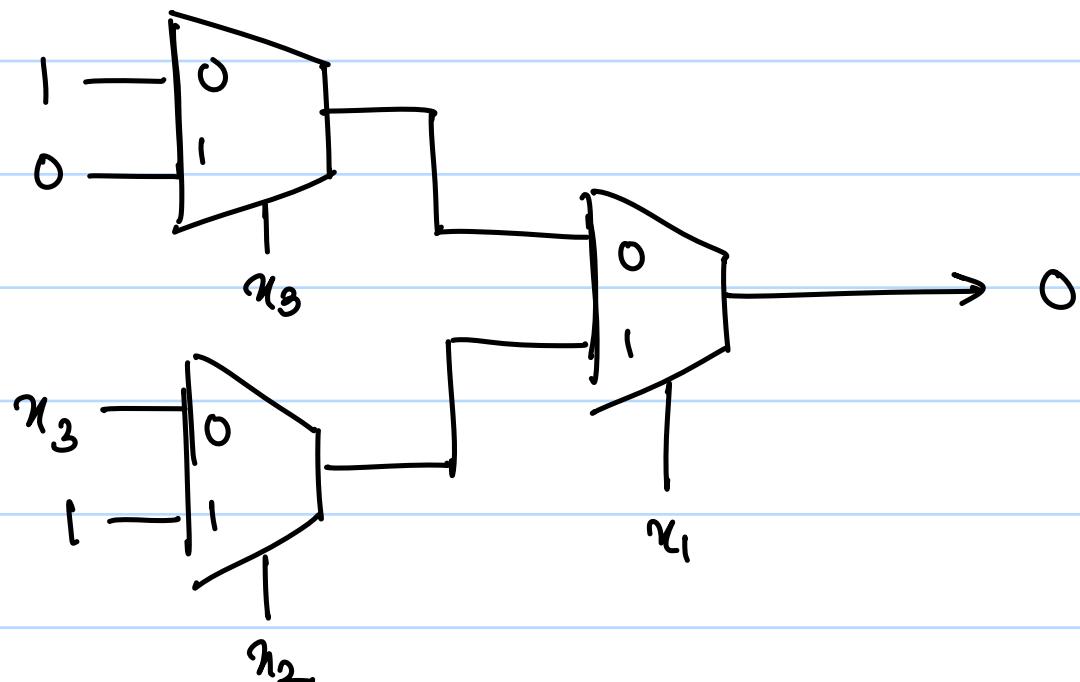
Example: Express the prev. function only using 2x1 MUXes.

$$\begin{aligned} f(x_1, x_2, x_3) &= \bar{x}_1 \bar{x}_3 + x_1 x_2 + x_1 x_3 \\ &= x_1 (x_2 + x_3) + \bar{x}_1 (\bar{x}_3) \end{aligned}$$

$$\begin{aligned} f(x_2, x_3) &= x_2 + x_3 \\ &= x_2(1) + \bar{x}_2(x_3) \end{aligned}$$



→ MOSFETs :-

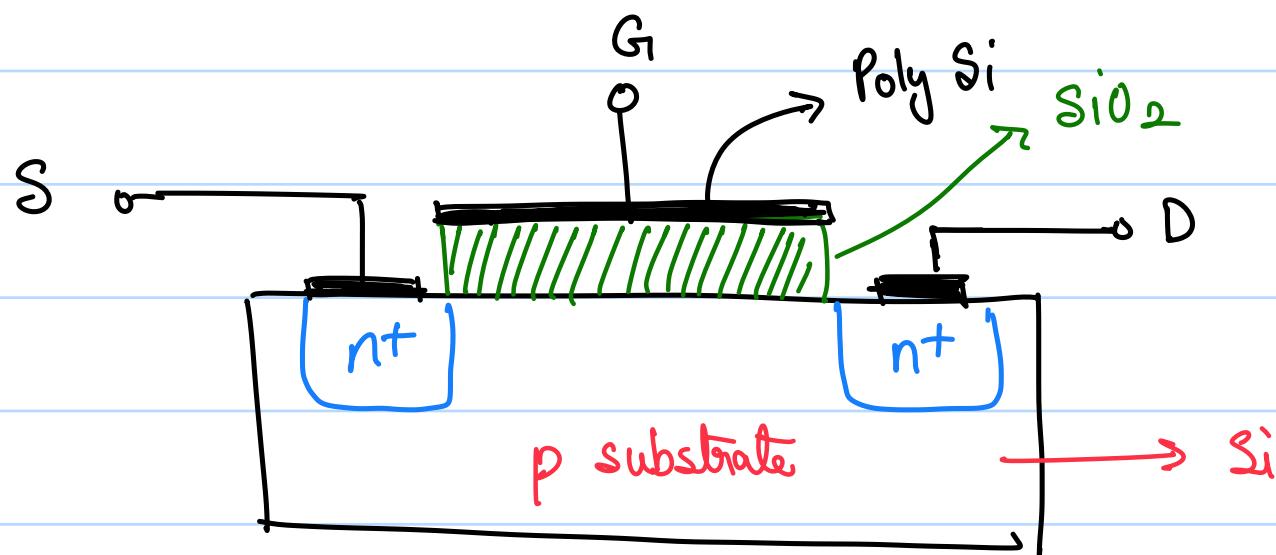


NMOS Structure

- Poly silicon is used in the gate terminal to simplify the manufacturing process, since silicon is the major element of a MOSFET.

- Let S and D be grounded and ,


1) $V_G < 0$

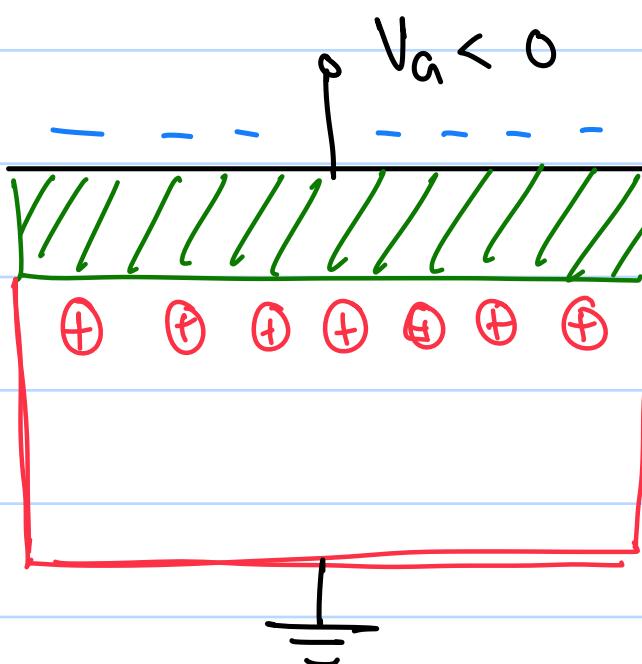

holes are attracted towards the gate

- This is accumulation mode of operation .


2) $V_G > 0$

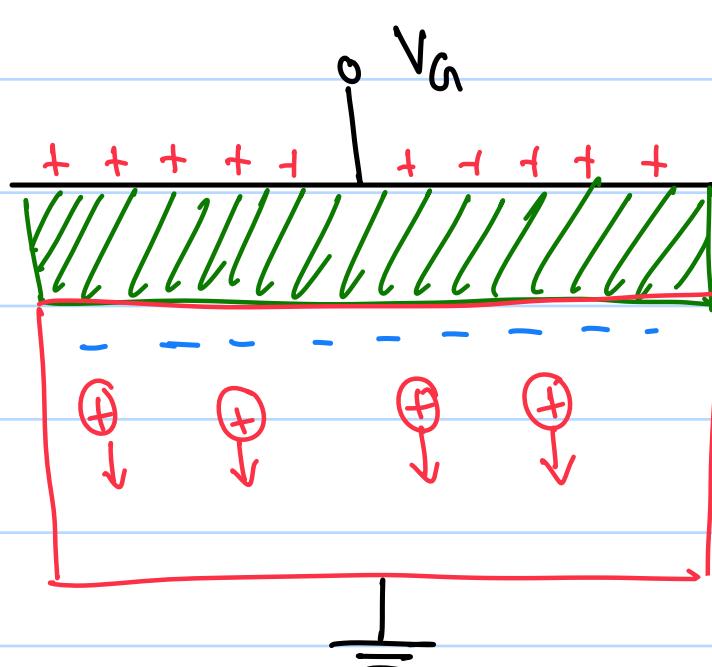

holes go away from gate, leaving -ve charge .


- This is depletion mode of operation .

3) $V_G \gg 0$

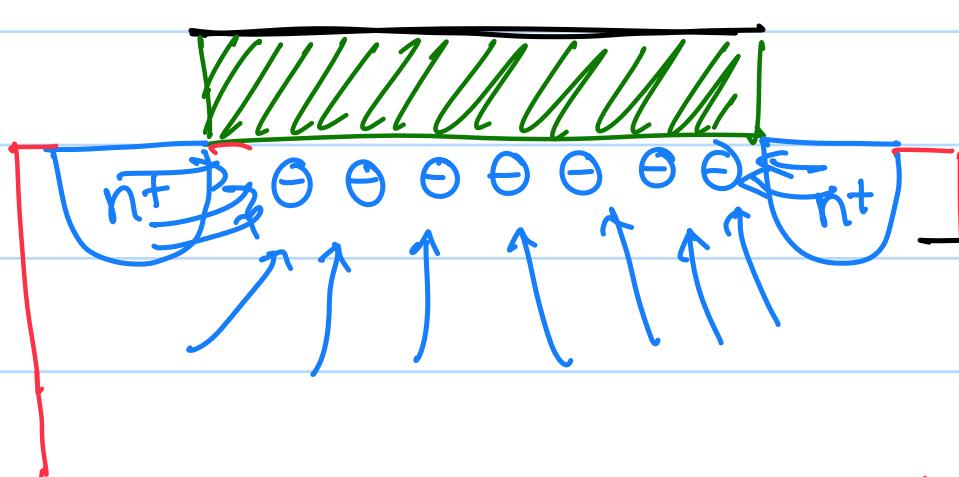

electrons are attracted from the substrate and (majority) from S and D

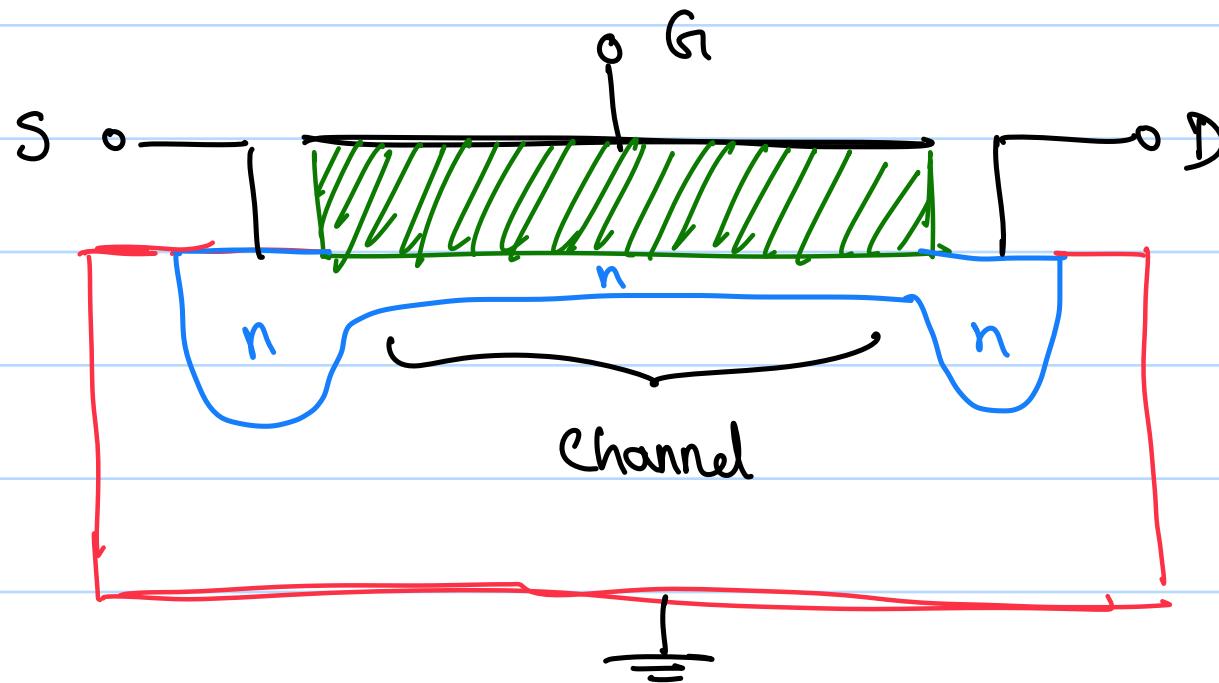
- The surface of the p-substrate becomes dominated by electrons, ie, becomes n-type.




- This is inversion mode of operation.

- If n_e at surface $< N_A$ (hole conc. of substrate), it is weak inversion / subthreshold mode.

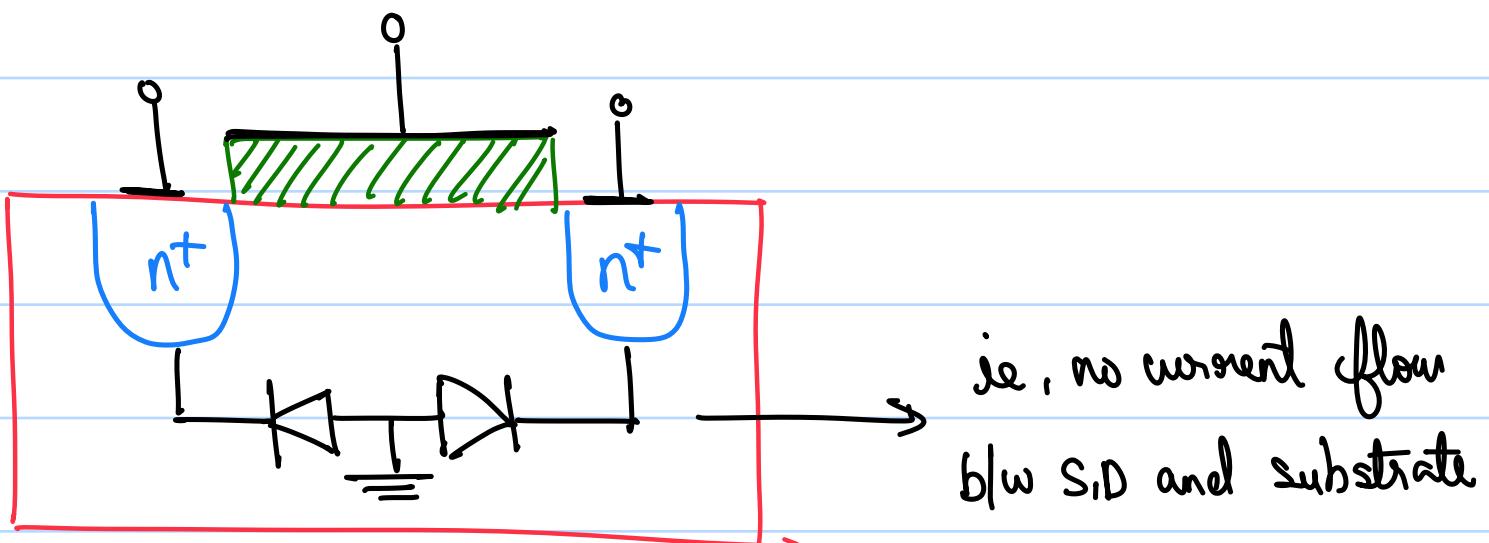- If n_e at surface $\geq N_A$, it is strong inversion. The min. gate voltage to attain strong inversion is V_{TH} (threshold voltage)




• 3D View:-

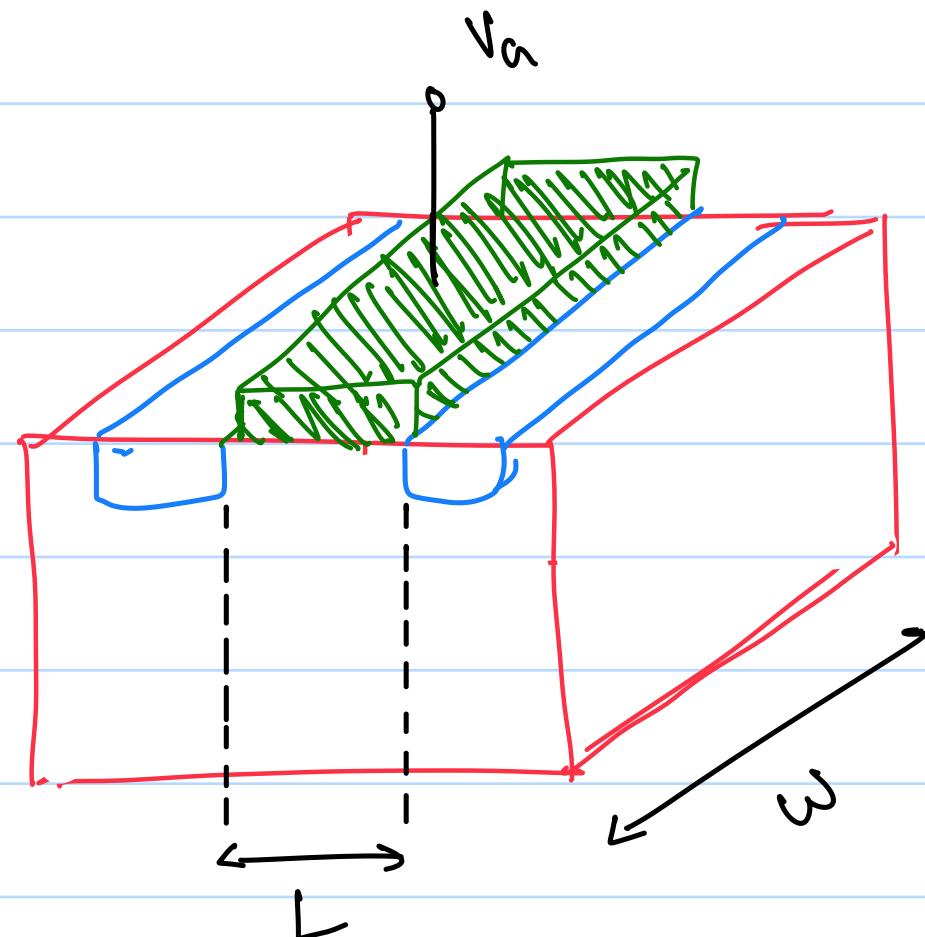

Since the n-channel is not perfectly conductive, it has some resistance to it, depending on the dimensions L and w.

Based on V_{AS}

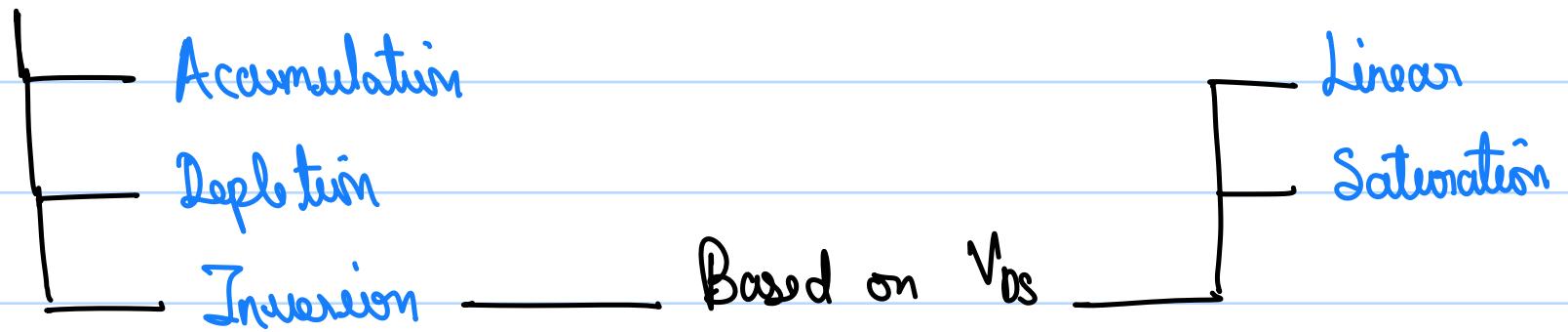

1) $V_{AS} \leq 0 \Rightarrow I_D = 0 + V_{DS}$. Accumulation mode has zero channel.

2) $0 < V_{AS} < V_{TH} \Rightarrow I_D \approx I_{D0} e^{\frac{V_{AS}-V_{TH}}{nVt}}$. V_t - thermal voltage.

Subthreshold conduction.

3) $V_{AS} > V_{TH}$ & $V_{DS} < V_{AS} - V_{TH} = V_{ov}$. (Overshoot voltage)

$$I_D = \frac{1}{2} \mu_n C_o \frac{w}{L} \left(2V_{ov}V_{DS} - \frac{V_{DS}^2}{2} \right) \rightarrow \text{Linear Mode of Opn.}$$

If $V_{DS} \ll V_{OV}$,

$$I_D = \left(\mu_n C_o x \frac{W}{L} V_{OV} \right) V_{DS}$$



$$\Rightarrow R = \frac{1}{\mu_n C_o x \frac{W}{L} V_{OV}}$$

4) $V_{GS} > V_{TH}$, $V_{DS} \geq V_{GS} - V_{TH}$

$$\Rightarrow V_{GS} - V_{DS} \leq V_{TH}$$

$$\Rightarrow \underline{V_{DS} \leq V_{TH}}$$

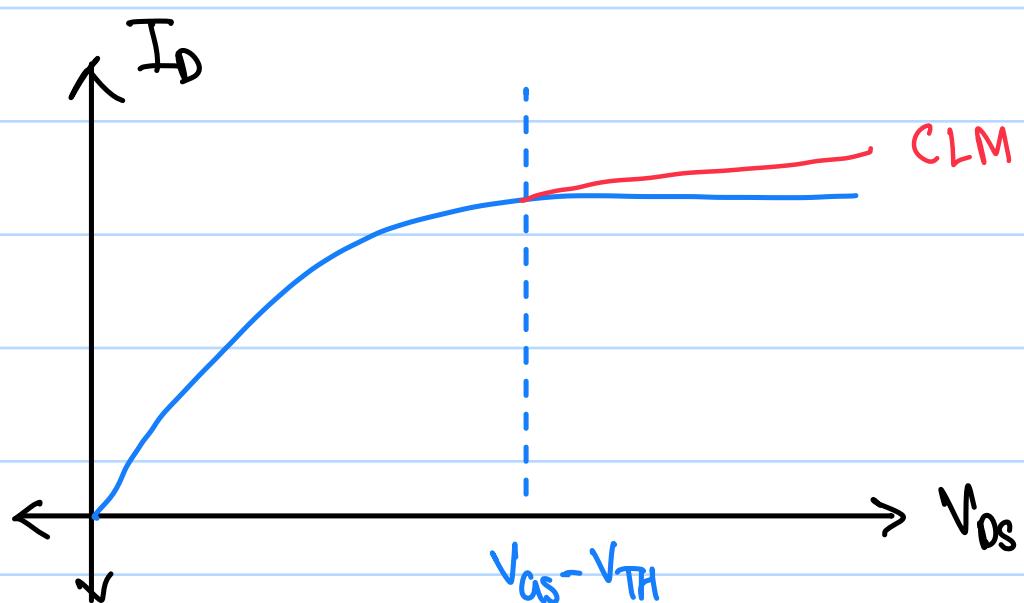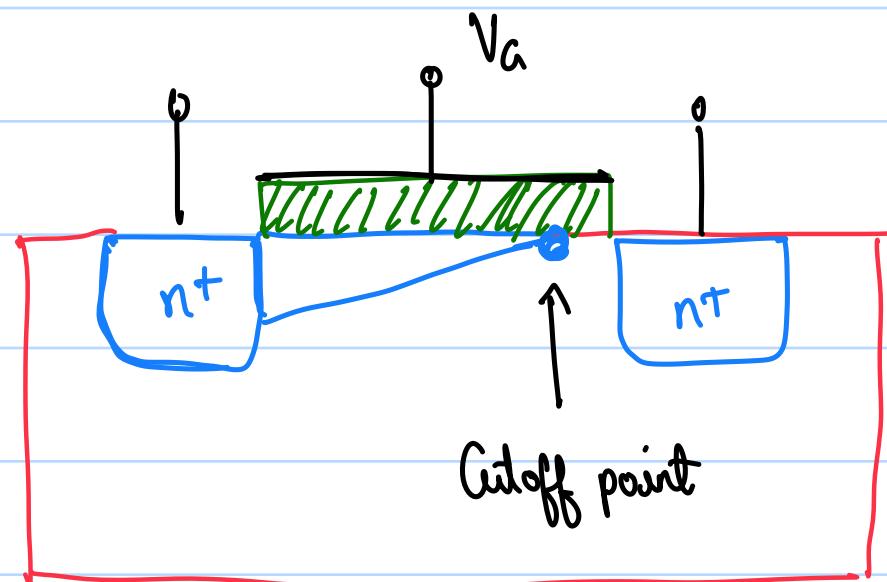Since $V_{DS} \leq V_{TH}$, the channel will cease to exist near the drain, since potential at the point will be lesser than threshold.



Beyond the cutoff point, the charge density is very low (depletion mode). Let linear charge density there be Q_d . $Q_d \approx 0$.

$$dQ = Q_d \cdot dx$$

$$\frac{dQ}{dt} = Q_d \frac{dx}{dt}$$

$$= I = Q_d V_d$$

$$= V_d = \frac{I}{Q_d} \Rightarrow \lim_{Q_d \rightarrow 0} \frac{I}{Q_d}$$

$\therefore V_d \rightarrow \infty$ for finite I .

\therefore The electrons are swept almost instantaneously across the cutoff point into the drain.

$$I_{DS} = \begin{cases} \mu n C_o \frac{W}{L} (2(V_{GS} - V_{TH})V_{DS} - \frac{V_{DS}^2}{2}), & V_{GS} > V_{TH}, V_{DS} < V_{ov} \\ \frac{1}{2} \mu n C_o \frac{W}{L} (V_{GS} - V_{TH})^2, & V_{GS} > V_{TH}, V_{DS} > V_{ov} \\ 0, & V_{GS} \ll V_{TH} \\ I_{DSS} e^{\frac{V_{GS}-V_T}{nVt}} [1 - e^{\frac{V_{DS}}{4}}], & V_{GS} < V_{TH} \end{cases}$$

(Subthreshold leakage)

• PMOS:

$$I_{SD_{PSI}} = \frac{1}{2} \mu p C_o \frac{W}{L} [V_{SA} - |V_T|]^2$$

$$V_{SA} \geq |V_T| \quad \&$$

$$V_{SD} \geq V_{SA} - |V_T|$$

$$I_{SD\text{plin}} = \mu_p C_{ox} \frac{W}{L} \left[(V_{SD} - |V_T|) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

• Second-Order Effects :-

1) Channel Length Modulation :-

Since the cutoff point moves further towards the source, as V_{DS} increases, I_D actually increases with V_{DS} even during saturation.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

λ CLM Parameter

$$\lambda V_{DS} = \frac{\Delta L}{L}$$


2) Body Biasing :-

If V_{BS} is increased, the threshold voltage of the MOSFET is decreased.

$$V_{TH} = V_{TH0} + \sqrt{2\psi_s + V_{SB}} - \sqrt{2\psi_s}$$

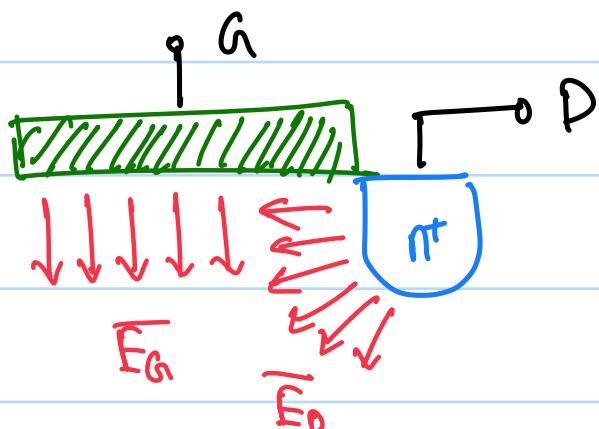3) Drain Induced Barrier Lowering :-


In short channel MOSFETs, the drain voltage will aid in the inversion of the channel.



Because of this aid, the threshold voltage of the MOSFET will be lower.

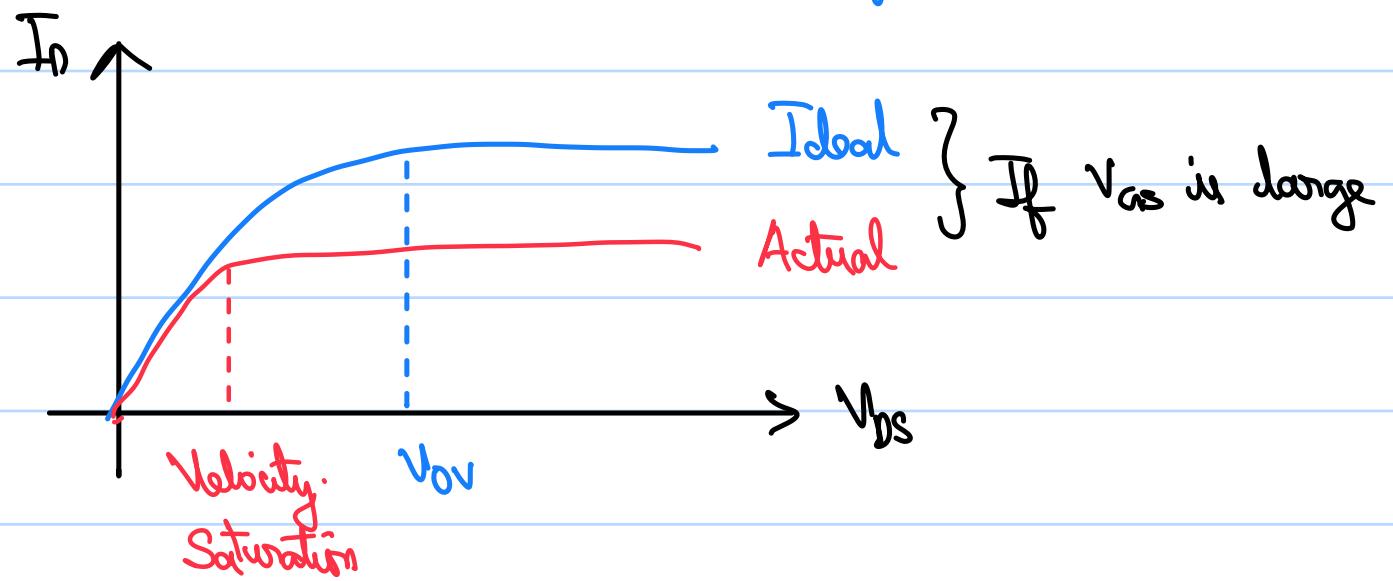4) Velocity Saturation :-

For each channel, there is a certain V_d at which mobility degradation occurs due to scattering of the charge carriers. Prominent if V_{as} is large.




If V_{as} is low, overdrive voltage is attained before velocity saturation, so the effect is not visible.

• Switch I_{ON}, I_{OFF} :-

- I_{ON} : Current through the switch when it is in the ON position.
- I_{OFF} : Current through the switch when it is in the OFF position.
- Ideally I_{OFF} should be zero, but it is non-zero due to effects like leakage.

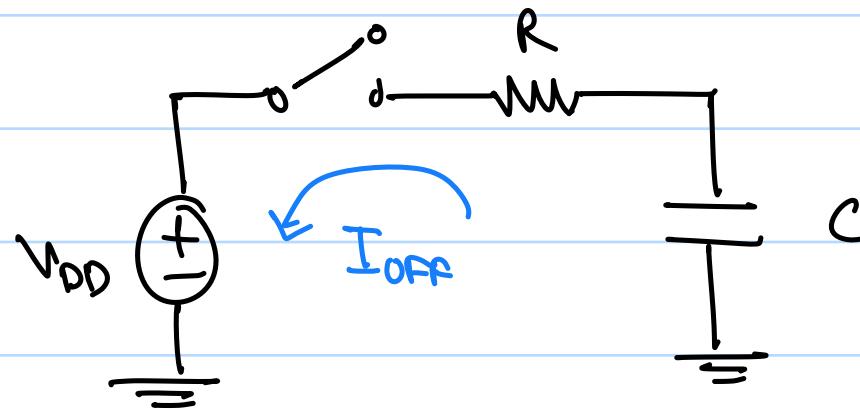
- t_{hold} : Time taken for a capacitor to discharge in an RC circuit when the switch is OFF.



$$\text{For a good circuit, } t_{\text{hold}} \geq \frac{1}{2} \frac{C V_{DD}}{I_{\text{off}}}$$

- o MOS Capacitor:



- i) Accumulation Region:-

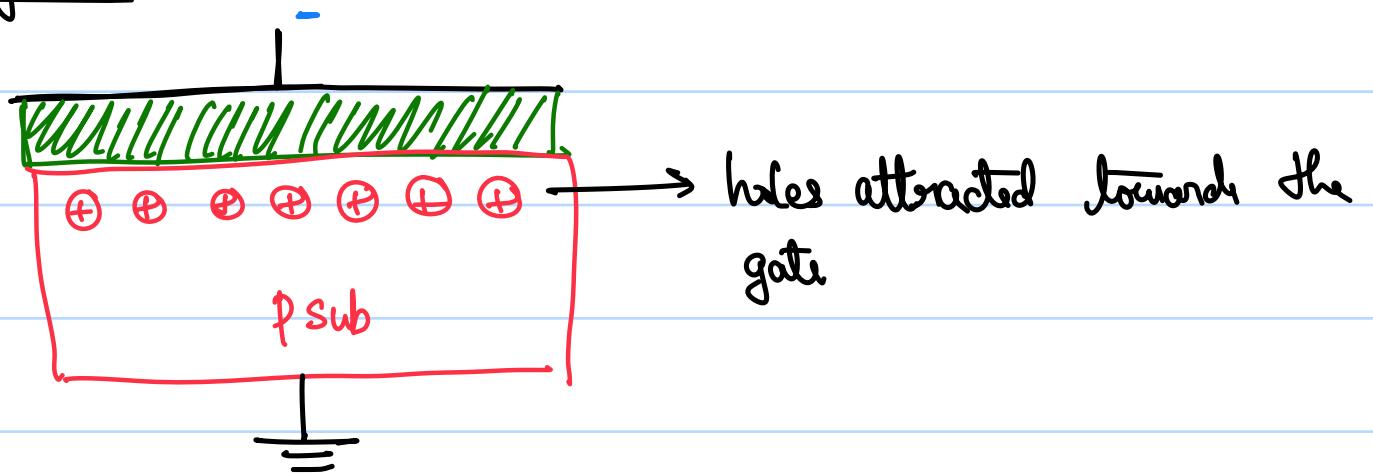


The capacitor acts like a normal parallel plate capacitor.

$$C = \frac{\epsilon A}{d} = \frac{\epsilon W L}{t_{ox}}$$

2) Depletion and Inversion :-

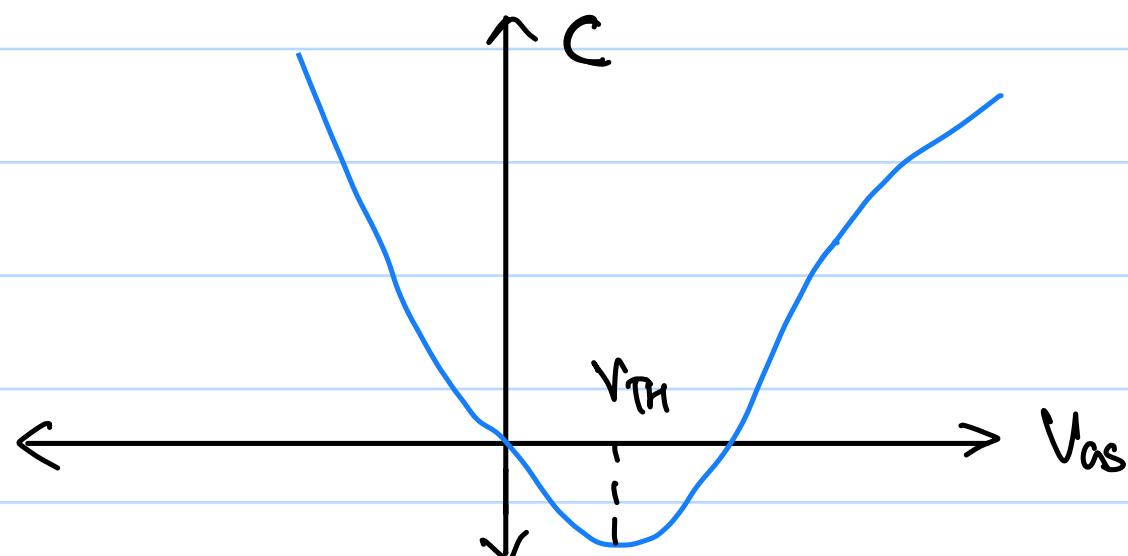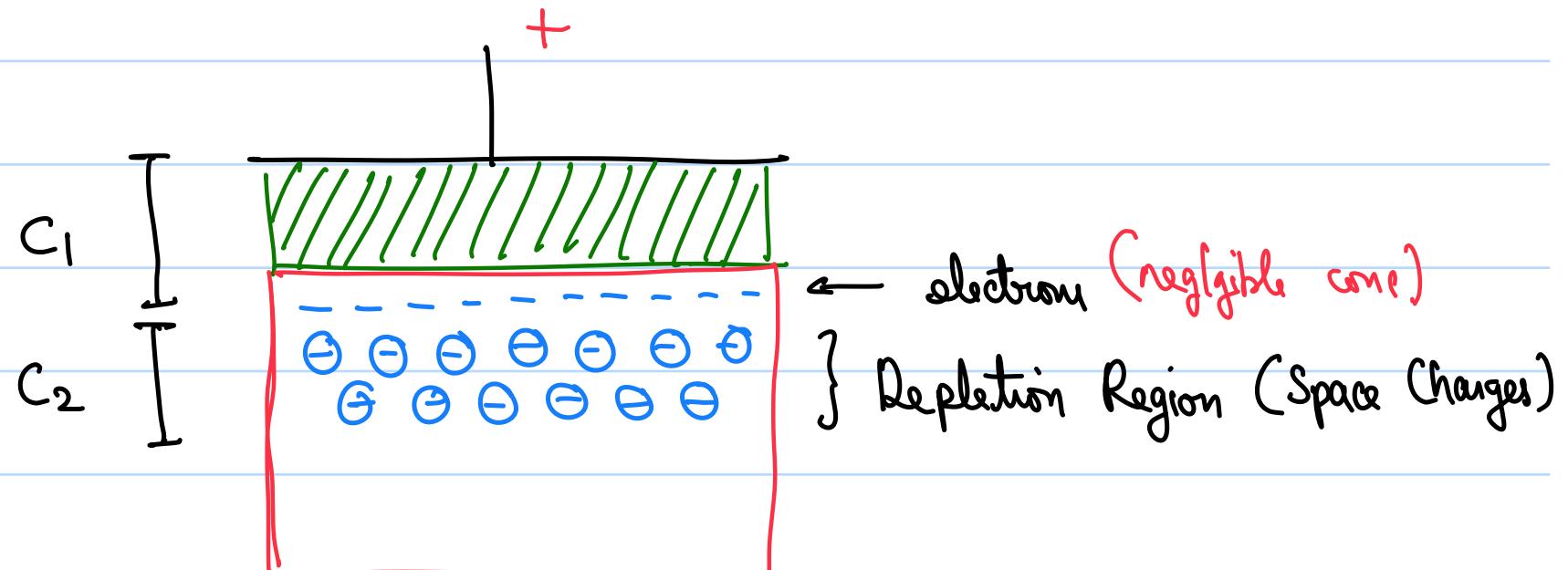

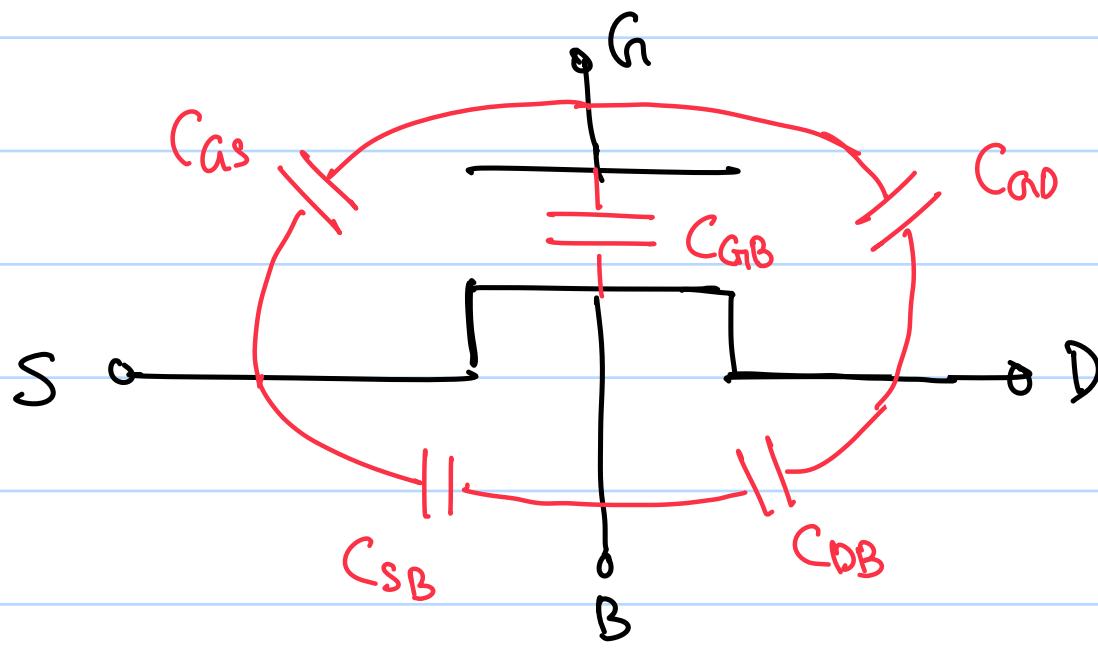• Capacitance in the Modes of Operation :-



1) In Cutoff: $C_{GS} = C_{GD} = wC_{ov} \rightarrow$ Overlap Capacitance

$$C_{ov} = WL C_{ox}$$

2) In Linear :- $C_{GD} = C_{GS} = \frac{WLCon}{2}$

$$C_{GD_{ov}} = C_{GS_{ov}} = WLCon$$

3) In Saturation :- $C_{GS} = WLCon + \frac{2}{3}WLCon$

5) Mobility Degradation :-

The mobility of the channel depends on the electric field inside the channel as follows,

$$\mu \propto E^0 \text{ for } E < 10^3 \text{ V/cm}$$

$$\mu \propto \frac{1}{\sqrt{E}} \text{ for } E \approx 10^3 - 10^4 \text{ V/cm}$$

$$\mu \propto \frac{1}{E} \text{ for } E > 10^4 \text{ V/cm}$$

Note: Short Channel MOSFETs are those MOSFETs whose channel length is of the same magnitude as the dimensions of the source / drain depletion regions.

6) Tunneling :

Tunneling is the conduction of current through the gate terminal. Significant in short channel MOSFETs.

→ Parametric Extraction :-


- $V_{GS} \geq V_T$ and $V_{DS} \ll (V_{GS} - V_T)$ [Deep Trickle]

$$\Rightarrow I_D = \mu_n C_o \frac{w}{L} (V_{GS} - V_{TH}) V_{DS}$$

is of the form $y = m(x - x_0)$ [I_D v/ V_{GS} sweep]

x_0 is the x intercept of the line

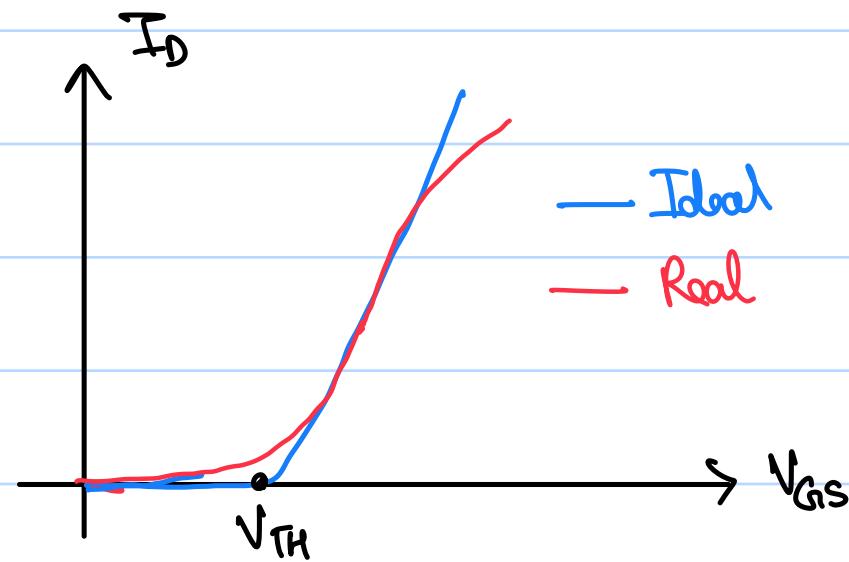$\therefore V_{TH}$ is the x intercept of the above line



We take the point of maximum slope to construct the line equation, to avoid mobility reducing second order effects.


$$\mu = \frac{\mu_0}{1 + \Theta(V_{GS} - V_{TH})}$$

If $V_{GS} \approx V_{TH}$

$$\mu = \frac{\mu_0}{1 + \Theta(V_{GS} - V_{TH})} \approx \underline{\underline{\mu_0}} \quad [\text{Maximum value}]$$


The effect of all the second order effects is modelled using Θ . So when $V_{GS} \approx V_{TH}$, ie at max mobility, Θ 's effect is low.

- C-V Characteristics :-

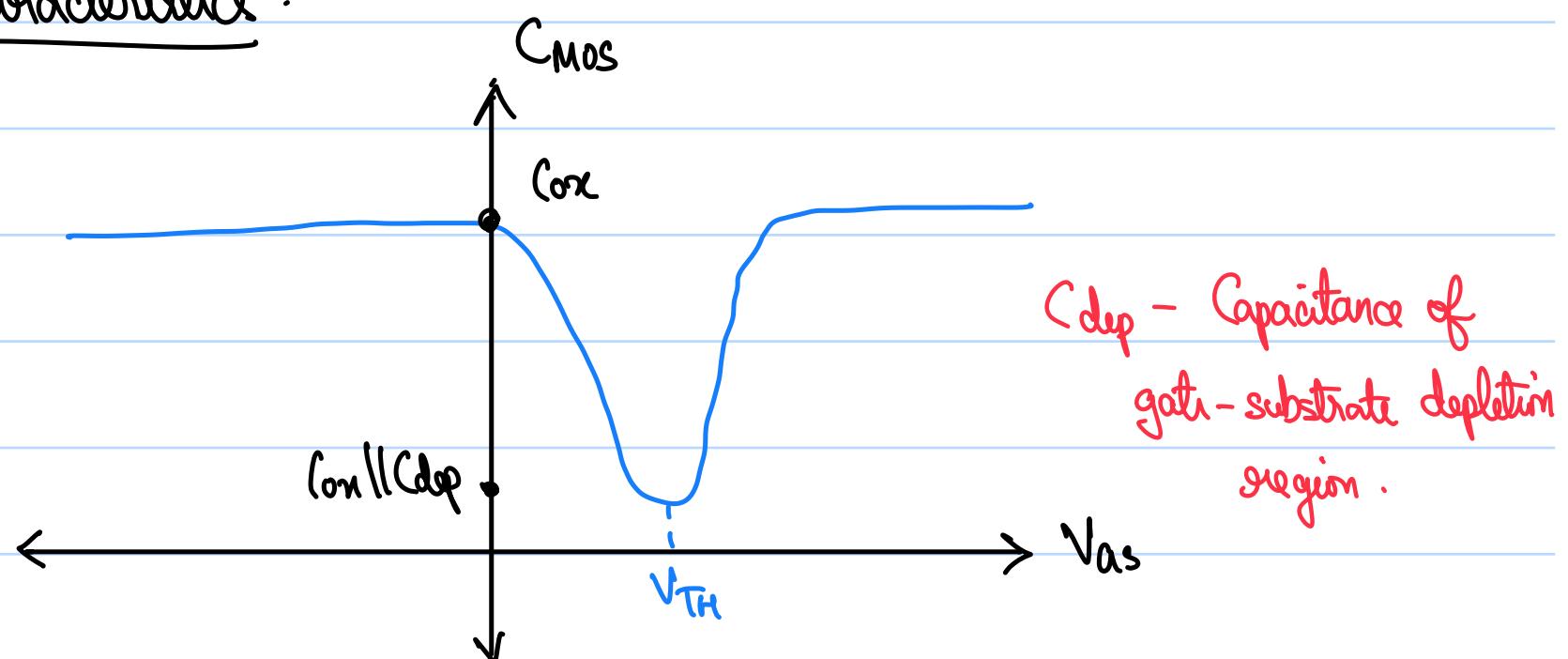

- CMOS Static Logic Devices :-

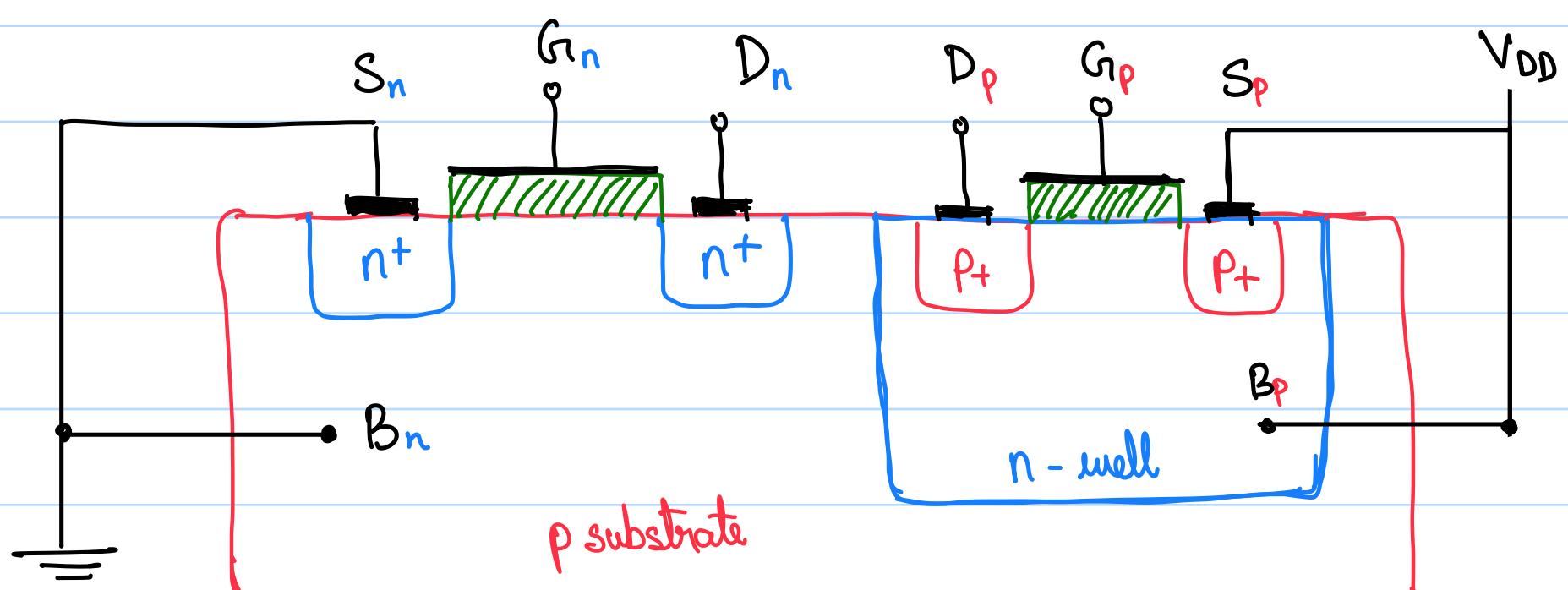- CMOS - Complementary MOS (Combination of PMOS and NMOS)



CMOS Structure

(Well settled)


- Static - Well defined op states : Either 0 (gnd) or 1 (V_{DD})

- CMOS Devices will have a Pull-up and Pull-down networks in each logic stage.

Pulls op and ip to 0,1 levels


- Purpose of Logic Stage : To evaluate i/p and pull the o/p up or down to match V_{DD} or GND .
 - No static power consumption , ie , while i/p s are unchanged the power consumption is zero . Circuit still draws power when the i/p s are changed , ie , switching power is non-zero . (dynamic power)
 - CMOS Inverter :- (Rabaray's CMOS Design textbook & Weste)
- 1) Transfer Characteristic (VTC) (output vs input)
 - 2) Noise Margin
 - 3) Dynamic Characteristics (Rise/fall, time delay)
 - 4) Inverter Design Flow
 - 5) Efficacy
 - 6) Inverter in Other Logics

- Circuit:

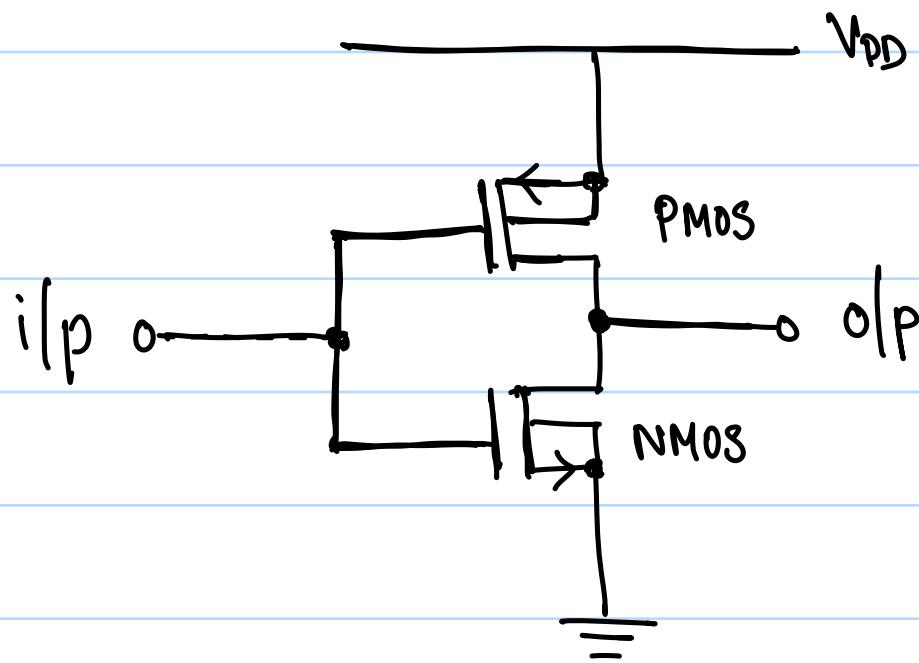

- The design procedure of the inverter needs to consider things like time delay, load impedance, output load type, etc.

Example:

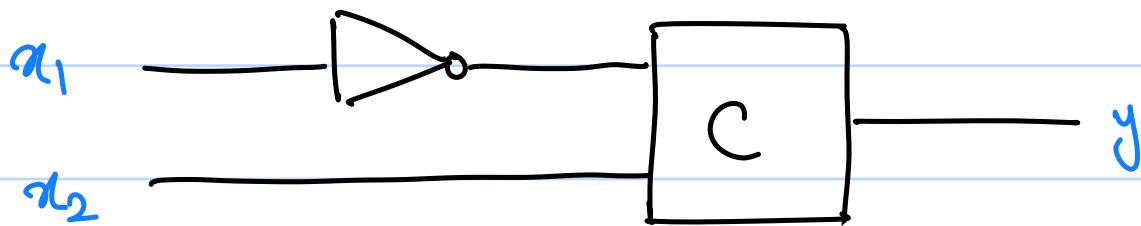


Since the inverter adds some delay, x_1 and x_2 will not reach C at the same time.

- Pull Up and Pull Down Network :-

- Pull Up : Pulls ilp to VDD

- Pull Down : Pulls ilp to GND

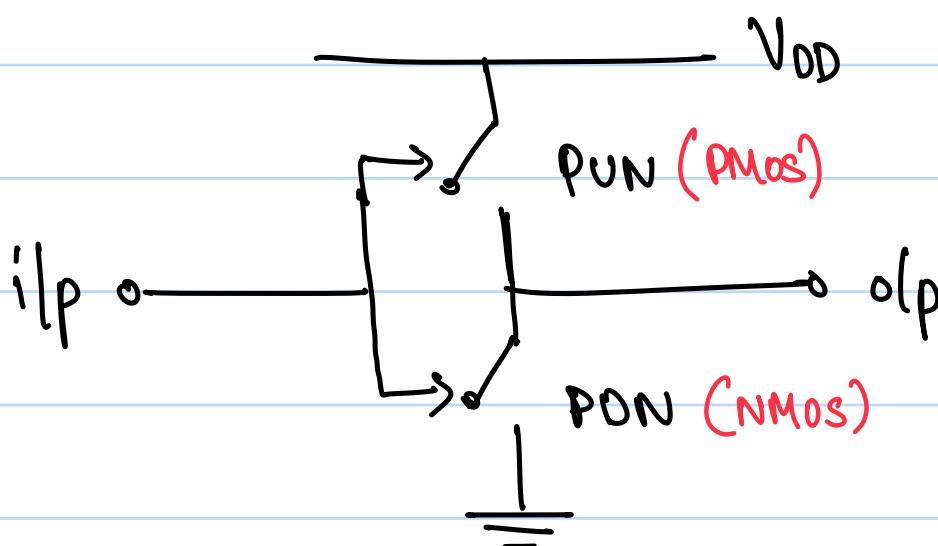

PUN and PDN are never on simultaneously.


- VTC of CMOS Inverter :-

- The VTC of a CMOS Inverter can be analyzed by plotting the different modes of the PMOS and NMOS.


- On condition for M_n : $V_{GSn} = V_{ip} \geq V_{Tn}$
- " " " " M_p : $V_{Sop} = V_{DD} - V_{ip} \geq |V_{Tp}|$
 $= V_{ip} \leq V_{DD} - |V_{Tp}|$

Condition	M_n	M_p	o/p
$V_{ip} = 0$	OFF	ON	V_{DD}
$V_{ip} = V_{DD}$	ON	OFF	0 } Inverter Behavior $V_{ip} \geq V_{Tn}$ $V_{ip} \leq V_{Tp} + V_{DD}$ $(V_{Tp} \leq 0)$

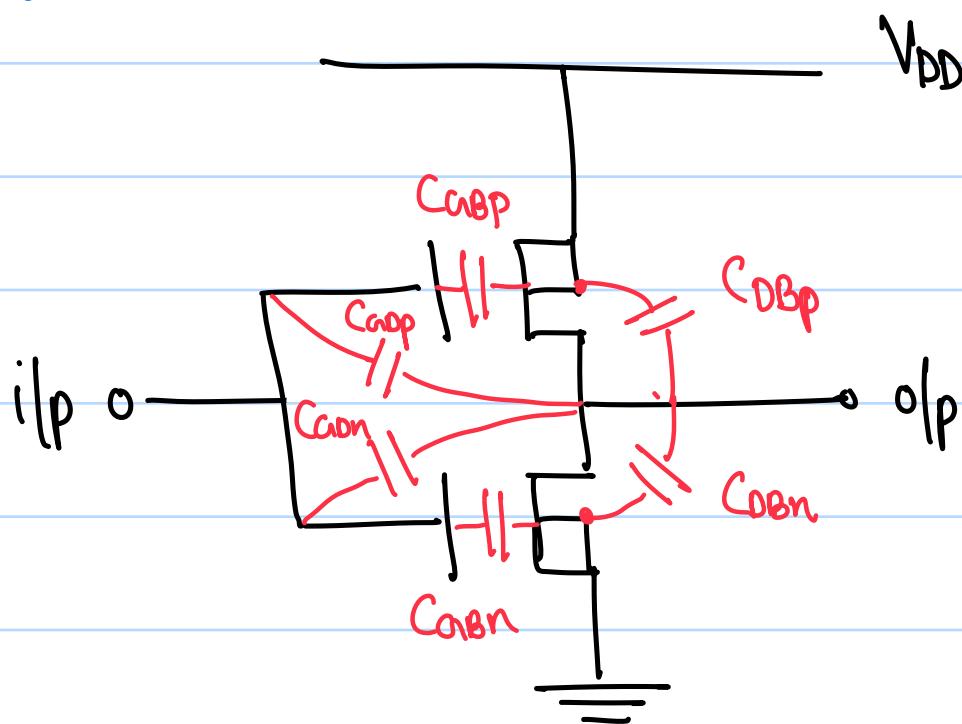- Modelling the capacitances in the inverter



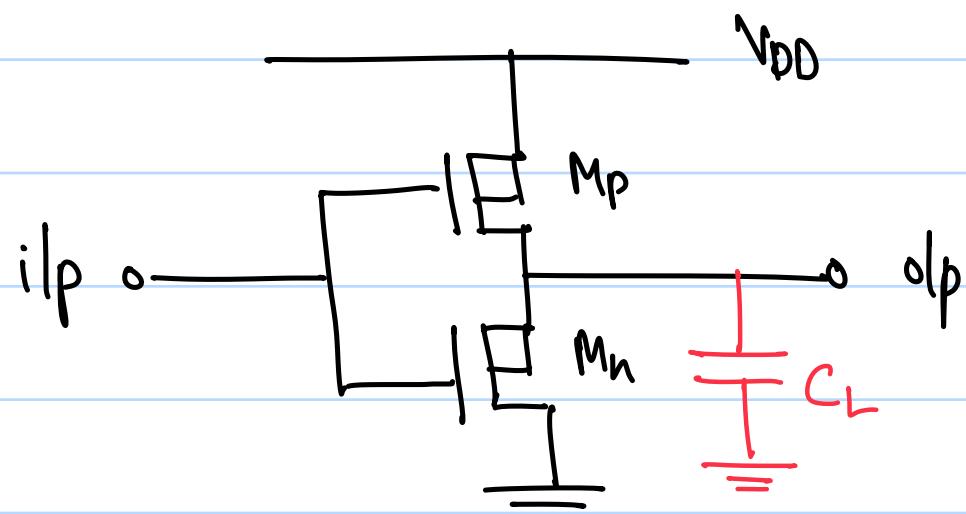Since at the settled state, the voltages are all constant, they can be considered as AC grounds. Therefore the total capacitive impedance can be modelled as a capacitive load.



Modes of Operation of MOS

Operation Mode	Type	Condition	Equation
Cut-Off	NMOS	$V_{GS} < V_{TH}$	$I_D = 0$
	PMOS	$ V_{GS} < V_{TH} $	$I_D = 0$
Linear	NMOS	$V_{GS} \geq V_{TH}$ $V_{DS} \leq V_{GS} - V_{TH}$	$I_D = K_n(2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2)$
	PMOS	$ V_{GS} \geq V_{TH} $ $ V_{DS} \leq V_{GS} - V_{TH} $	$I_D = K_p(2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2)$
Saturation	NMOS	$V_{GS} \geq V_{TH}$ $V_{DS} \geq V_{GS} - V_{TH}$	$I_D = K_n(V_{GS} - V_{TH})^2(1 + \lambda V_{DS})$
	PMOS	$ V_{GS} \geq V_{TH} $ $ V_{DS} \geq V_{GS} - V_{TH} $	$I_D = K_p(V_{GS} - V_{TH})^2(1 - \lambda V_{DS})$

$$I_D = K_p(V_{GS} - |V_{TH}|)^2(1 + \lambda V_{DS})$$

Case 1: $0 \leq V_{ilp} < V_{Th}$

$$M_n : V_{asn} = V_{ilp}$$

$$V_{ilp} \leq V_{Th} \rightarrow M_n \text{ is in cutoff}$$

$$M_p : |V_{asp}| = |V_{ilp} - V_{DD}| = V_{DD} - V_{ilp} \quad (V_{ilp} < V_{DD})$$

$$V_{DD} - V_{ilp} \geq |V_{Tp}| \quad [\text{Assuming } V_{Th} \approx |V_{Tp}|] \quad \text{--- (1)}$$

$$\Rightarrow |V_{asp}| \geq |V_{Tp}|$$

$$|V_{asp}| \approx |V_{DD} - V_{DD}| = 0$$

$$|V_{asp}| - |V_{Tp}| = V_{DD} - V_{ilp} - |V_{Tp}| > 0 \quad [\text{Assuming } V_{DD} > 2|V_{Tp}|]$$

$$\Rightarrow |V_{asp}| \leq |V_{asp}| - |V_{Tp}| \rightarrow M_p \text{ is in linear mode}$$

Case 2: $V_{Th} \leq V_{ilp} < V_{DD}/2$ $\rightarrow V_{ilp} < V_{DD}$ [Take $V_{ilp} \approx V_{ilp}$]

$$M_p : |V_{asp}| = |V_{ilp} - V_{DD}| = V_{DD} - V_{ilp}$$

$$V_{DD} - V_{ilp} \geq |V_{Tp}| \quad [\text{By Assn. (1)}]$$

$$V_{DS} = V_{ilp} - V_{DD} < 0 \quad [V_{ilp} < V_{DD}]$$

$$\Rightarrow |V_{DS}| \approx 0 \Rightarrow |V_{DS}| < |V_{asp}| - |V_{Tp}| \quad \xrightarrow{\text{Mp is linear}}$$

$$M_n : V_{asn} = V_{tp}$$

$$V_{tp} \geq V_{Tn}$$

$$V_{bsn} \approx V_{DD} \Rightarrow V_{bsn} \geq V_{asn} - V_{Tn} \rightarrow M_n \text{ is in Saturation}$$

$$\text{Case 3: } V_{in} = V_{DD}/2 \rightarrow V_{tp} \approx V_{DD}/2$$

$$M_n : V_{asn} = \frac{V_{DD}}{2} \geq V_{Tn} \quad [\text{Assn ②}]$$

$$V_{bsn} = \frac{V_{DD}}{2}$$

$$\frac{V_{DD}}{2} \geq \frac{V_{DD}}{2} - V_{Tn} \rightarrow M_n \text{ is in Saturation}$$

$$M_p : |V_{asp}| = \left| \frac{V_{DD}}{2} - V_{DD} \right| = \frac{V_{DD}}{2} > V_{tp}$$

$$|V_{asp}| = \left| \frac{V_{DD}}{2} - V_{DD} \right| = \frac{V_{DD}}{2}$$

$$\frac{V_{DD}}{2} > \frac{V_{DD}}{2} - |V_{tp}| \Rightarrow |V_{asp}| \geq |V_{asp}| - |V_{tp}| \rightarrow M_p \text{ is in Saturation}$$


III proof can be stated for $V_{DD}/2 < V_{tp} < V_{DD} - |V_{tp}|$ and $V_{DD} - |V_{tp}| < V_{tp}$.

Once the voltages are settled

\therefore The VTC of the CMOS Inverter can be summarized as,

Condition	M _p	M _n	O/p
$0 \leq V_{in} \leq V_{Tn}$	Lin	OFF	V_{DD}
$V_{Tn} \leq V_{in} < \frac{V_{DD}}{2}$	Lin	Sat	$< V_{DD}$
$V_{in} = \frac{V_{DD}}{2}$	Sat	Sat	$\frac{V_{DD}}{2}$
$\frac{V_{DD}}{2} < V_{in} < V_{DD} - V_{tp} $	Sat	Lin	$< \frac{V_{DD}}{2}$
$V_{DD} - V_{tp} < V_{in}$	OFF	Lin	0

This switching point is valid if $V_{in} = |V_{tp}|$

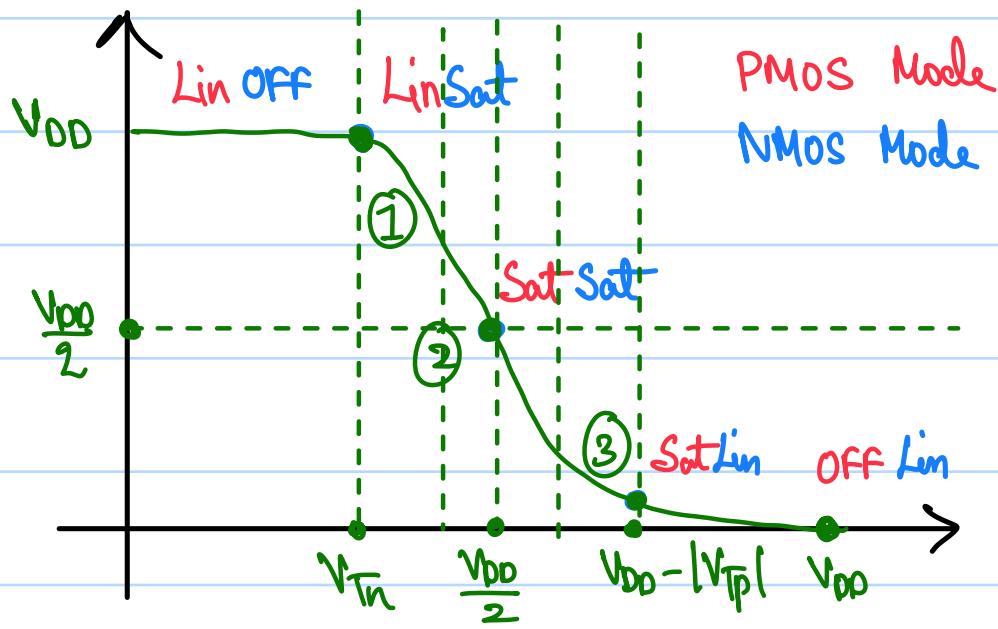

Note: By KCL, currents through both the MOSFETs will always be equal in the 3 intermediate points (LinSat SatSat SatLin)

At ① (LinSat)

$$I_{Dp\text{ Lin}} = I_{Dn\text{ Sat}}$$

$$= K_p \left[(V_{SD} - |V_{Tp}|) V_{SD} - \frac{V_{SD}^2}{2} \right] = \frac{1}{2} K_n (V_{DS} - V_{Tn})^2$$

$$= K_p \left[(V_{DD} - V_{in} - |V_{Tp}|)(V_{DD} - V_{Dp}) - \frac{(V_{DD} - V_{Dp})^2}{2} \right] = \frac{K_n}{2} (V_{Dp} - V_{Tn})^2$$

On Solving, we will get, (Take $V_{DD} - V_{Dp} = y$, $V_{Dp} - V_{Tn} = x$ easy)
and $K_n = K_p$

$$V_{Dp} = (V_{Dp} + |V_{Tp}|) \pm \sqrt{(V_{DD} - V_{Tn} - |V_{Tp}|)(V_{DD} - 2V_{Dp} + V_{Tn} - |V_{Tp}|)}$$

Since $V_{Dp} \approx V_{DD}$ near ①,

$$V_{Dp} = (V_{Dp} + |V_{Tp}|) + \sqrt{(V_{DD} - V_{Tn} - |V_{Tp}|)(V_{DD} - 2V_{Dp} + V_{Tn} - |V_{Tp}|)}$$

$$\text{Condition : } V_{DD} \geq V_{Tn} + |V_{Tp}|, V_{Dp} \leq \frac{V_{DD} + V_{Tn} - |V_{Tp}|}{2}$$


Therefore, the operating requirements of a CMOS inverter are:

$$V_{DD} \geq V_{Th} + |V_{Tp}| \quad 2) \quad V_{ilp} \leq \frac{V_{DD} + V_{Th} - |V_{Tp}|}{2} \approx \frac{V_{DD}}{2}$$

min. power supply

max. ilp voltage

||| by we can calculate for all the other points , by equating PMOS current and NMOS current .

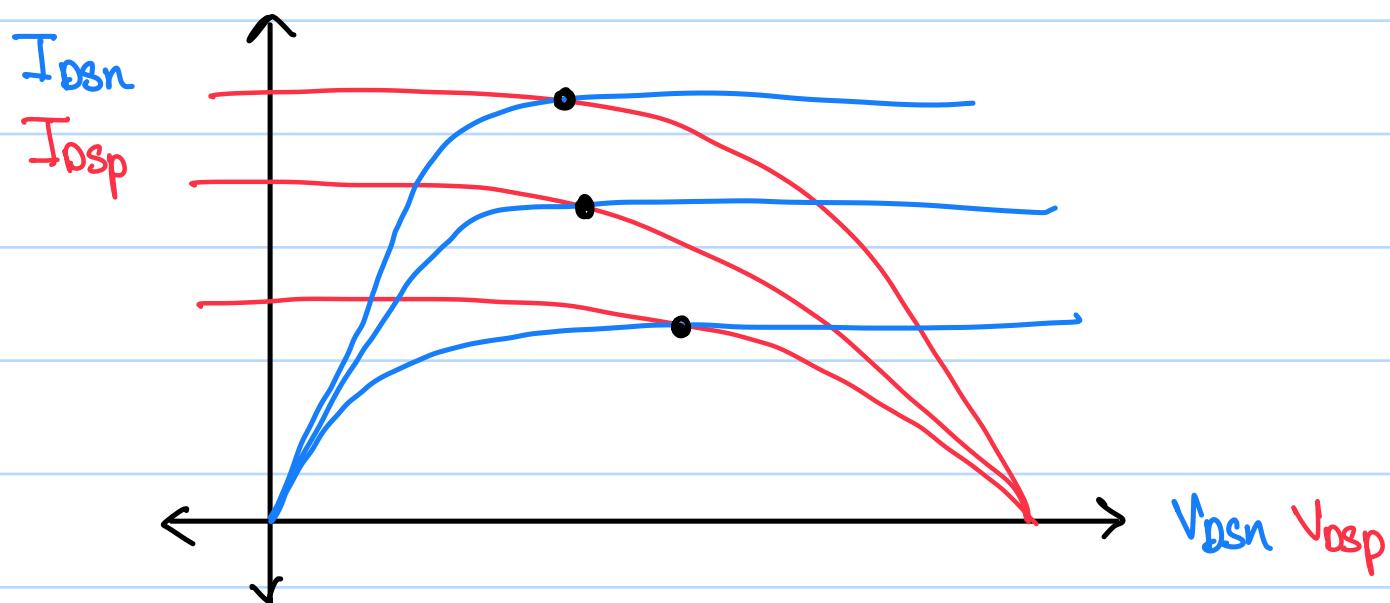

$V_{DD} \approx 1.8\text{ V}$ for 180 nm technology node.

At ② (Sat Sat),

$$\begin{aligned}
 I_{DSNsat} &= I_{DSPsat} \\
 &= K_n (V_{DSN} - V_{TRN})^2 = K_p (V_{SDP} - |V_{TRP}|^2)^2 \\
 &= K_n (V_{DIP} - V_{TRN})^2 = K_p (V_{DD} - V_{DIP} - |V_{TRP}|^2)^2
 \end{aligned}$$

$$\Rightarrow V_{ilp} = \frac{V_{DD} + \sqrt{B} V_{Thn} - |V_{Thpl}|}{1 + \sqrt{B}} \quad B = \frac{k_n}{k_p}$$

$$V_{DSN} \geq V_{ASN} - V_{THN}$$

$$\Rightarrow V_{Olp} \geq V_{ILP} - V_{THN}$$

$$V_{SDP} \geq V_{ASD} - |V_{THP}|$$


$$V_{DD} - V_{Olp} \geq V_{DD} - V_{ILP} - |V_{THP}|$$

$$\Rightarrow V_{Olp} \leq V_{ILP} + |V_{THP}|$$

$$\therefore V_{Olp} \in [V_{ILP} - V_{THP}, V_{ILP} + |V_{THP}|]$$

In this region, V_{Olp} vs V_{ILP} is approximately a straight line of very high slope. Therefore it shows amplifying action.

- Noise Margin :-

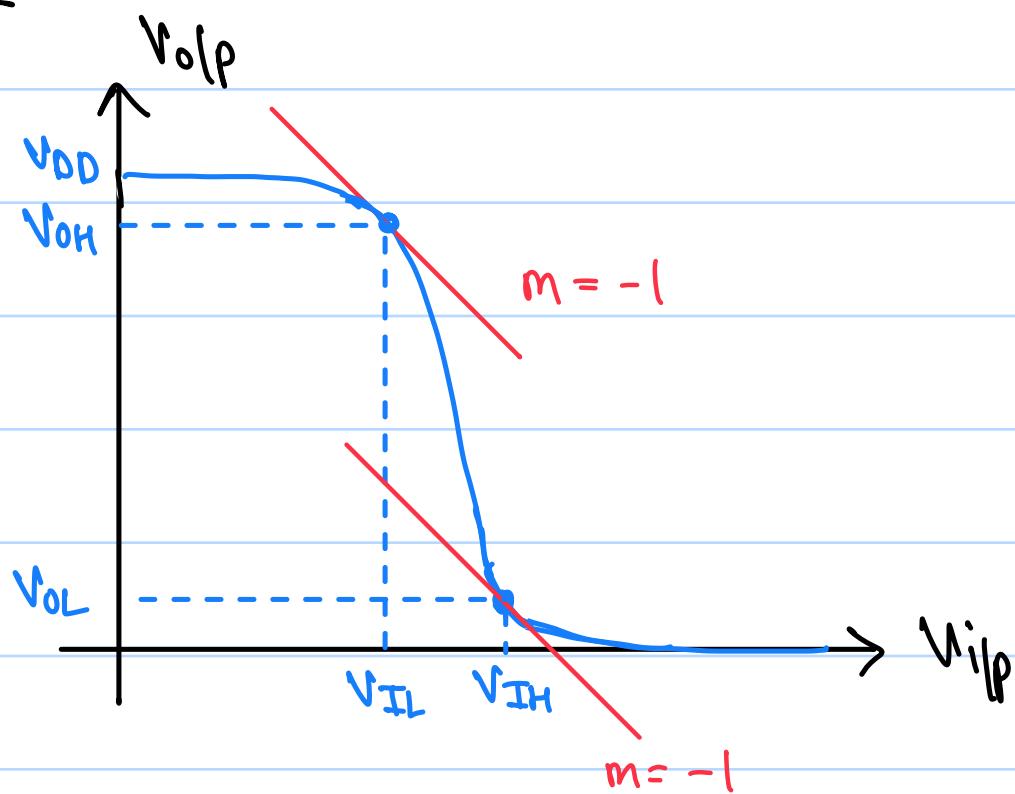

- To avoid the amplification behavior, we set

$$V_{out} \in [V_{OH}, V_{OD}] \longrightarrow \text{Logic 1}$$

$$V_{out} \in [0, V_{OL}] \longrightarrow \text{Logic 0}$$

$\Rightarrow V_{OH}$ = Minimum o/p for o/p logic 1


V_{OL} = Maximum o/p for o/p logic 0

V_{IH} = Minimum i/p for o/p logic 0

V_{IL} = Minimum i/p for o/p logic 1

- If $V_{i/p} \in (V_{IL}, V_{IH})$, the Inverter acts like an amplifier, which is unwanted since it **amplifies noise as well, creating undefined behavior.**

- If we have 2 inverters in series as,

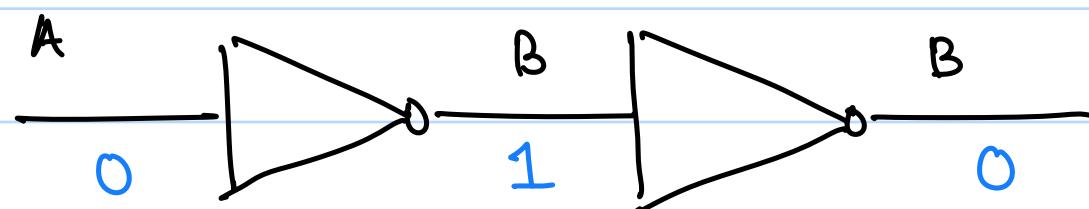

$$V_A \in [0, V_{IL}] \quad V_B \in [V_{OH}, V_{OD}] \quad V_C \in [0, V_{OL}]$$

$$[V_{OH}, V_{OD}] \subseteq [V_{IH}, V_{OD}]$$

- From the VTC, we can say that $V_{OH} > V_{IH}$ and $V_{OL} < V_{IL}$. So, we define the noise margin of our inverter as,

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

- But since $V_{IH} < V_{OH}$, even if $V_B < V_{OH}$, as long as $V_B > V_{IH}$ the inverter C will output 0. Hence the noise margin NM_H . Only for V_B low, we have NM_L .

- Also if the 2 inverters are not the same, then it must be ensured that,

$$V_{OH1} > V_{IH2}$$

- The parameter extraction of V_{OH} , V_{OL} , V_{IH} , V_{IL} , can be done as follows,

For point (V_{IL}, V_{OH}) , Inv. is in region of LinSat

For point (V_{IH}, V_{OL}) , Inv. is in region of SatLin

We know the current equation at both these regions (or atleast how to derive them). The required points will have $\frac{dV_{Op}}{dV_{Ip}} = -1$

We will get,

$$V_{IL} = \frac{3V_{DD} + 5V_{Tn} - 8|V_{Tp}|}{8}$$

$$V_{OH} = \frac{7V_{DD} + V_{Tn} + |V_{Tp}|}{8}$$

$$V_{IH} = \frac{5V_{DD} + 3V_{Tn} - 5|V_{Tp}|}{8}$$

$$V_{OL} = \frac{V_{DD} - V_{Tn} + |V_{Tp}|}{8}$$

Assume

$$K_n = K_p$$

$$(or) \beta = 1$$

$$\Rightarrow NM_H = \frac{V_{DD} - V_{Th} + 3|V_{Tp}|}{4}$$

$$NM_L = \frac{V_{DD} + 3V_{Th} - |V_{Tp}|}{4}$$

if $V_{Th} = |V_{Tp}| = V_T$




- From the NM_H/L equations we can see that increasing V_{DD} and V_{Th} will give us better noise margin.

Trade-offs :


- $V_{DD} \uparrow$ increases power consumption
- $V_T \uparrow$ increases min. V_{PD} , lower current causing delays and lower speed.

Higher current charge the capacitances faster, reducing delay / increasing bandwidth

Dynamic Characteristics :-

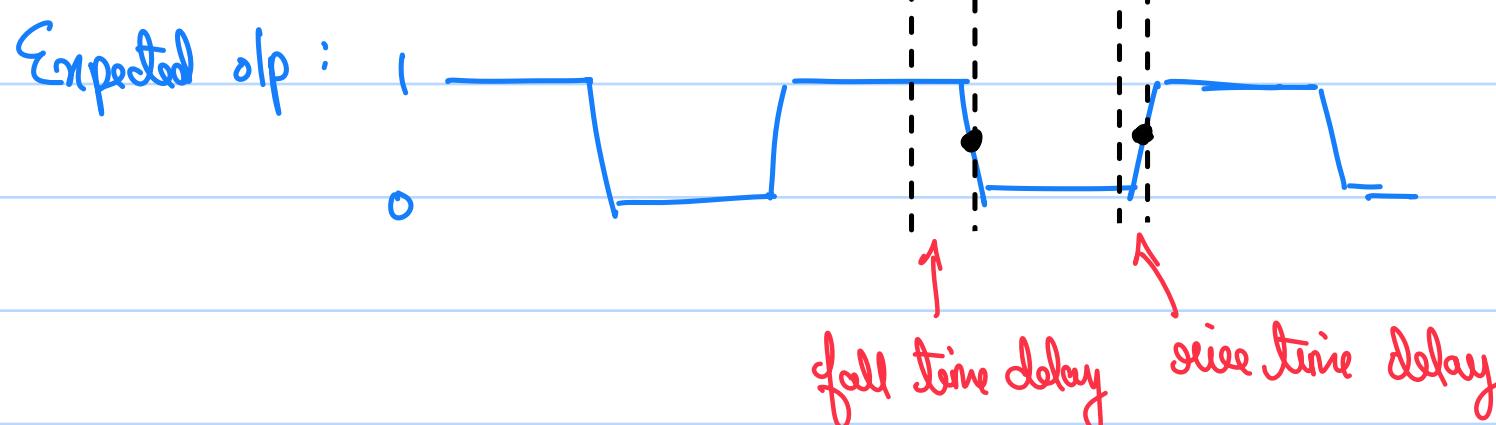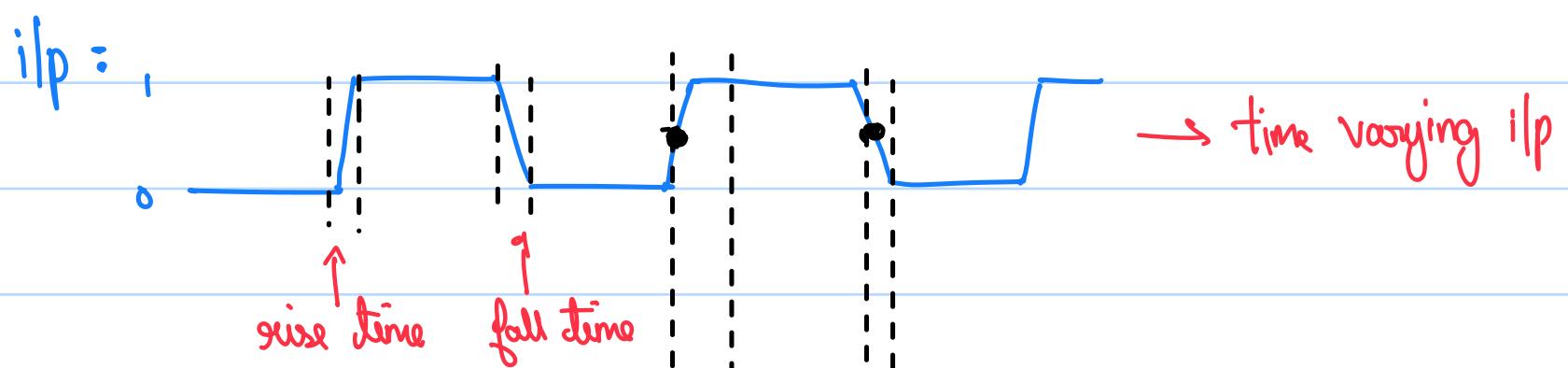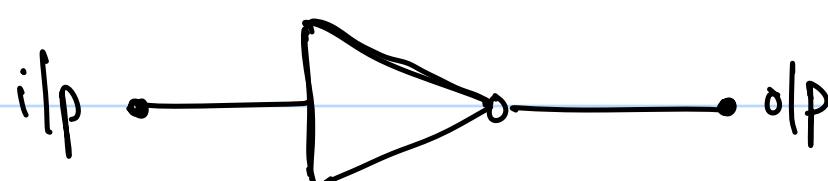

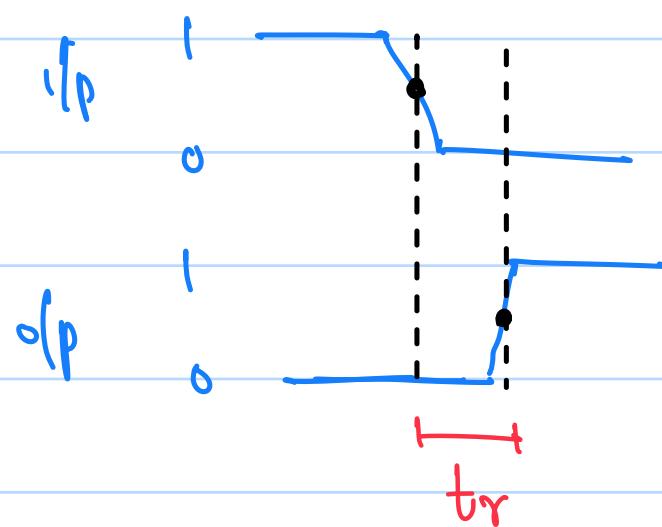
- The delay between the i/p and its respective o/p is due to the internal capacitances of the device and is unavoidable.
- Ideally, we want fall time delay and rise time delay to be the same, to get symmetric behavior.
- We assume that one of the MOSFETs is ON and the other is OFF always, to develop an intuition for the system.
- Rise Time Delay :-




Assumptions:

$$V_{i/p} = V_{IL}$$

$V_{o/p}$ = Grows from 0 to V_{OH} .

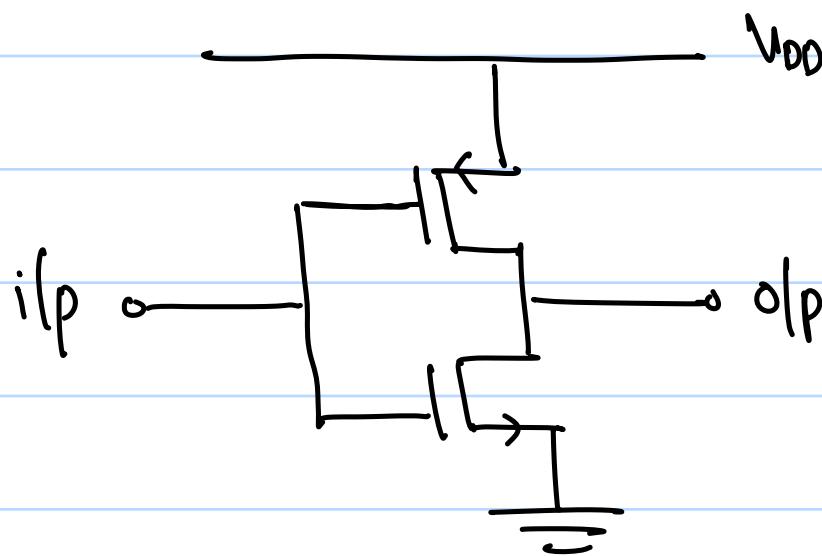

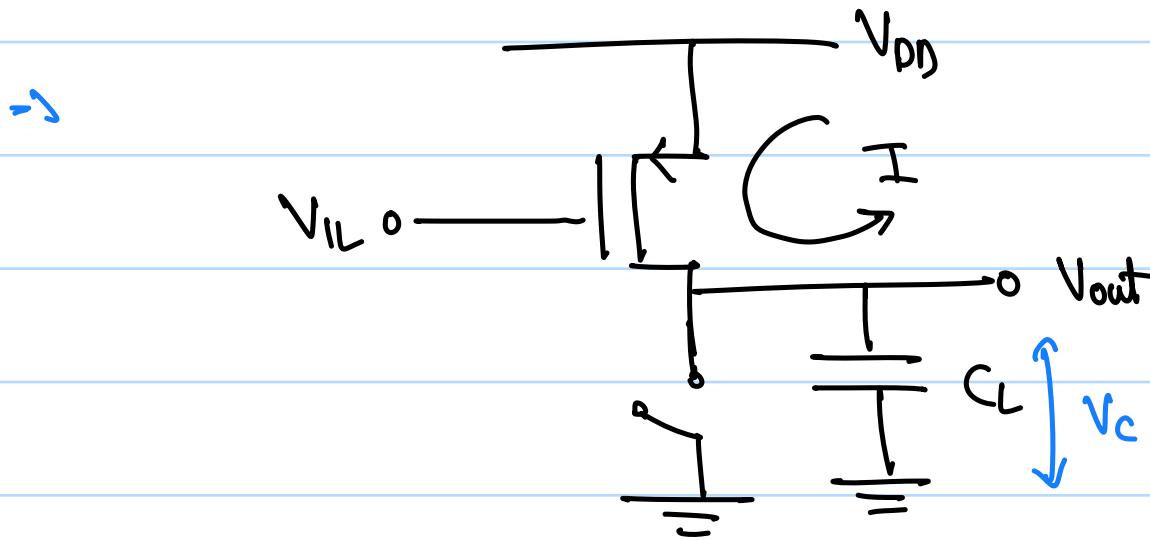~ In rise time, NMOS is OFF and PMOS is ON



$$I = I_{SD}, \Rightarrow I_{SD} = C \frac{dV_c}{dt}$$

$$\Rightarrow dt = \frac{C dV_c}{I_{SD}}$$

$$\Rightarrow t_r = \int_0^{V_{on}} \frac{C dV_c}{I_{SD}}$$

The mode of operation of the MOSFET,

$$V_{SDp} = V_{DD} - V_c$$

$$V_{on} = V_{SDp} - |V_{Tp}| = V_{DD} - V_{IL} - |V_{Tp}|$$

For linear,

$$V_{SDp} < V_{on}$$

$$\Rightarrow V_{DD} - V_c < V_{DD} - V_{IL} - |V_{Tp}|$$

$$\Rightarrow V_c > V_{IL} + |V_{Tp}|$$

\therefore For $V_c \in [0, V_{IL} + |V_{Tp}|]$, PMOS is in Saturation mode

For $V_c \in [V_{IL} + |V_{Tp}|, V_{on}]$, PMOS is in Linear mode

$$\rightarrow t_r = \int_0^{V_{IL} + |V_{Tp}|} \frac{dV_c}{I_{SO\text{ sat}}} + \int_0^{V_{IL} + |V_{Tp}|} \frac{dV_c}{I_{SO\text{ lin}}}$$

↑ constant current changing ↑ RC charging

$$I_{SPP} = \begin{cases} \frac{1}{2} K_p (V_{SDP} - |V_{Tp}|)^2, & \text{saturation} \\ K_p (V_{SDP} - |V_{Tp}|) V_{SDP} - \frac{V_{SDP}^2}{2}, & \text{linear} \end{cases}$$

Where,

$$V_{SDP} = V_{DD} - V_{IL}, \quad V_{SDP} = V_{DD} - V_C$$

On solving, we will get,

$$t_r = \frac{\alpha C [V_{IL} + |V_{Tp}|]}{K_p [V_{DD} - V_{IL} - |V_{Tp}|]^2} + \frac{C}{K_p [V_{DD} - V_{IL} - |V_{Tp}|]} \ln \left(\frac{V_{DD} + V_{OH} - 2V_{IL} - 2|V_{Tp}|}{V_{DD} - V_{OH}} \right)$$

↑ Constant current charging time ↓ RC charging time


↓ $\frac{1}{K_p (V_{DD} - V_{IL} - |V_{Tp}|)}$ is the apparent ON resistance of the circuit

~ We can see that t_r is dependent on the ON resistance of the circuit

~ Also, the voltage terms resemble the Noise margin parameters of the inverter, i.e., for given Noise margin parameter,

$$\frac{K_p t_r}{C} \approx \text{const}$$

- Fall Time Delay :-

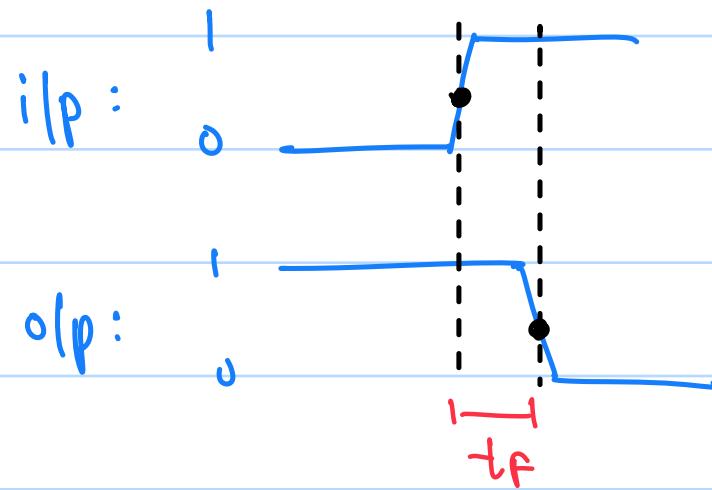


Assumptions :

$$V_{lp} = V_{IH}$$

V_{lp} = Falls from V_{DD} to V_{OL}

PMOS is OFF, NMOS is ON

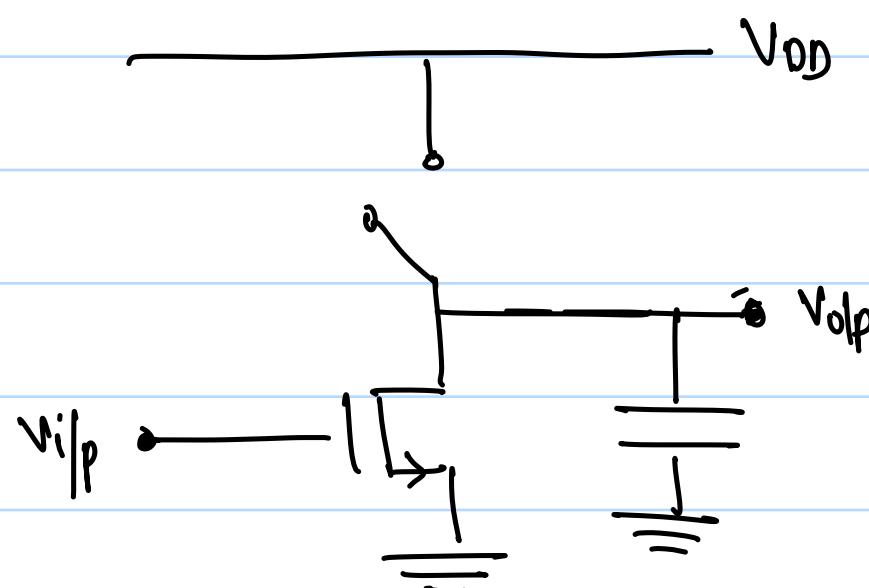

$$I_{DS} = -C \frac{dV_C}{dt} \Rightarrow dt = -\frac{C dV_C}{I}$$

$$\Rightarrow t_f = -C \int_{V_{LP}}^{V_{OL}} \frac{dV_C}{I} = C \int_{V_{OL}}^{V_{DD}} \frac{dV_C}{I}$$

$$\Rightarrow t_f = \int_{V_{DD}}^{V_{IH} - V_{TN}} \frac{dV_C}{I_{DSsat}} - \int_{V_{IH} - V_{TN}}^{V_{OL}} \frac{dV_C}{I_{DSlin}}$$

$$\Rightarrow \frac{K_{n\text{tf}}}{c} = \frac{2(V_{DD} - V_{IH} + V_{Th})}{(V_{IH} - V_{Th})^2} + \frac{1}{V_{IH} - V_{Th}} \ln \left(\frac{2(V_{IH} - V_{Th}) - V_{OL}}{V_{OL}} \right)$$

$$\Rightarrow \frac{K_{n\text{tf}}}{c} = \text{const for a given NM}$$

- Delay: -

The total delay of the inverter is given by,

$$\tau = \frac{t_r + t_f}{2}$$

$$\Rightarrow \tau \propto \frac{c}{k_p + k_n}$$

~ We know,

$$C_{IN} = C_{asn} + C_{asp} + C_{aon} + C_{aop}$$

$$\approx w_n L_n C_{oxn} + w_p L_p C_{oxp} + C_{ovn} + C_{ovp}$$

$$+ w_n C_{ovn} + w_p C_{ovp}$$

Since $K_{p/n} \propto W$, we can say $C_{IN} \propto K_p / n$

$$\Rightarrow \tau \propto \frac{C_L}{C_{IN}}$$

~ Also, $C_L = C_{ext} + C_{self}$


$$C_{self} = C_{DBn} + C_{DBp} + C_{aon} + C_{aop}$$

$$\Rightarrow C_{self} \propto K \Rightarrow C_{self} \propto C_{IN}$$


$$\Rightarrow T \propto \frac{C_{ext}}{C_{IN}} + \text{const}$$

~ Because of the constant in the equation, if we increase C_{IN} to a very large number, any further increase will be dominated by the constant.

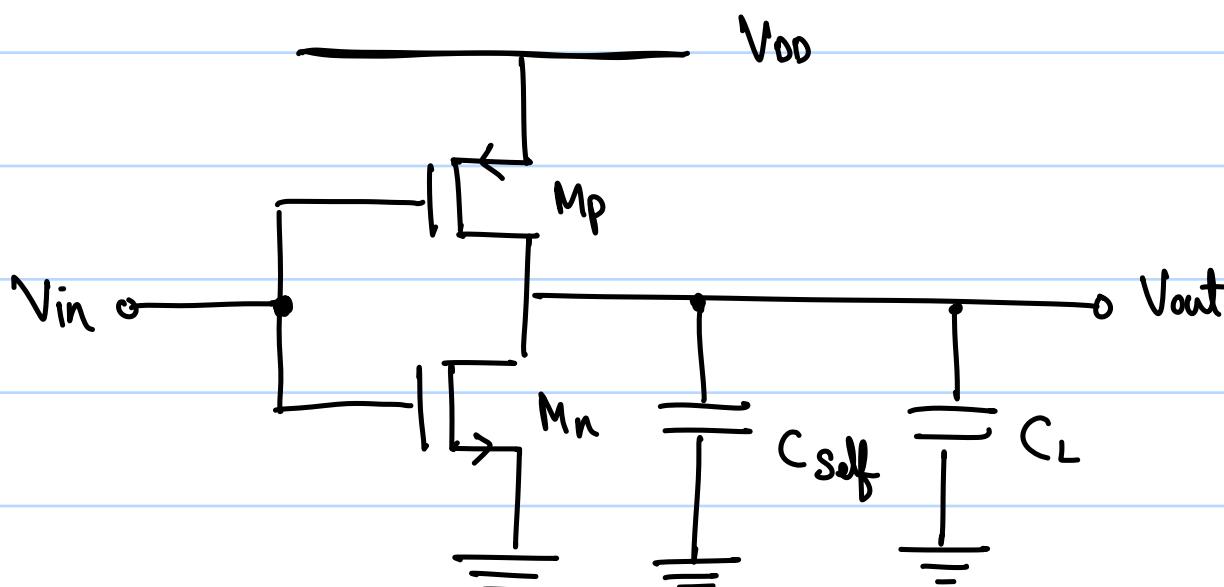~ Also, C_{IN} will act as C_{ext} for any logic circuit in the previous stage.



Note: Miller's effect,

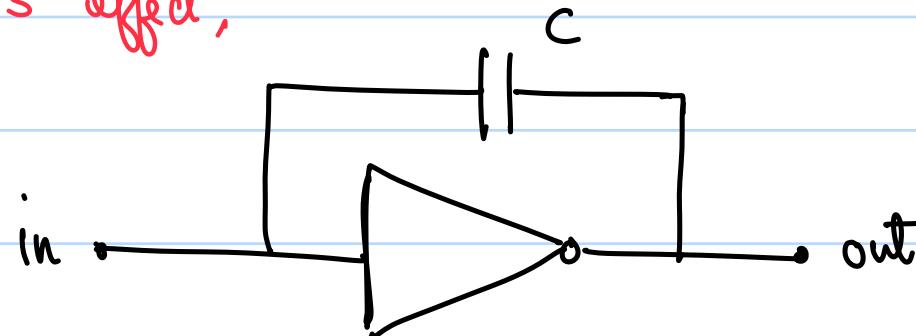

This is high for
inv. in the Ampl.

$$C_{out} = C(1 + A) \quad A - \text{Gain mode}$$

+ Any DC potential acts like a ground for AC responses in capacitances.

$$\sim C_{self} = C_{Aop} + C_{GDN} + C_{DBn} + C_{DB}$$


~ Define $\frac{C_{ext}}{C_{in}} = h$, since Delay = $\frac{C_{ext}}{C_{in}} + \text{const.}$

$$\Rightarrow \text{Delay} = (h + p)\tau \quad p - \text{Constant Term}$$

τ - Proprietary Const.


h - Electrical effort of the gate.

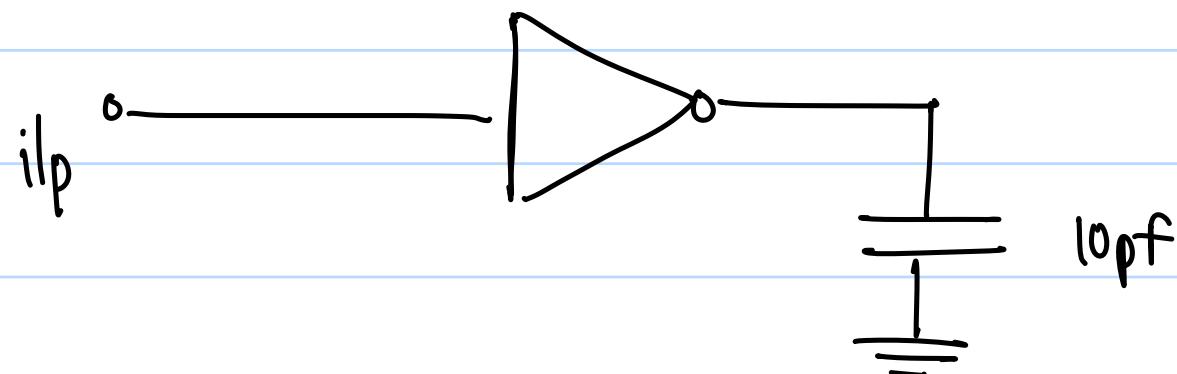~ If we have a big capacitor on the output side.



Since a huge driving current is required to quickly charge the capacitor, the width of the inverter must be high, which increases C_{IN} .

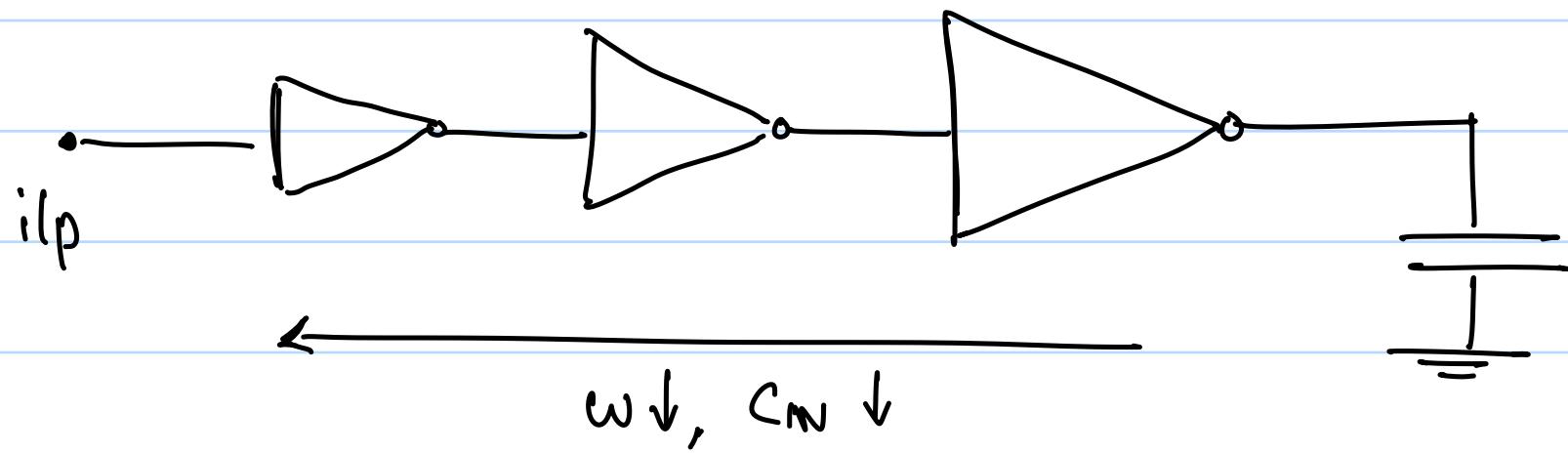If C_{IN} must be low, we can chain multiple inverters together.



Since $C_{IN} < C_{ext}$, smaller inverters are used to drive the

smaller i/p capacitance.

~ If $K_n = K_p$, then $\frac{W_p}{W_n} = \frac{M_n}{M_p} \Rightarrow W_p = \frac{M_n}{M_p} W_n$

If we say an inverter has width W , we usually mean the width W_n . W_p is calculated by $\frac{M_n}{M_p} W_n$. ($\approx 2W_n$)

~ Having such a chain of inverters will actually be faster than a single inverter, ie, the delay is lower.

Min. size transistor : $L = L_{min} = \text{Tech.node}$, $W = W_{min} > L_{min}$
 $0.18\mu\text{m}$, $0.27\mu\text{m}$ in 180nm TSMC.


If we directly use a min. size transistor, the delay will be extremely high. (low W). But C_{IN} will be good.

So, using a series of inverters with increasing widths will be faster, since the smaller transistors drive a smaller capacitance, leading to smaller delays.

This is termed as the buffer chain / tapered buffer design.

- Buffer Chain Design :

~ Simplified Model of an Inverter,

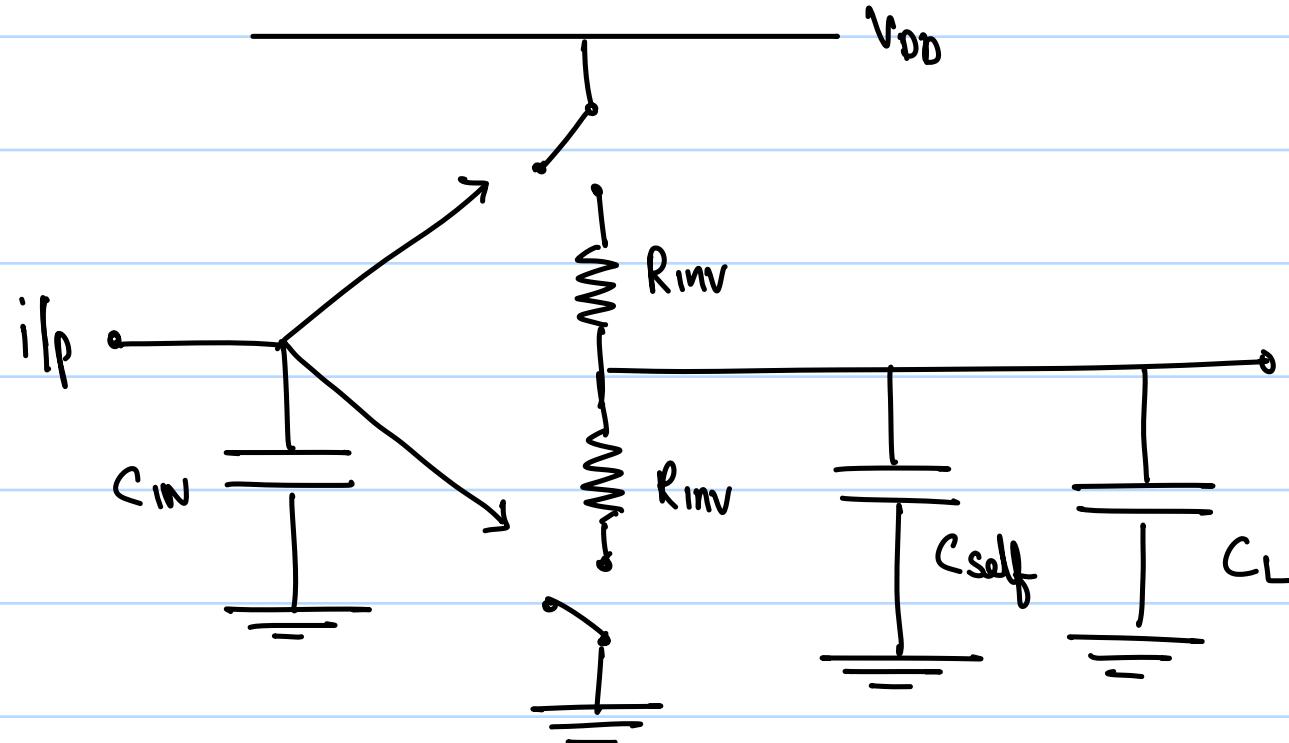

Case 1: If $\rho = 0$ (ie $C_{self} = 0$), then $T_1 = R_{inv} C_L$

Case 2: $T_2 = R_{inv} (C_{self} + C_L) \rightarrow$ General Case


$$\frac{T_2}{T_1} = \frac{C_{self} + C_L}{C_L} = 1 + \frac{C_{self}}{C_L}$$

In buffer chain, $C_L = i_ip$ capacitance of next inverter. (C_{in-inv})

$$\Rightarrow \frac{T_2}{T_1} = 1 + \frac{C_{self}}{C_{in-inv}}$$

$$\Rightarrow T_2 = \left(1 + \frac{C_{self}}{C_{in-inv}}\right) T_1$$

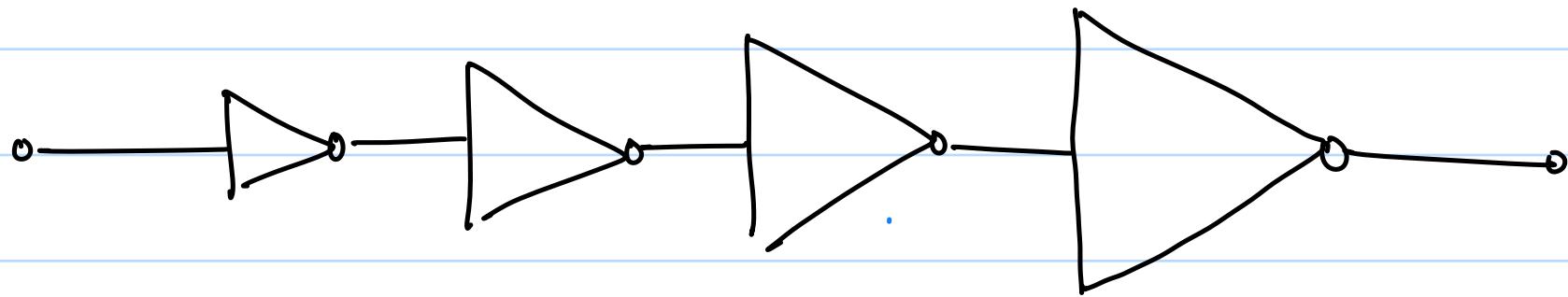So, given C_L and C_{in} limitations we can design a buffer chain for the lowest delay, through the following algorithm.




Total delay = \sum Delay in each inverter.

$$\text{Also, in } \tau_2 = \tau_1 \left(1 + \frac{C_{self}}{C_{in-inv}} \right)$$

Since $C_{self} \propto C_{in-inv}$, $\frac{C_{self}}{C_{in-inv}} = \text{const} = f$


$$\Rightarrow \tau_2 = \tau_1 (1 + p)$$

Case 1:

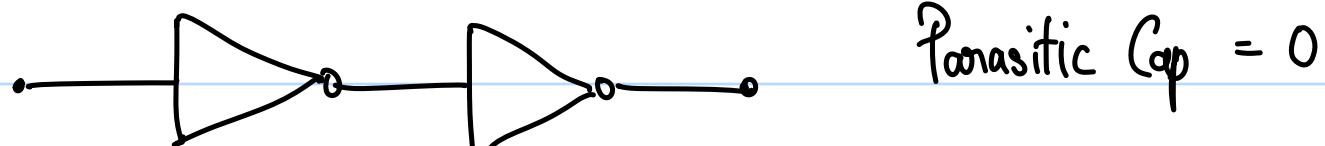

$$\tau = R_{inv} \cdot C_{in-inv}$$

Case 2:

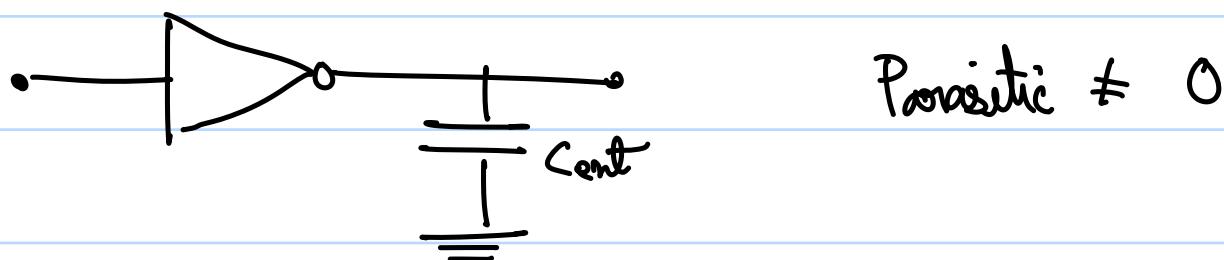


$$D = R_{inv} (C_{ext} + C_{self})$$

$$\frac{D}{\tau} = \frac{C_{out} + C_{self}}{C_{in-inv}}$$

$$\Rightarrow D = \tau \left(\frac{C_{out}}{C_{in-inv}} + p \right)$$

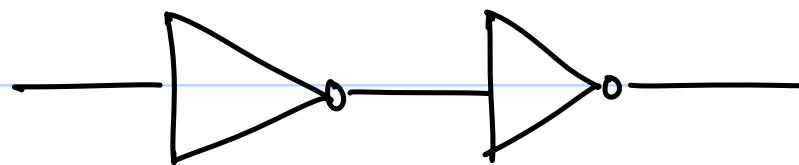
Using this formula, if the inverter is driving 1 other inverter,



$$C_{out} = C_{in-inv}$$


$$\Rightarrow D_1 = \tau(1+p)$$

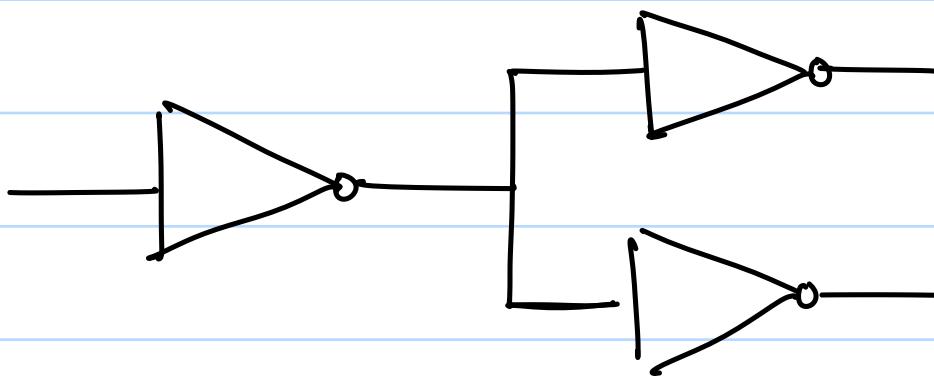If the inverter is driving 2 other inverters in parallel,




$$C_{out} = 2C_{in-inv}$$

$$\Rightarrow D_2 = \tau(2+p)$$

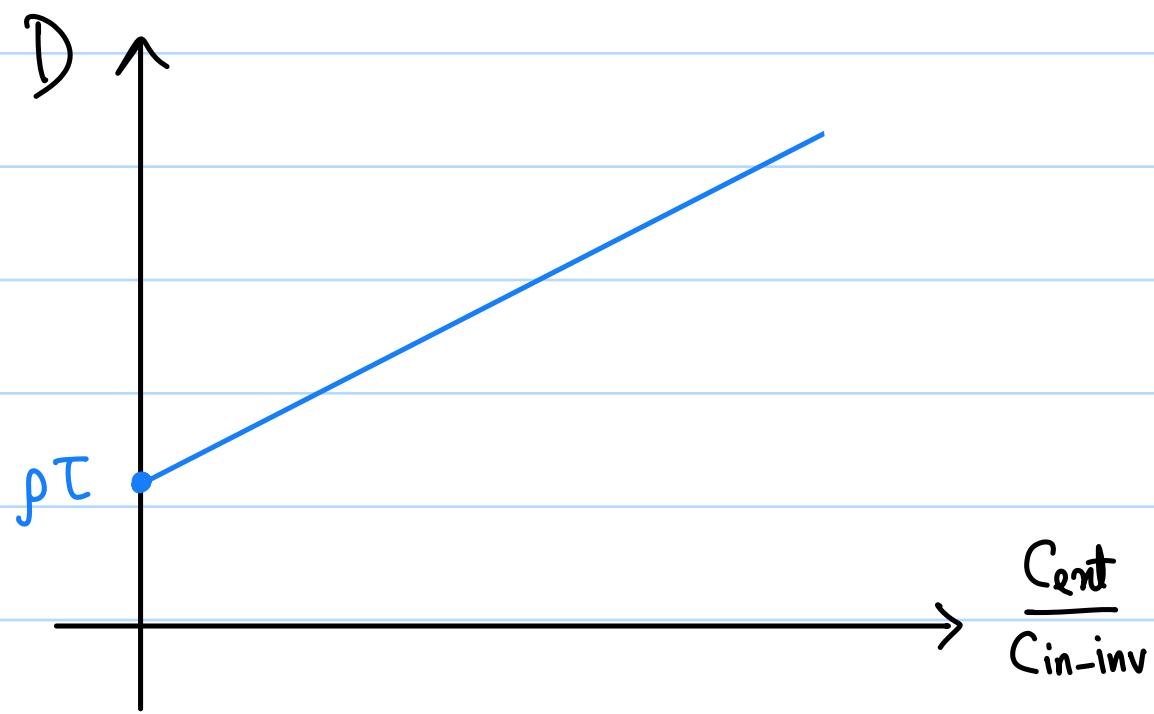

~ In an N -stage buffer chain,

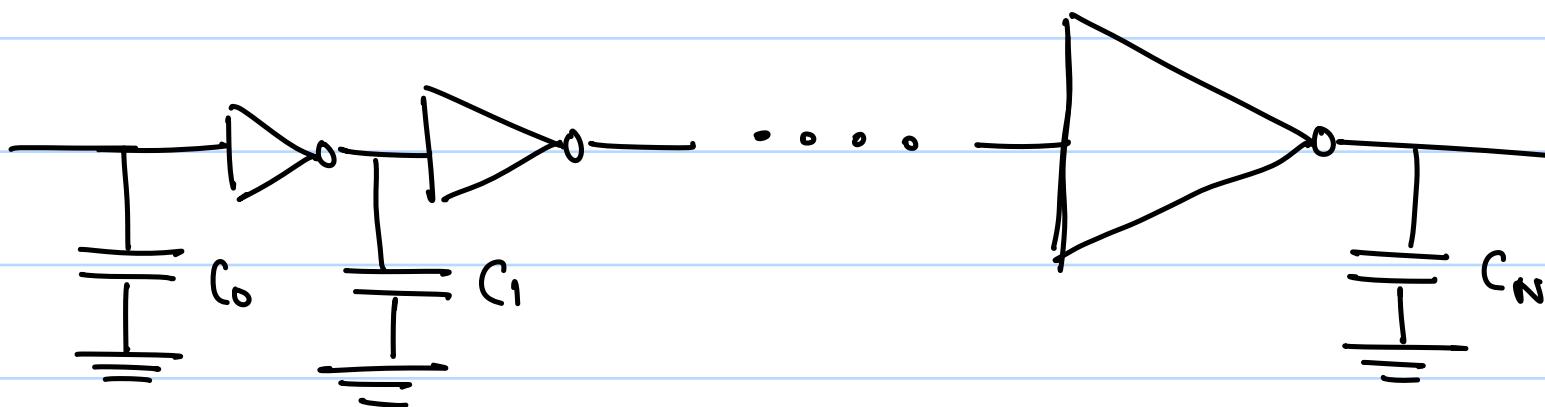

$$D = D_1 + D_2 + D_3 + \dots + D_N$$

$$= \left(\left(\frac{C_1}{C_0} + \rho \right) + \left(\frac{C_2}{C_1} + \rho \right) + \dots + \left(\frac{C_N}{C_{N-1}} + \rho \right) \right) \tau$$

$$\Rightarrow D = \tau \left(\sum_{i=1}^N \frac{C_i}{C_{i-1}} + N\rho \right)$$

$$\Rightarrow D = \tau \left(\sum_{i=1}^N h_i + N\rho \right) \quad h_i - \text{Electrical Effort} = \frac{C_{out}}{C_{in}}$$

~ To optimize delay,

$$1) h_1 = h_2 = h_3 = \dots = h_N$$

$$\frac{SD}{SC_i} = \frac{S}{SC_i} \left(\frac{c_i}{c_{i-1}} + \beta + \frac{c_{i+1}}{c_i} + \beta \right) = 0$$

$$= \frac{1}{c_{i-1}} + c_{i+1} \left(\frac{-1}{c_i^2} \right) = 0$$

$$= \frac{1}{c_{i-1}} = \frac{c_{i+1}}{c_i^2}$$

$$= c_i = \sqrt{c_{i+1} c_{i-1}} \longrightarrow \text{For Min. delay}$$

$$h_i = \frac{c_i}{c_{i-1}} = \sqrt{\frac{c_{i+1}}{c_{i-1}}}$$

$$\Rightarrow h_1 = h_2 = h_3 = h_4 = \dots = h_N$$

Overall electrical effect $H = \frac{C_{ext}}{C_{in}}$

$$\frac{C_N}{C_0} = \frac{c_1}{c_0} \times \frac{c_2}{c_1} \times \frac{c_3}{c_2} \times \dots$$

$$H = h_1 \times h_2 \times h_3 \times \dots$$

$$\Rightarrow h = H^{1/N}$$

$$D = \tau \left(\sum_{i=1}^N h_i + N_p \right)$$

$$= N \tau (h + \beta)$$

$$\Rightarrow D = N \tau (h^{1/N} + \beta)$$

$$\text{Take } x = H^{1/N}, \Rightarrow \ln x = \frac{1}{N} \ln H$$

$$D(x) = \tau N(x + \rho)$$

$$\Rightarrow D(x) = \tau \frac{\ln H}{\ln x} (x + \rho)$$

$$D'(x) = \tau \frac{\ln H}{\ln x} \left[\frac{x \ln x - (x + \rho)}{x \ln x} \right] = 0$$

$$\Rightarrow x \ln x - x = \rho$$

