

Bipolar Junction Transistor

3 Qs ????


❖ What is transistor action and how does it occur in a BJT?

❖ Is BJT two back-to-back diodes connected together?

❖ How does a BJT amplify?



Transistor

Trans-resistor

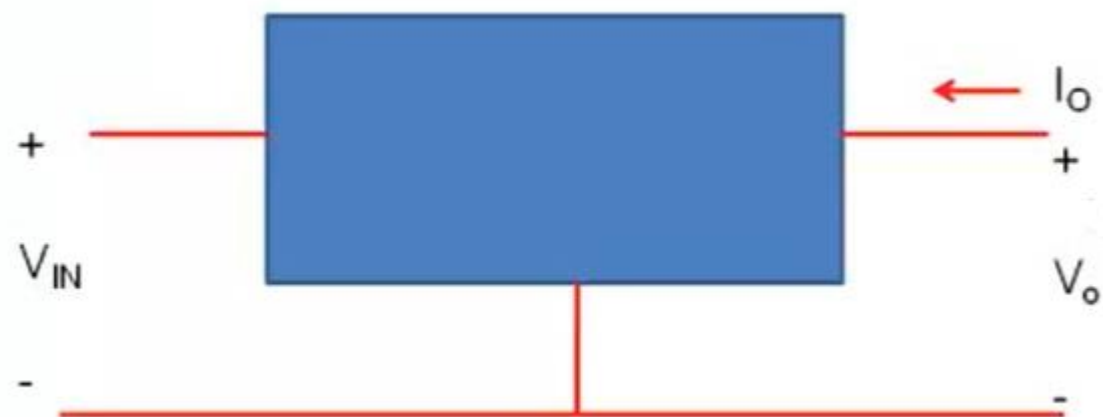


Current I_O is much more sensitive to V_{IN} than V_O

“Ideal Transistor”

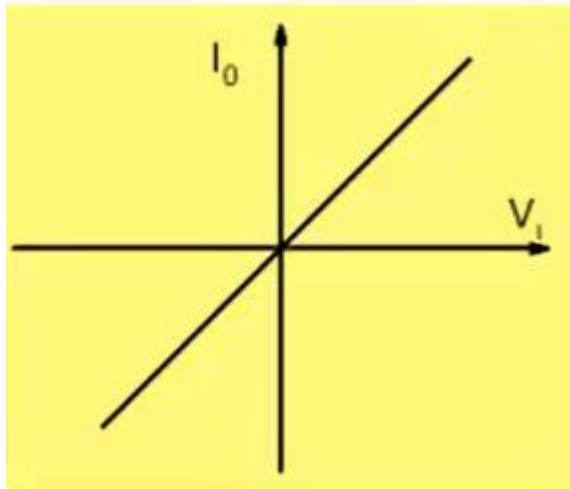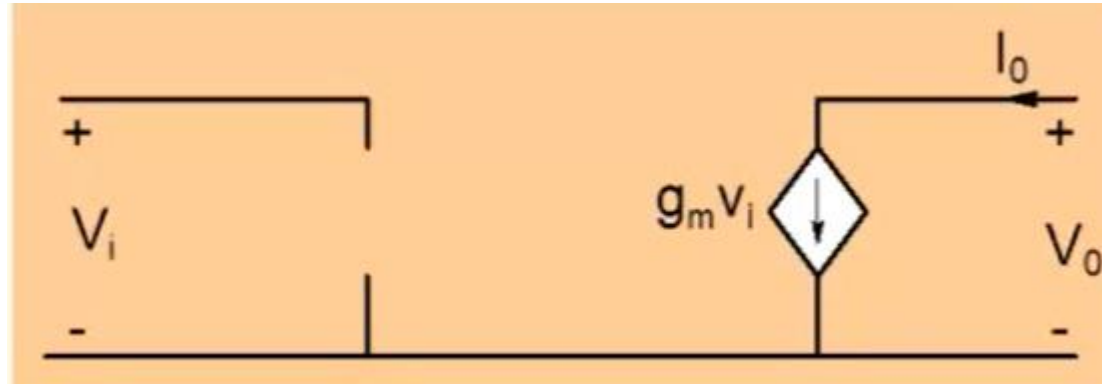



Transfer Characteristics

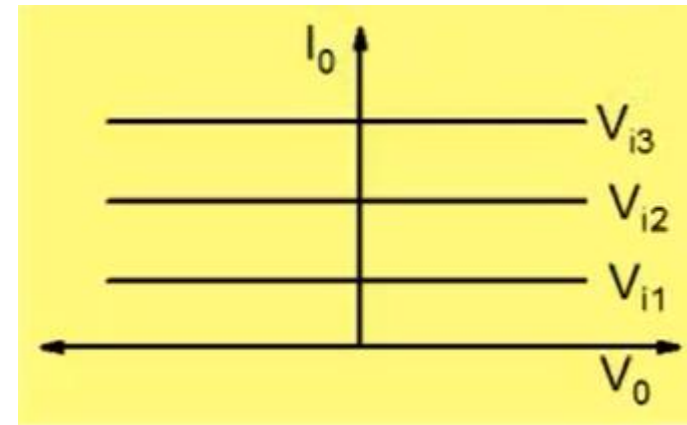

Output Characteristics

Voltage controlled Current Source (VCCS)

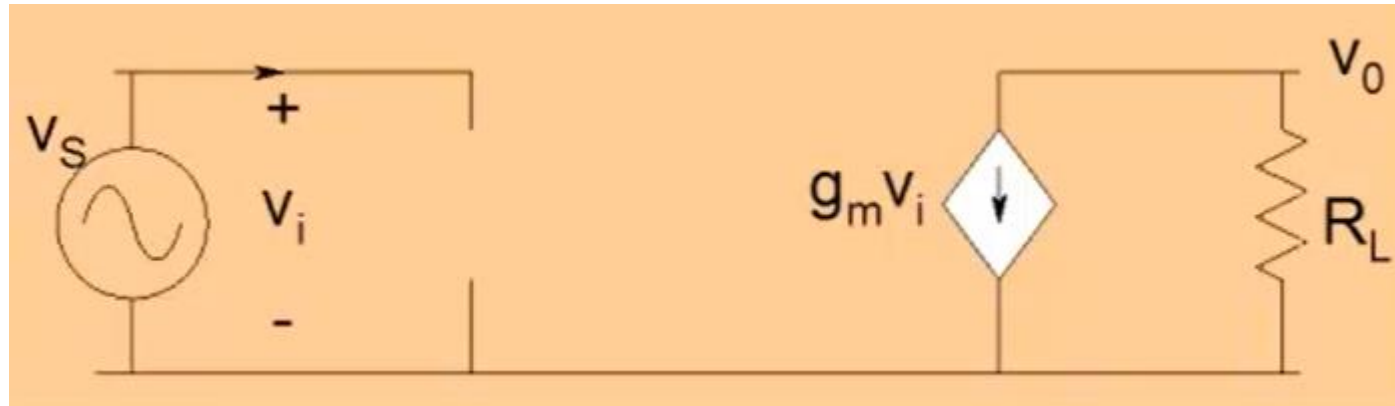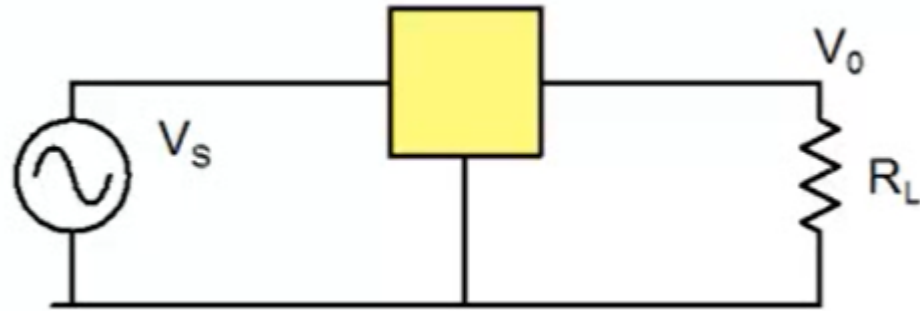
Transistors can be used for AMPLIFICATION




$$A_v = \frac{V_o}{V_s} = -g_m \times R_L$$

By choosing sufficiently larger load resistance, voltage gain can be obtained

Bipolar Junction Transistor (BJT)

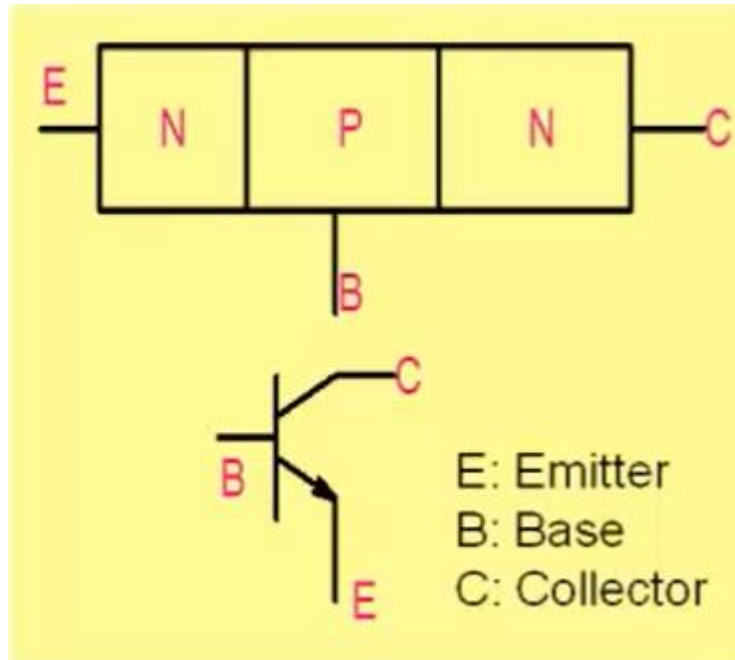


NPN

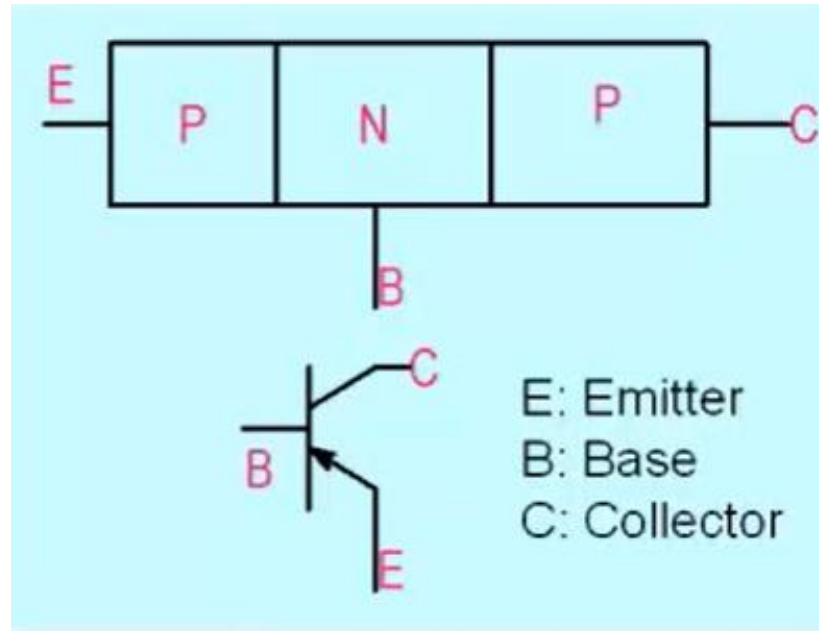


PNP


More Realistic View

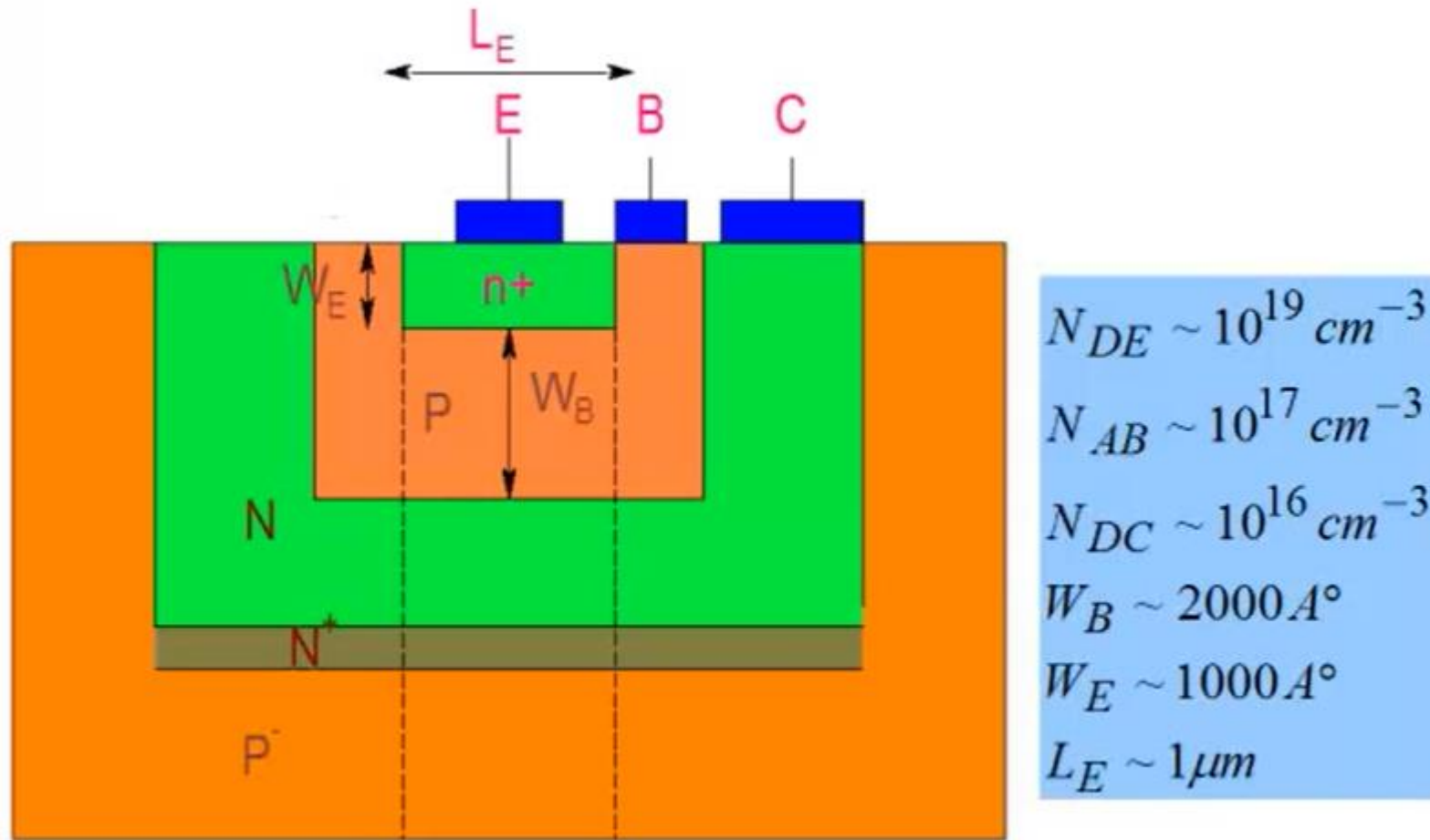

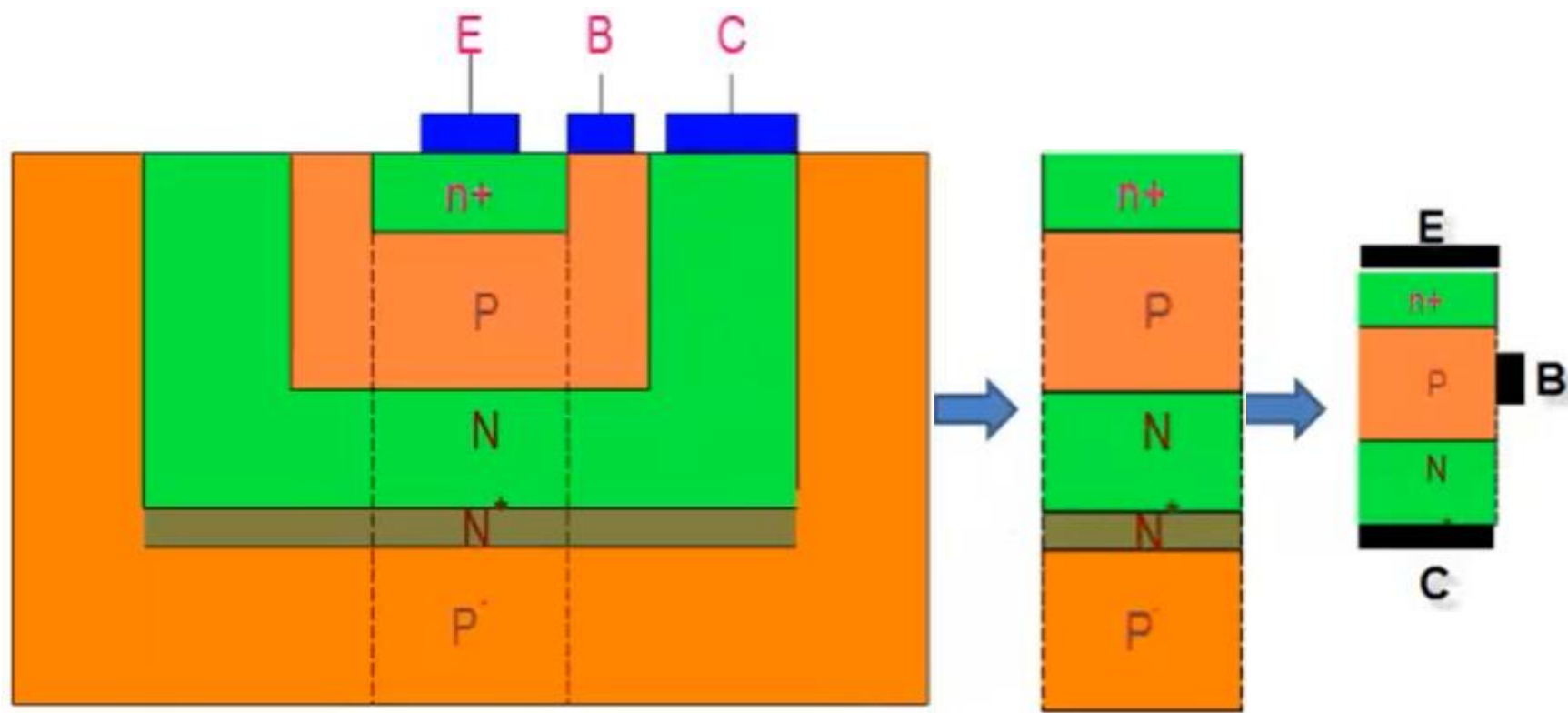
BJT is not symmetric: emitter and collector cannot be simply interchanged



Top View

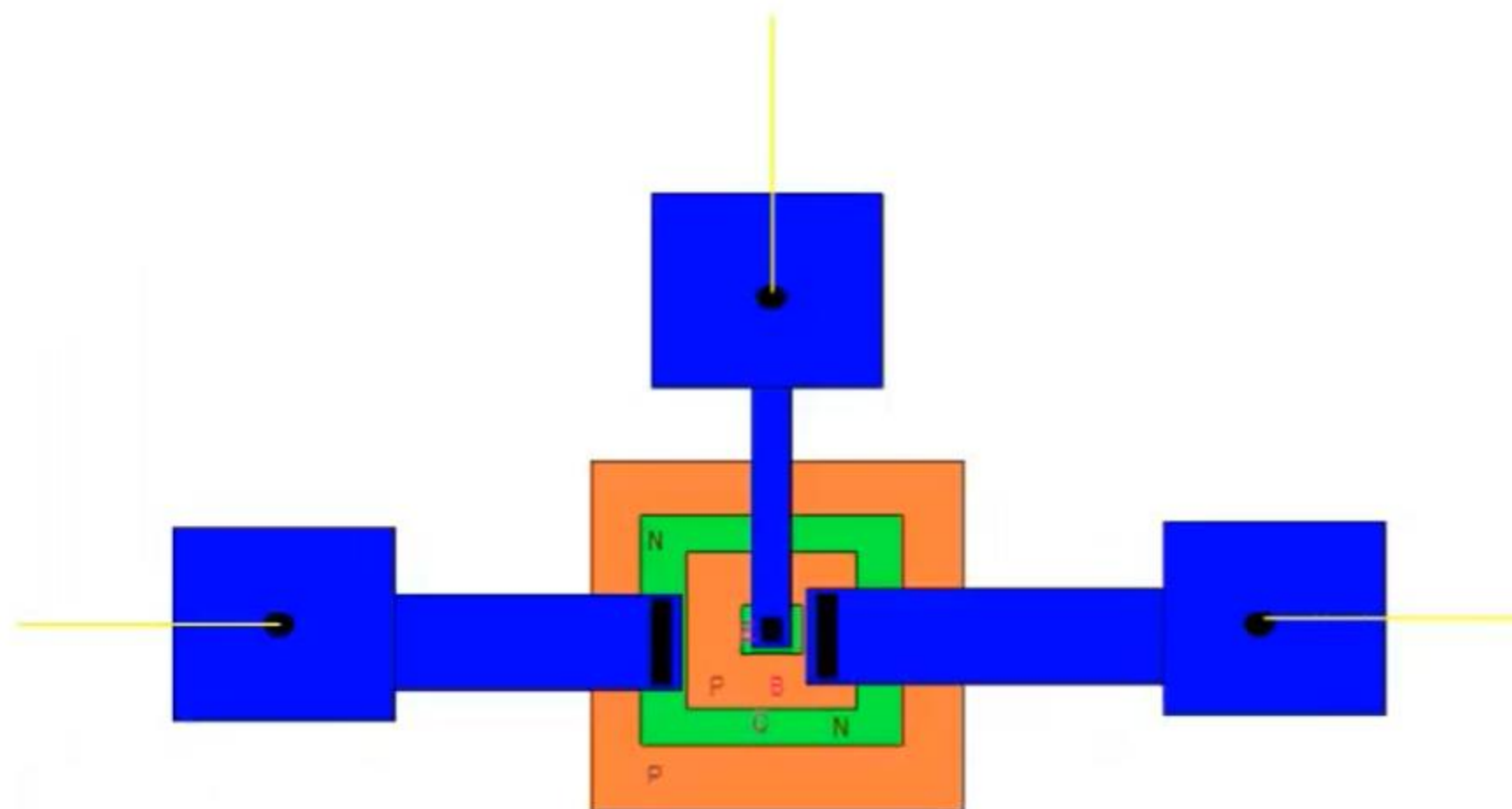

Background

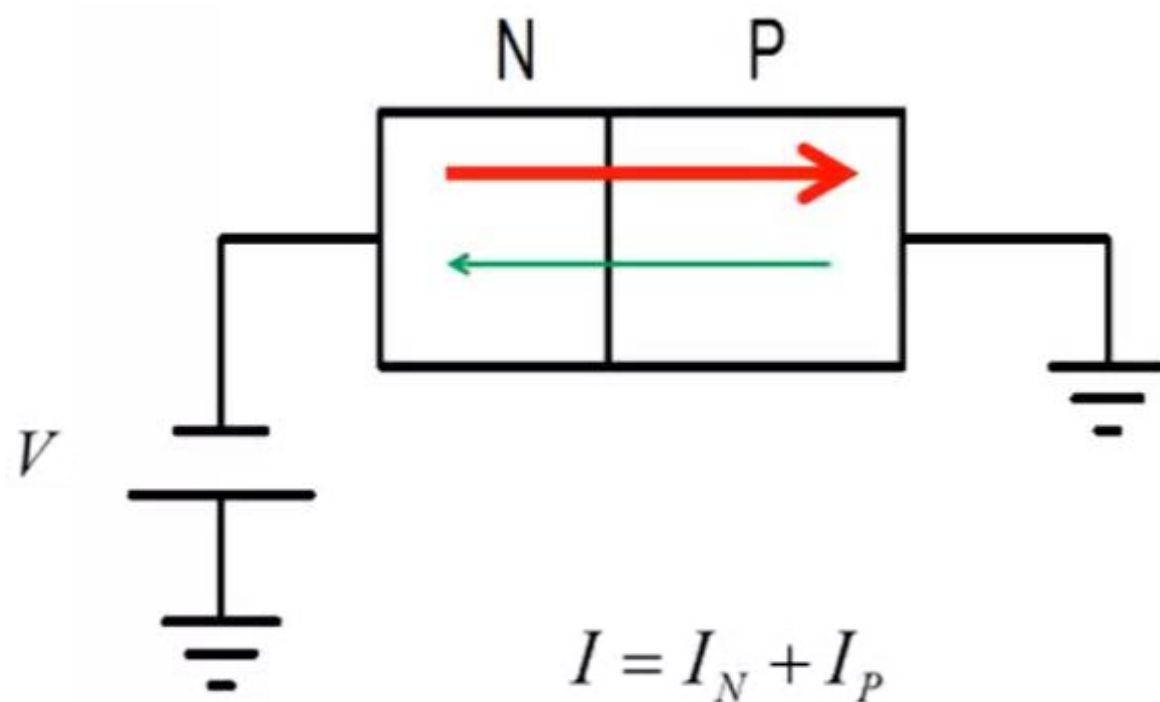


$$I = I_N + I_P$$

$$I_N; I_P \propto \exp\left(\frac{V}{V_T}\right)$$


If doping in N region is much larger than doping in p region
then $I_N \gg I_P$

Basic Transistor Operation

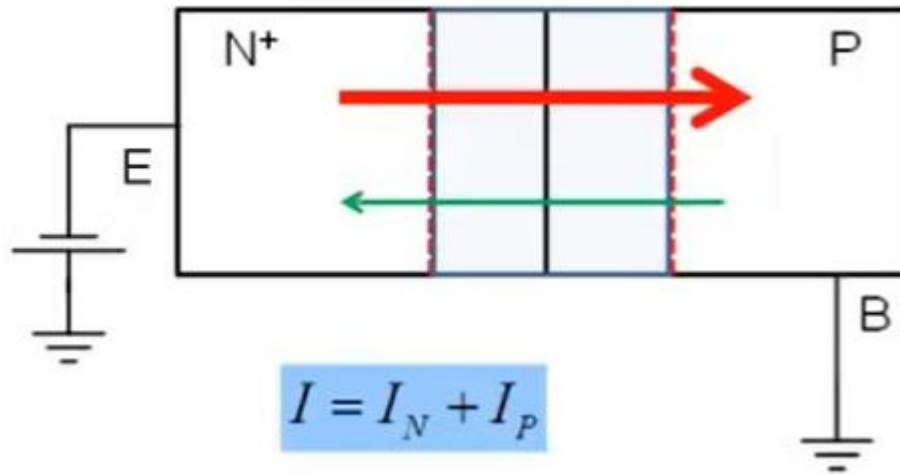

We will assume that doping in emitter is much more than base so that electron current is much larger than hole current


$$I_N \gg I_P$$

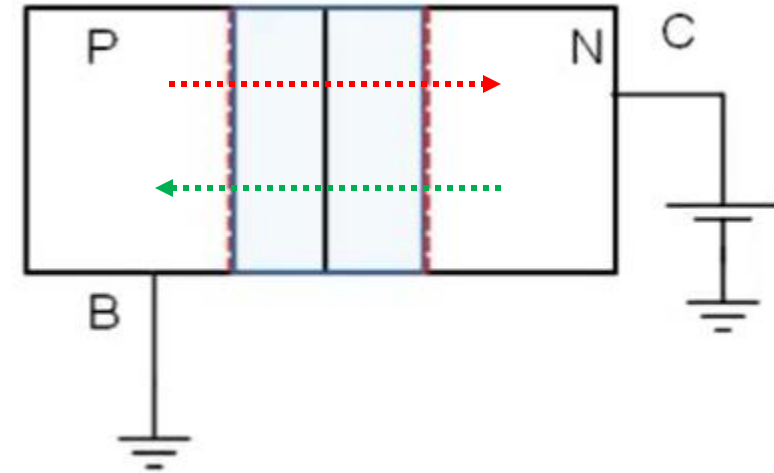


In the reverse biased junction current is small because there are very few electrons in P and holes in N-region

Basic Transistor Operation

$$I = I_N + I_P$$

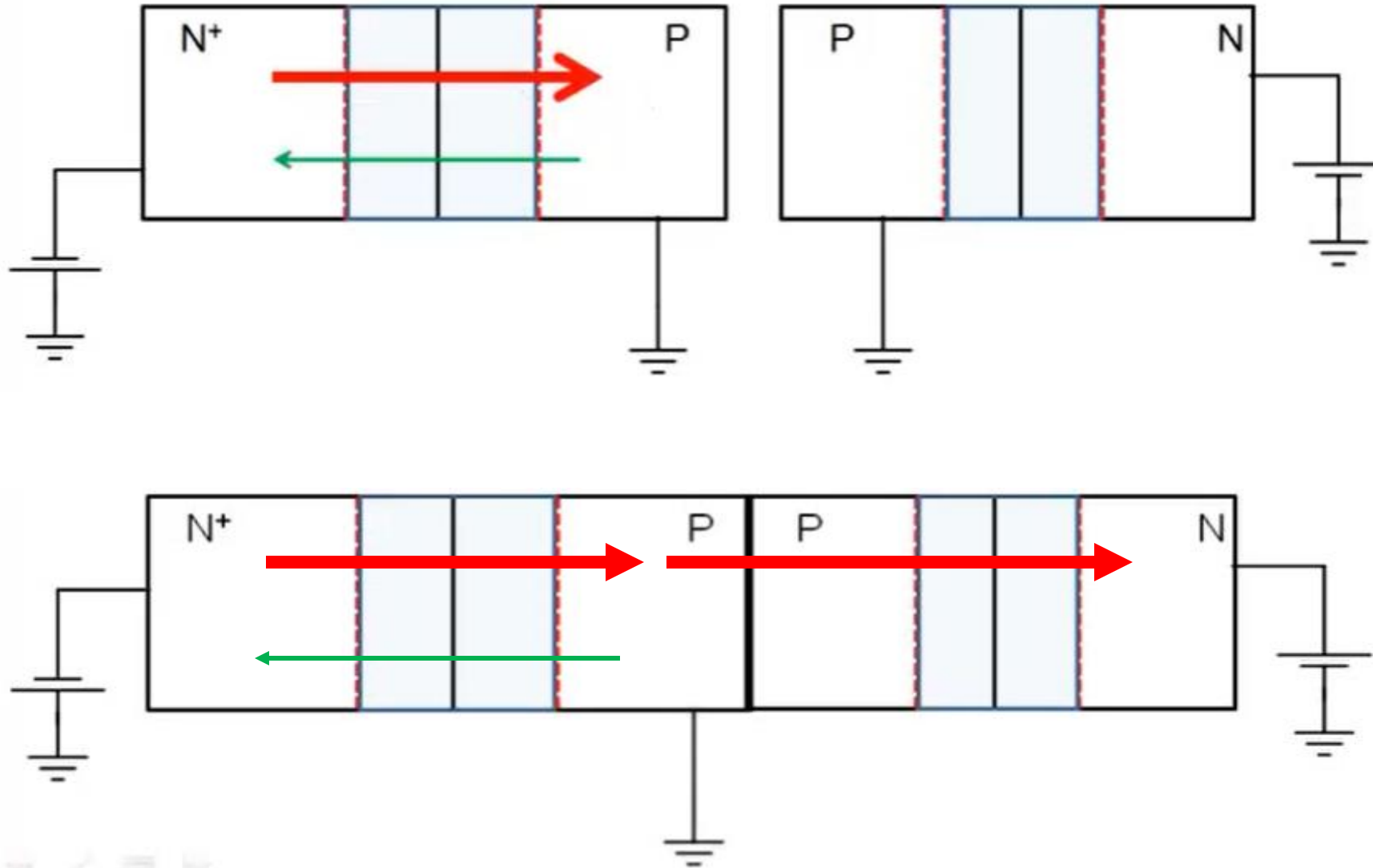


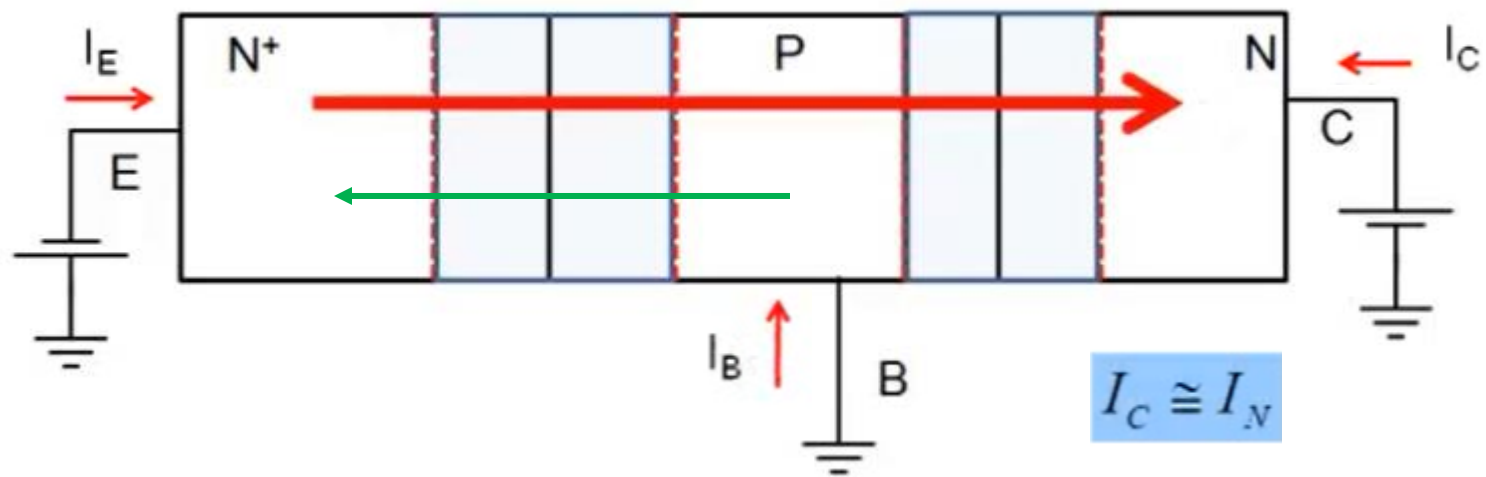

$$I_E = I_N + I_P$$

$$I_B \approx I_P$$
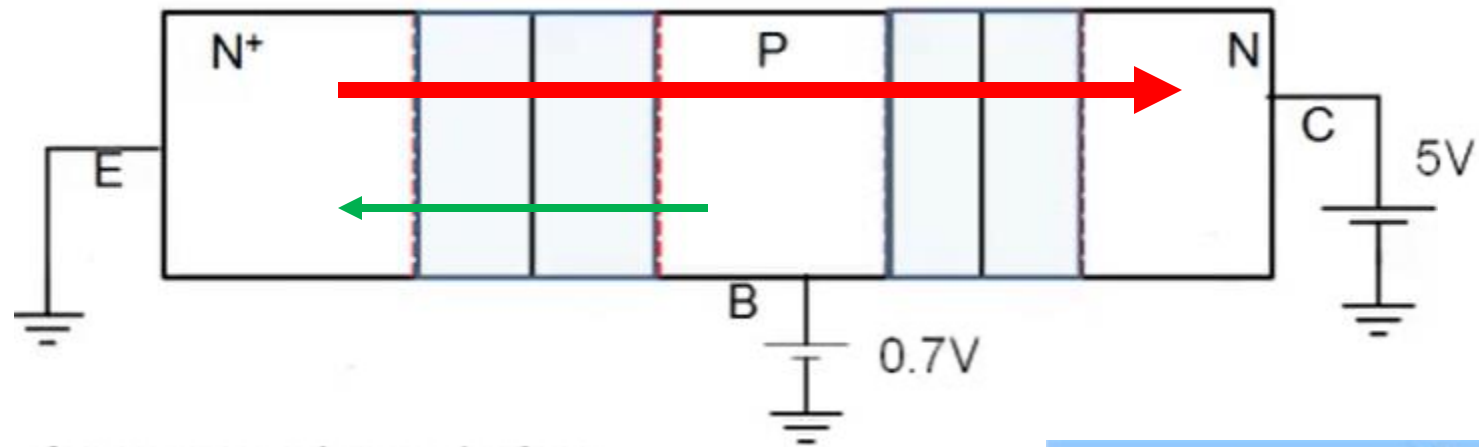
$$\text{Current Gain : } \beta = \frac{I_C}{I_B} = \frac{I_N}{I_P} \gg 1$$





Same operation as before


$$I_C = I_N \propto \exp\left(\frac{V_{BE}}{V_T}\right)$$

Transistor action

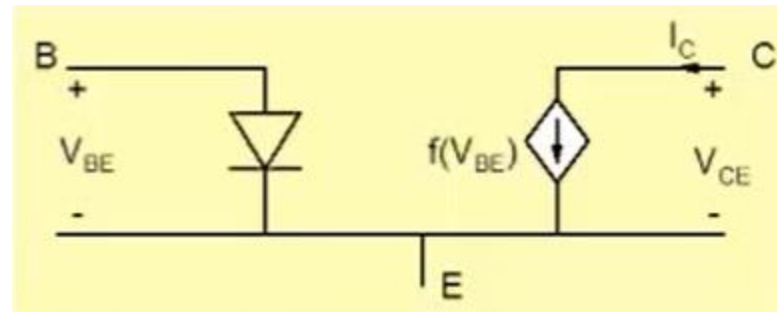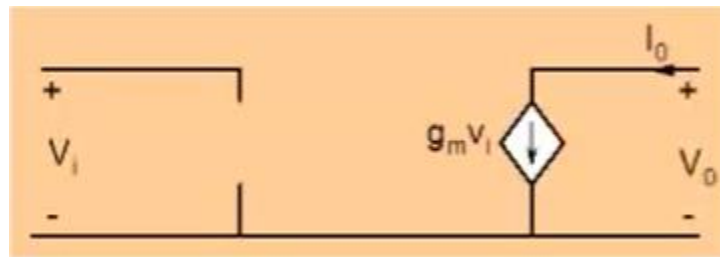Current is affected by base-emitter voltage and not by collector-base voltage



Alternative representation

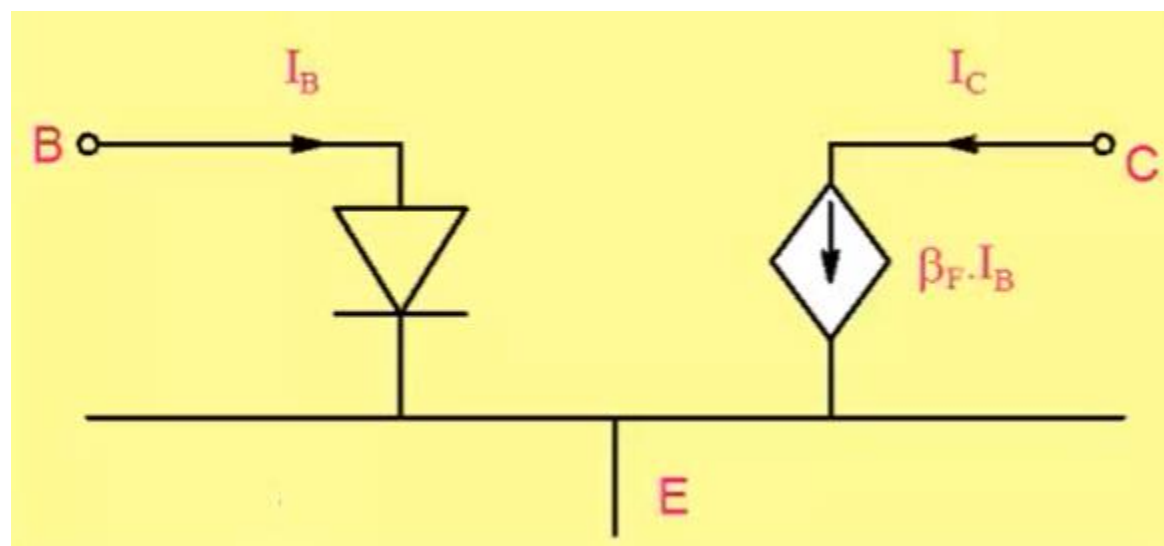

$$\beta = \frac{I_C}{I_B}$$





$$I_B = I_{BS} \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$

$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$


$$I_B = \frac{I_C}{\beta_F}$$

Transistor Characteristics

Forward Active Mode

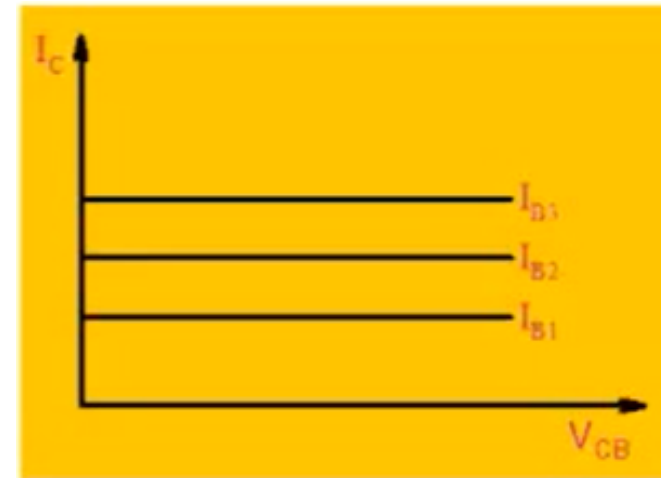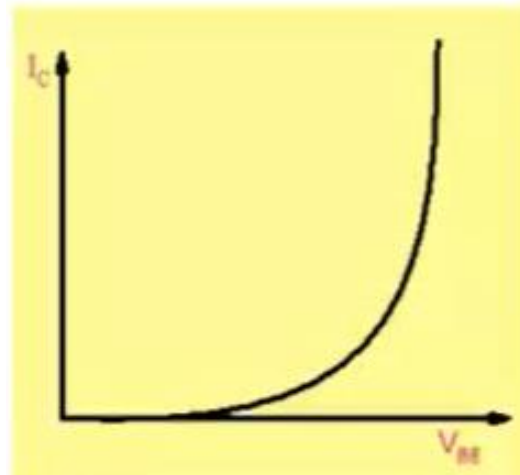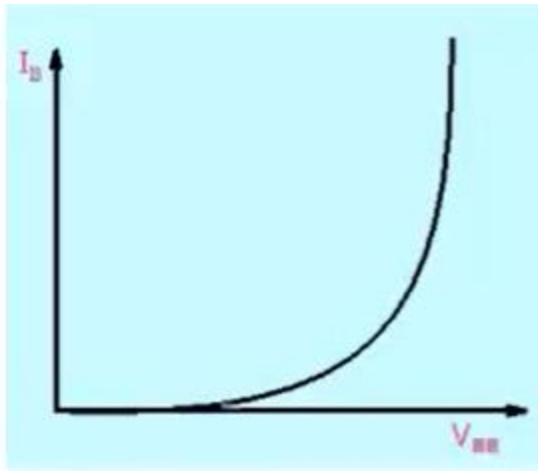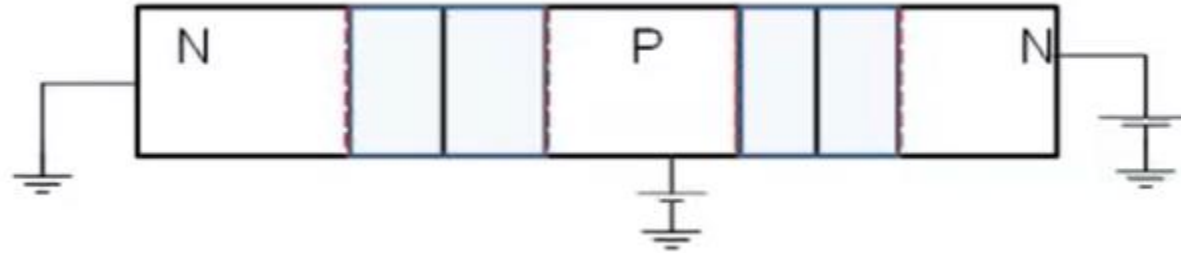



Output Characteristics of the transistor

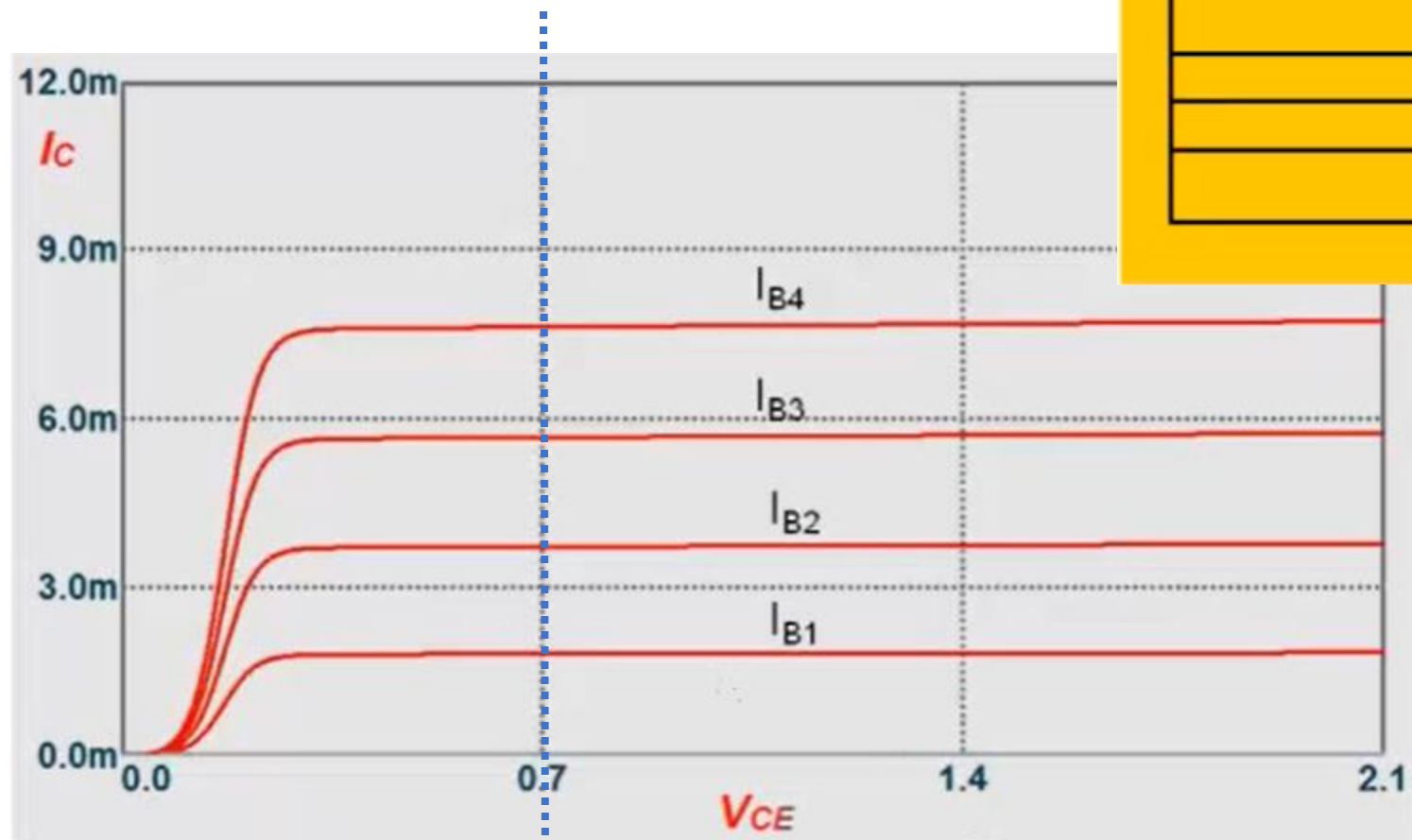



$$\begin{aligned} V_{CE} &= V_{CB} + V_{BE} \\ &= V_{BE} - V_{BC} \end{aligned}$$

$$V_{CE} = 0.7 - V_{BC}$$



Modes of operation

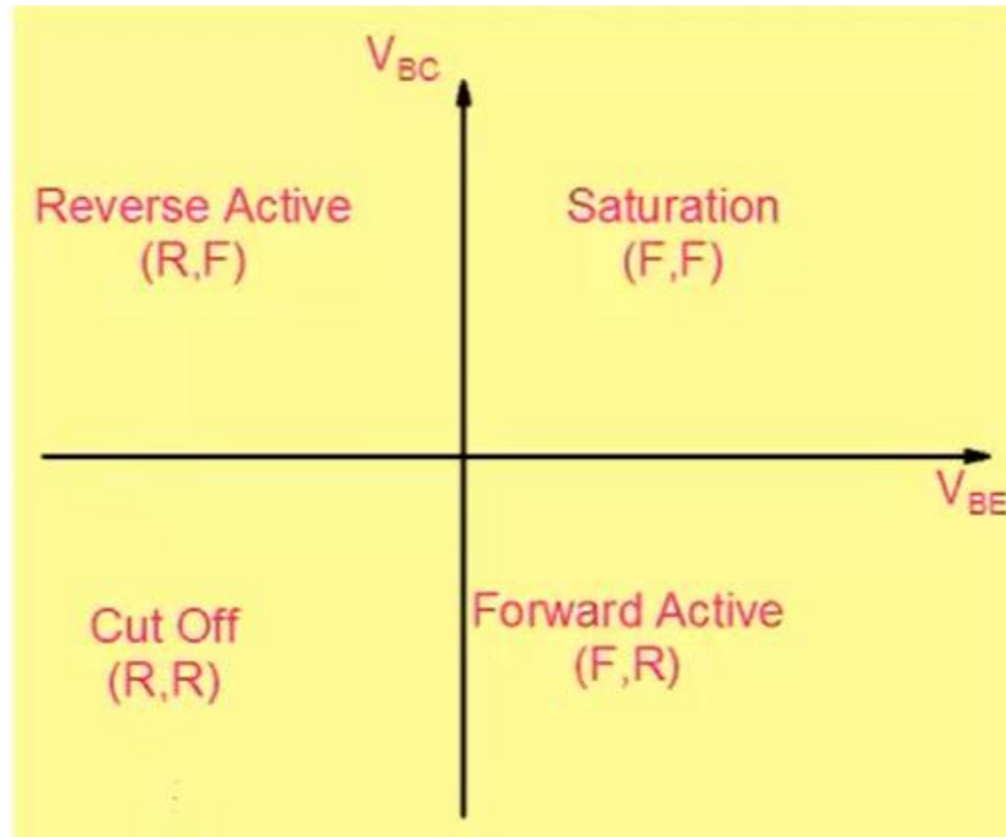
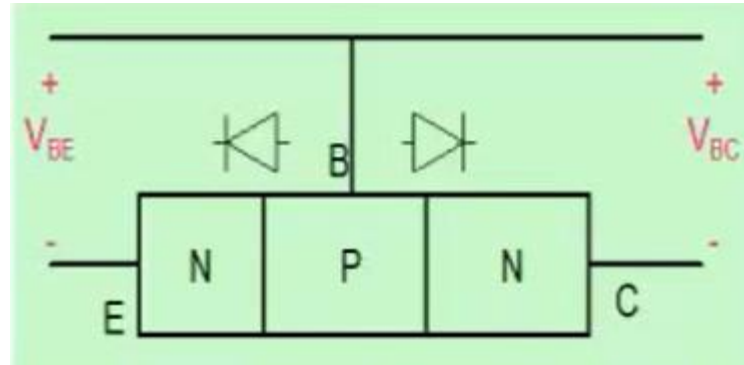



Saturation

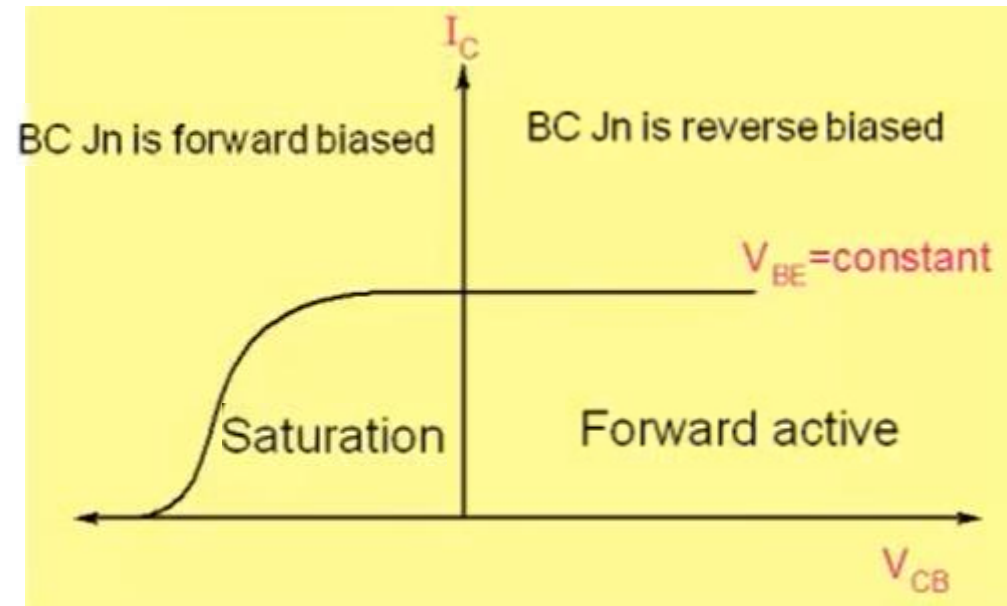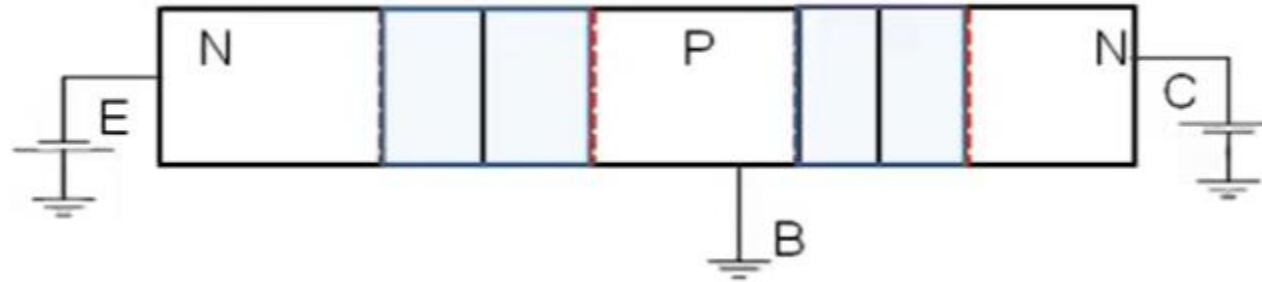

Why does I_C drop in saturation?

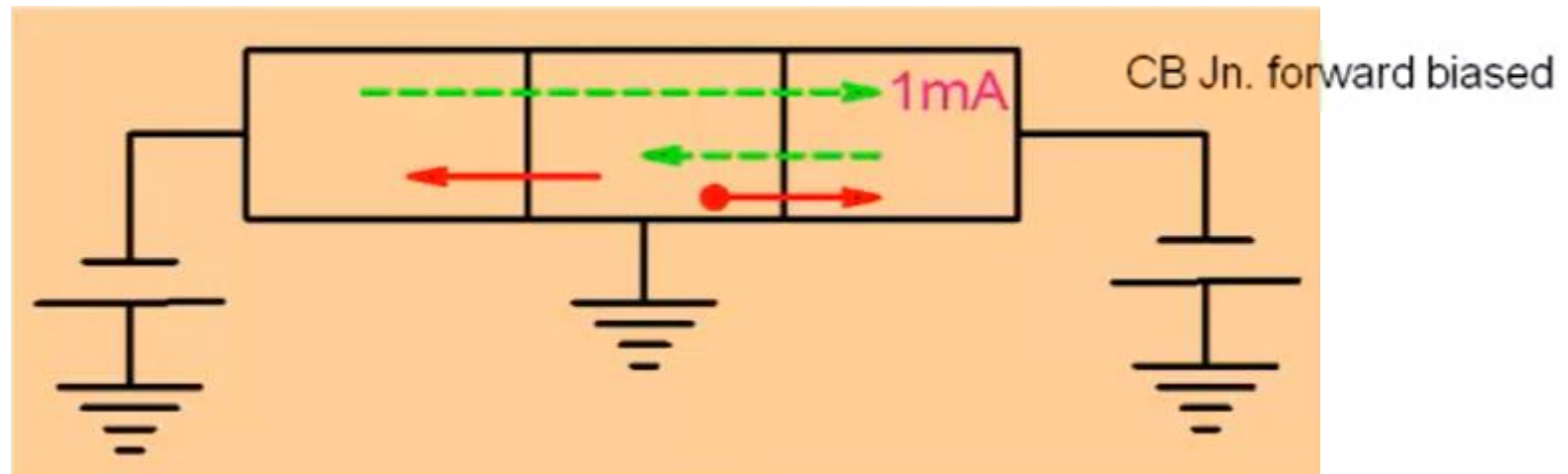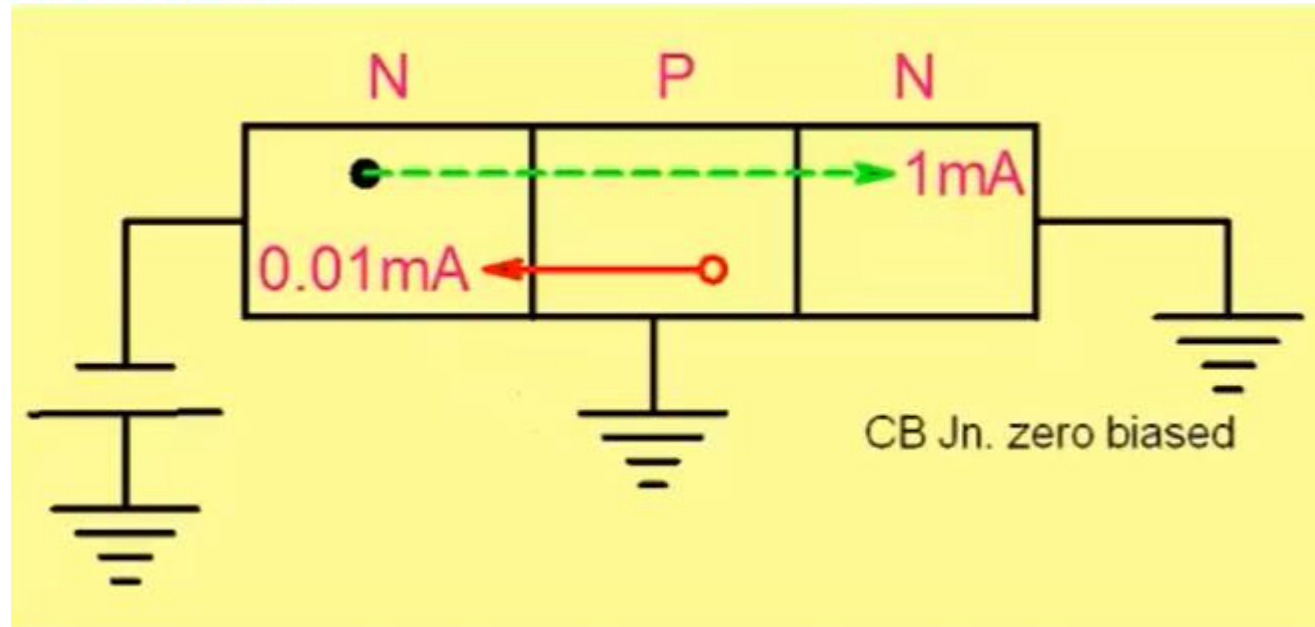

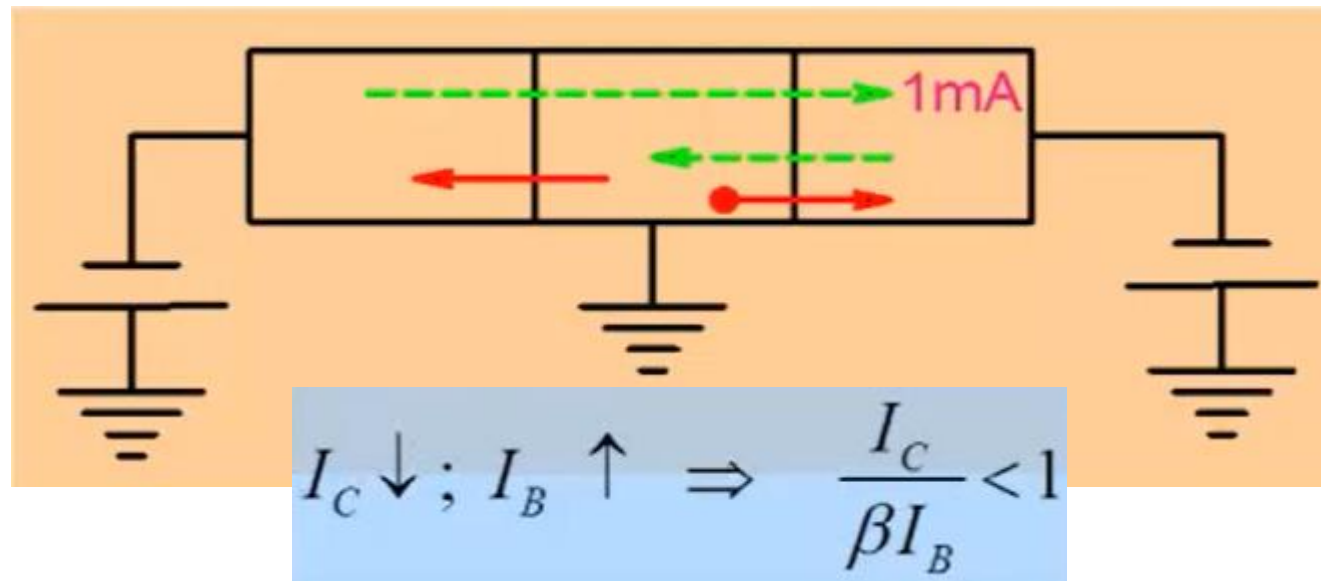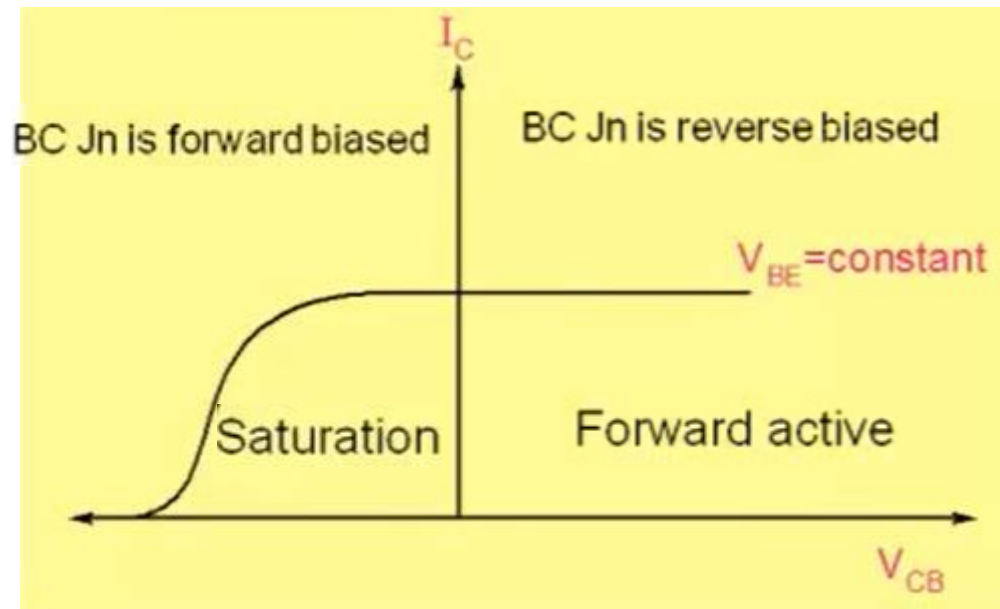

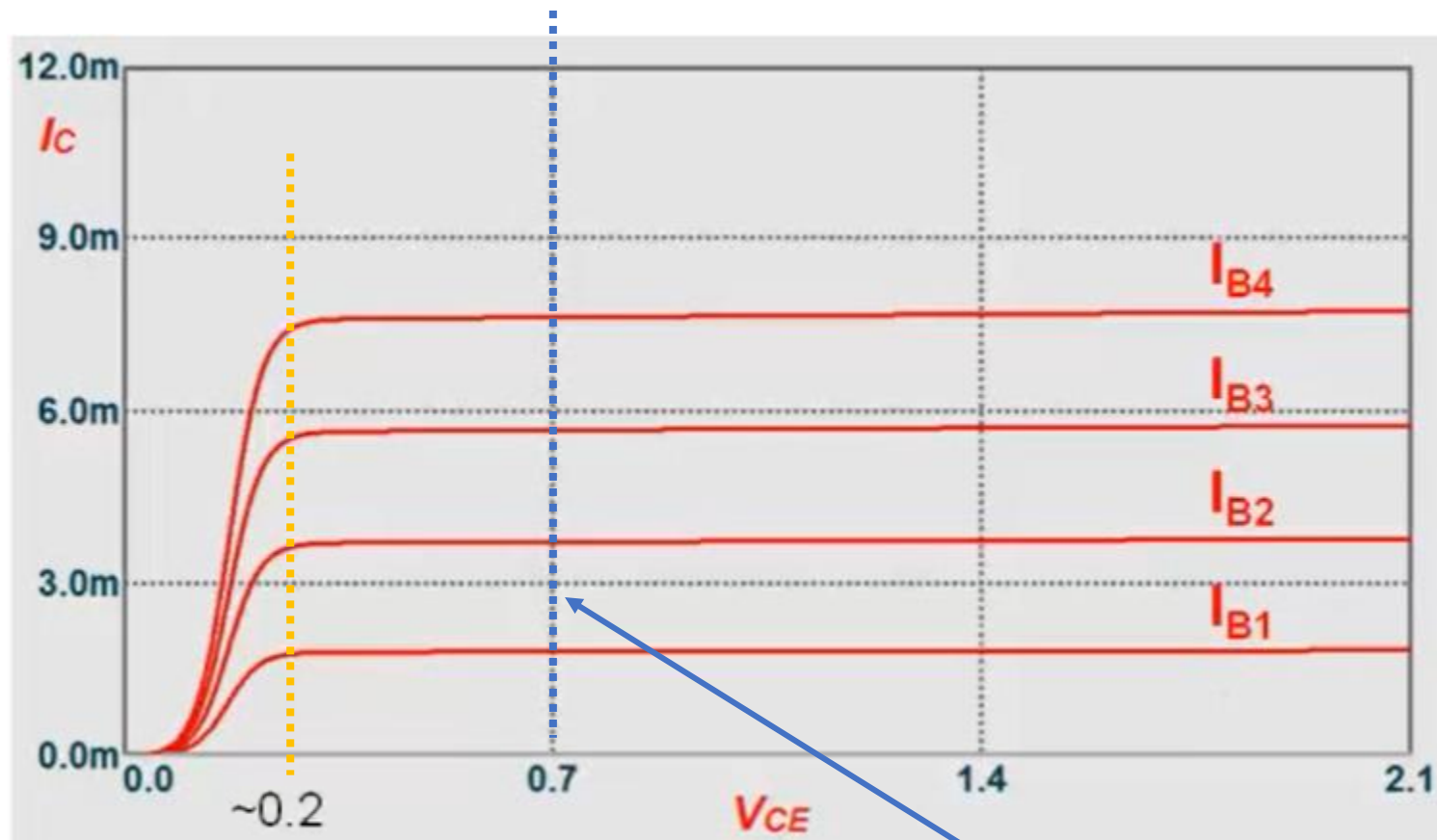

$$V_{CE} = V_{CB} + V_{BE}$$




$$= V_{BE} - V_{BC}$$

$$V_{CE} = 0.7 - V_{BC}$$

CB In start to get FB

Note that in saturation: $\frac{I_C}{\beta I_B} < 1$



Model of a BJT in Saturation mode

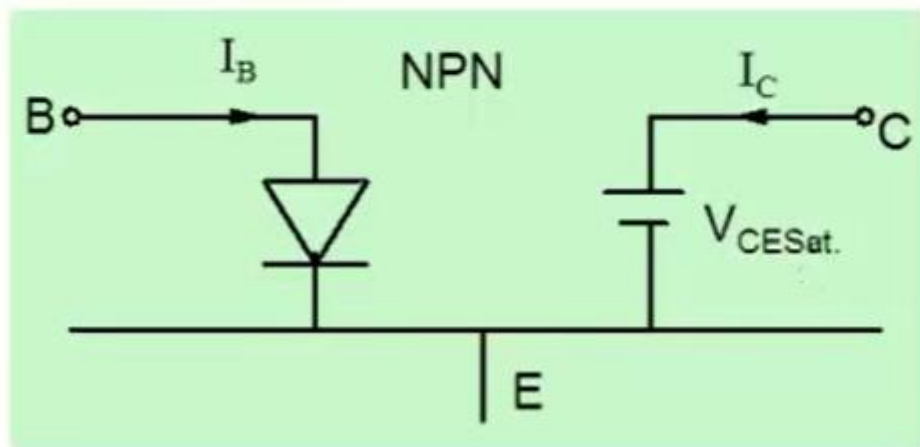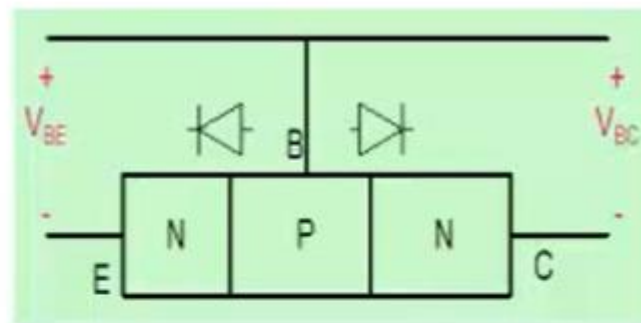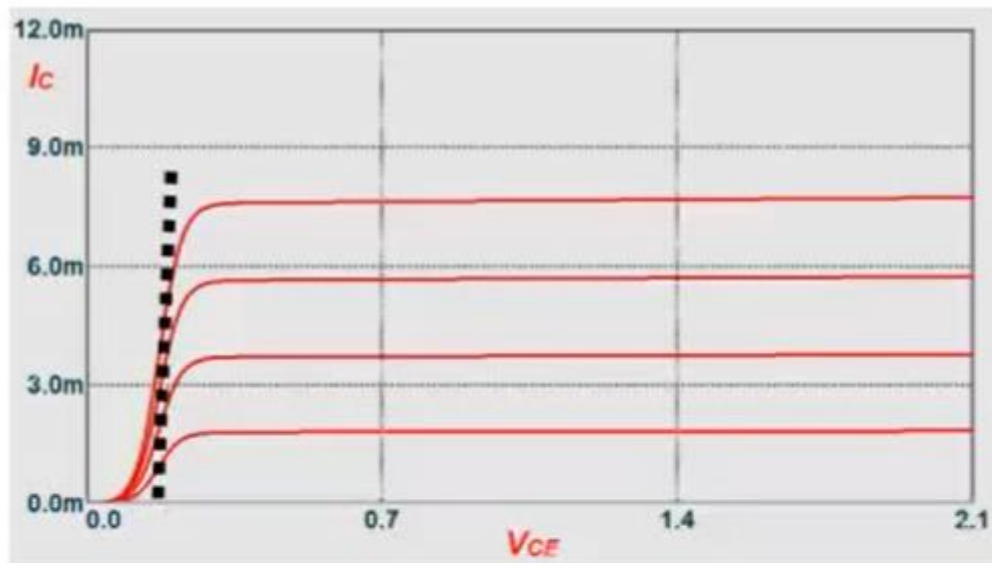

$$I_C \neq \beta_F I_B$$


$$V_{CESat.} \cong 0.2V$$

Model of a BJT in Saturation mode

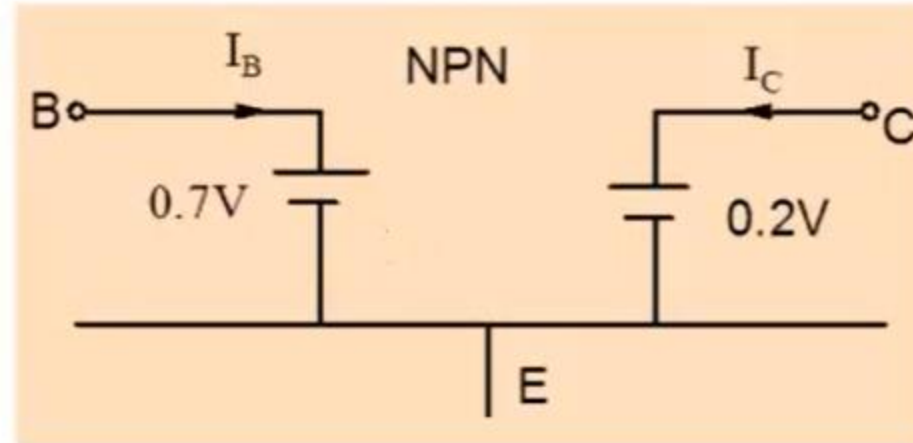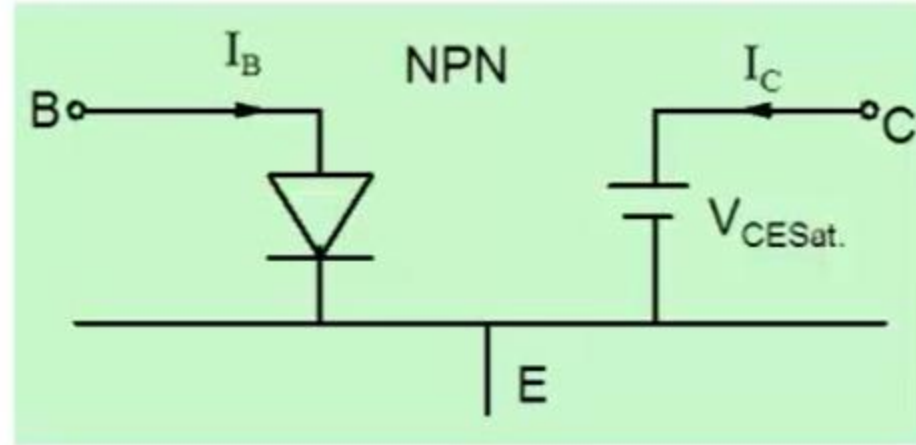


Generalized Transistor Model

Forward Active Mode

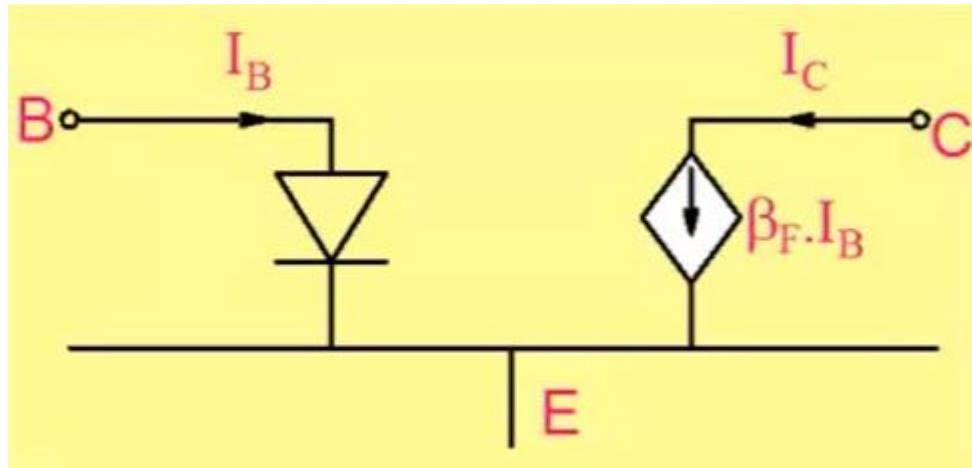
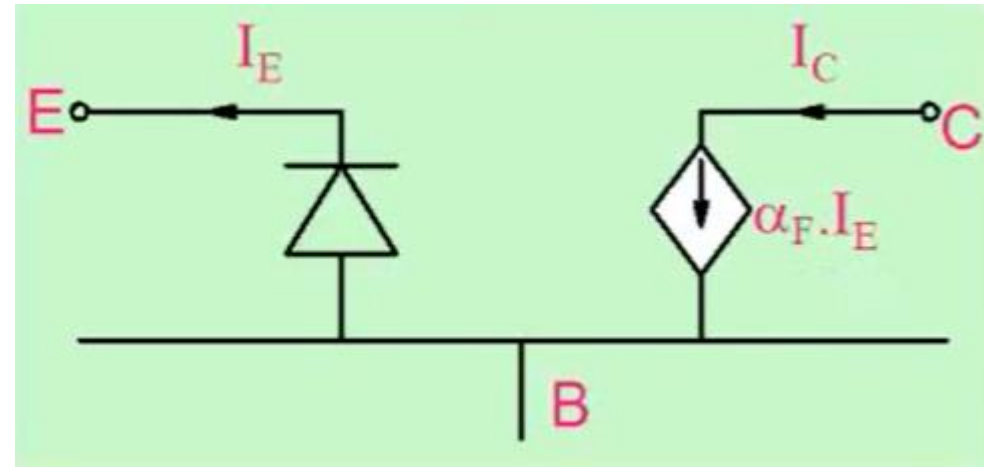
$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$
$$I_B = \frac{I_C}{\beta_F}$$



$$I_C = \beta_F \times I_B$$



$$I_E = I_C + I_B$$

$$I_C = \alpha_F \times I_E$$

$$\alpha_F = \frac{\beta_F}{1 + \beta_F}$$



β_F : Common Emitter Current Gain

α_F : Common Base Current Gain


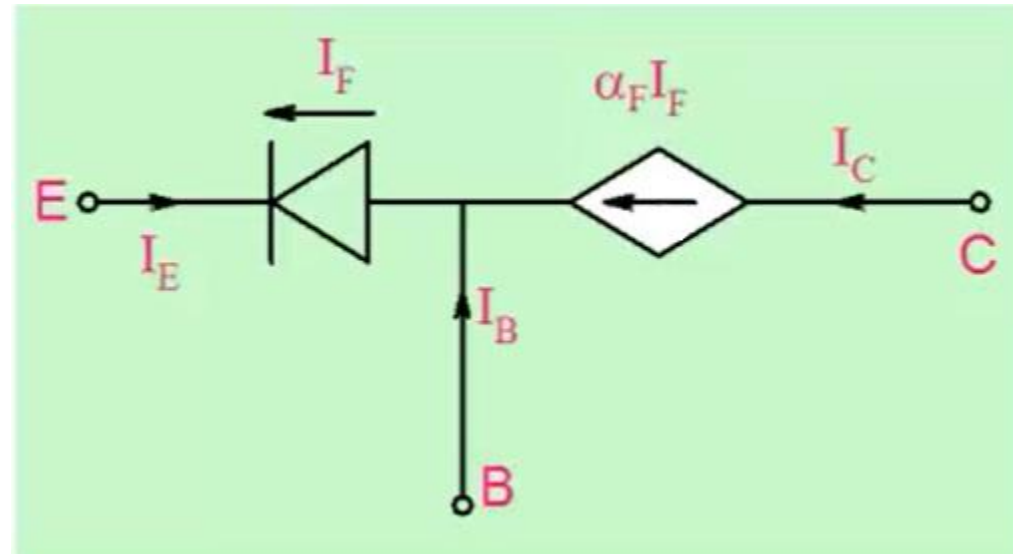
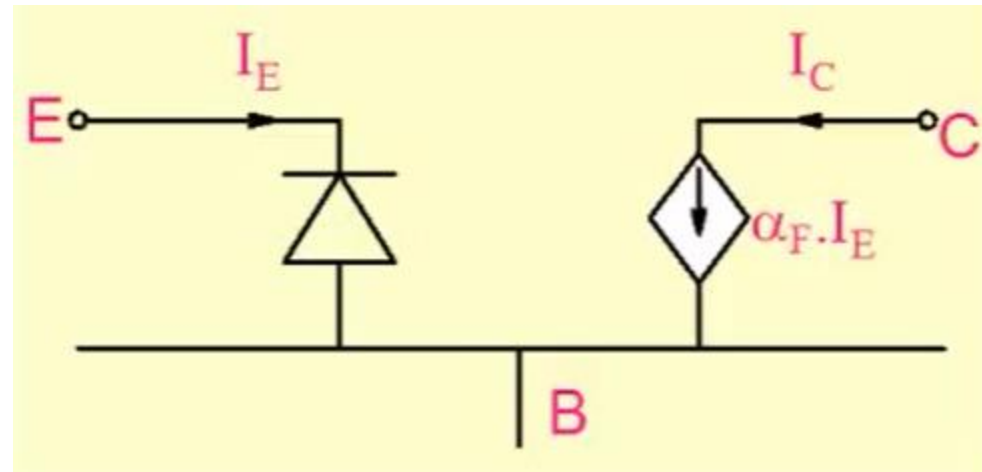




Forward Active Mode

Reverse Active Mode

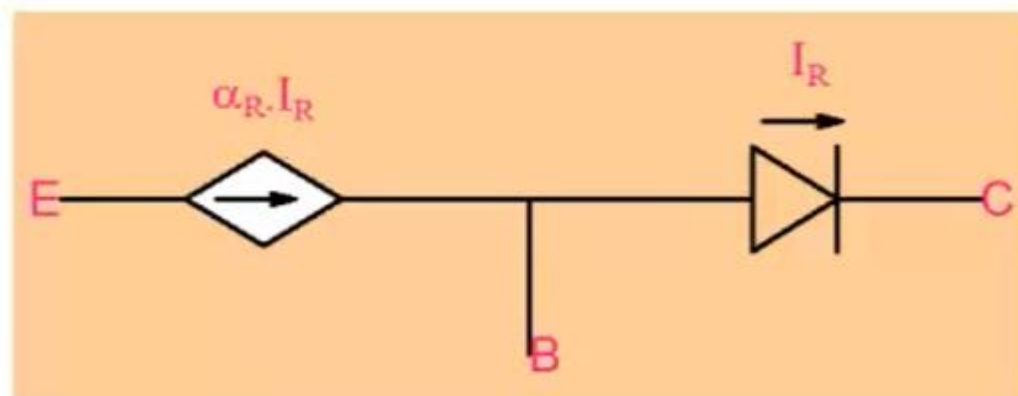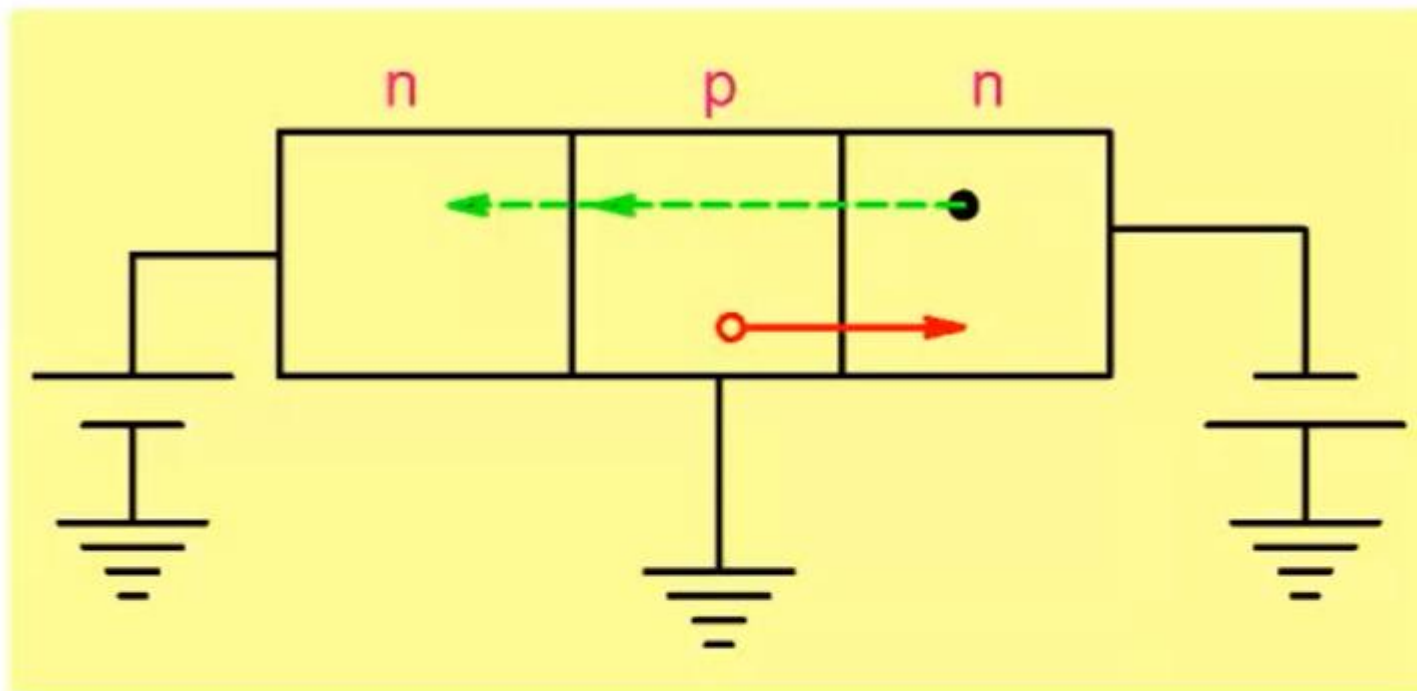


Ebers Moll Model

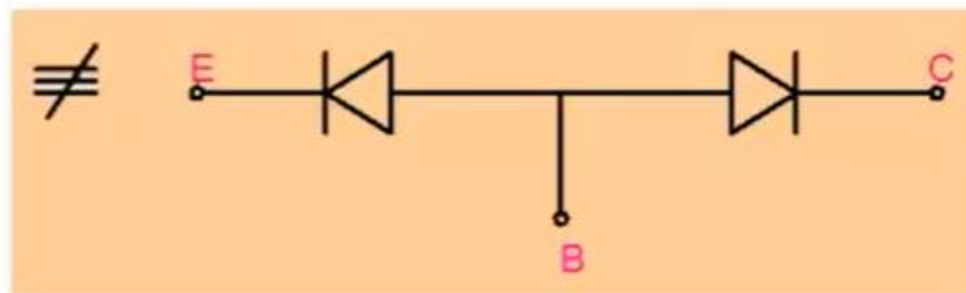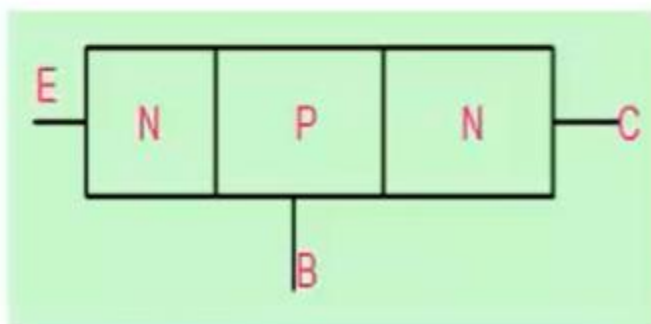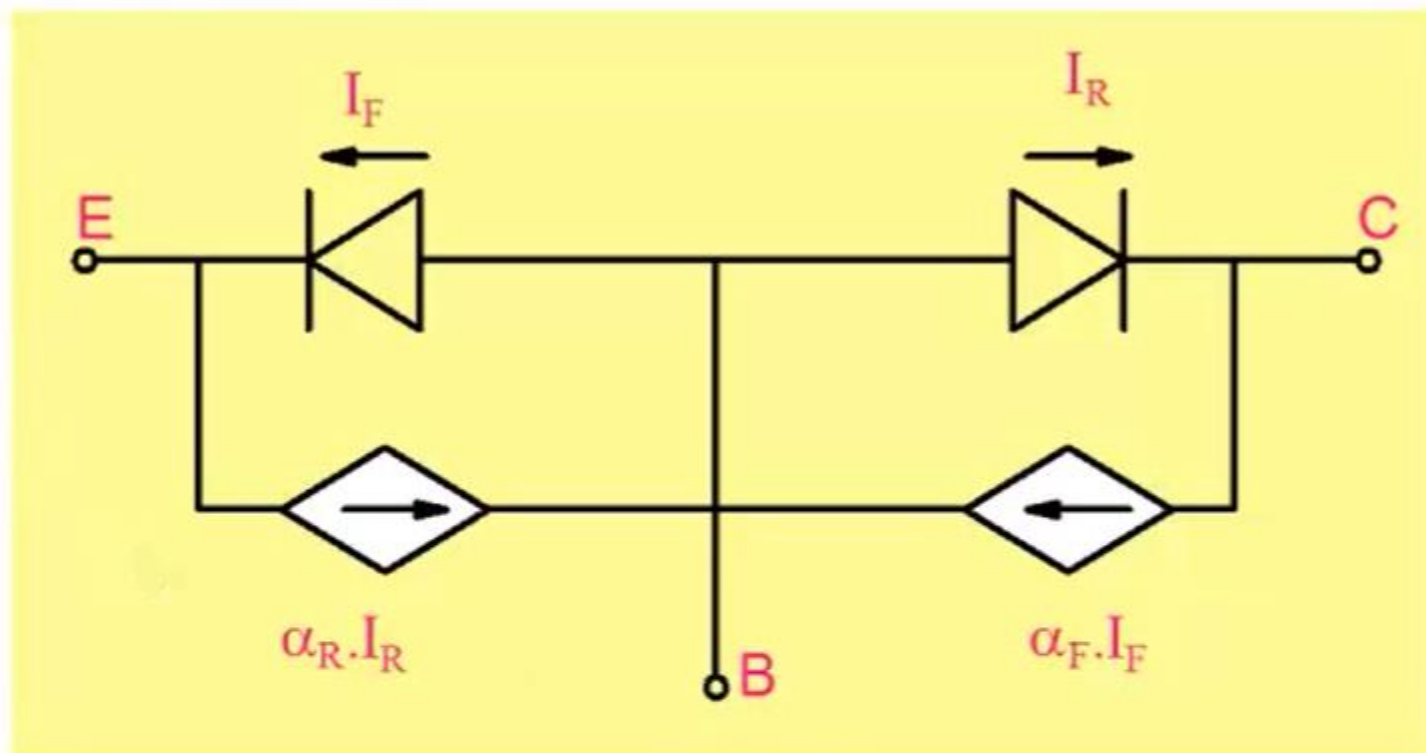


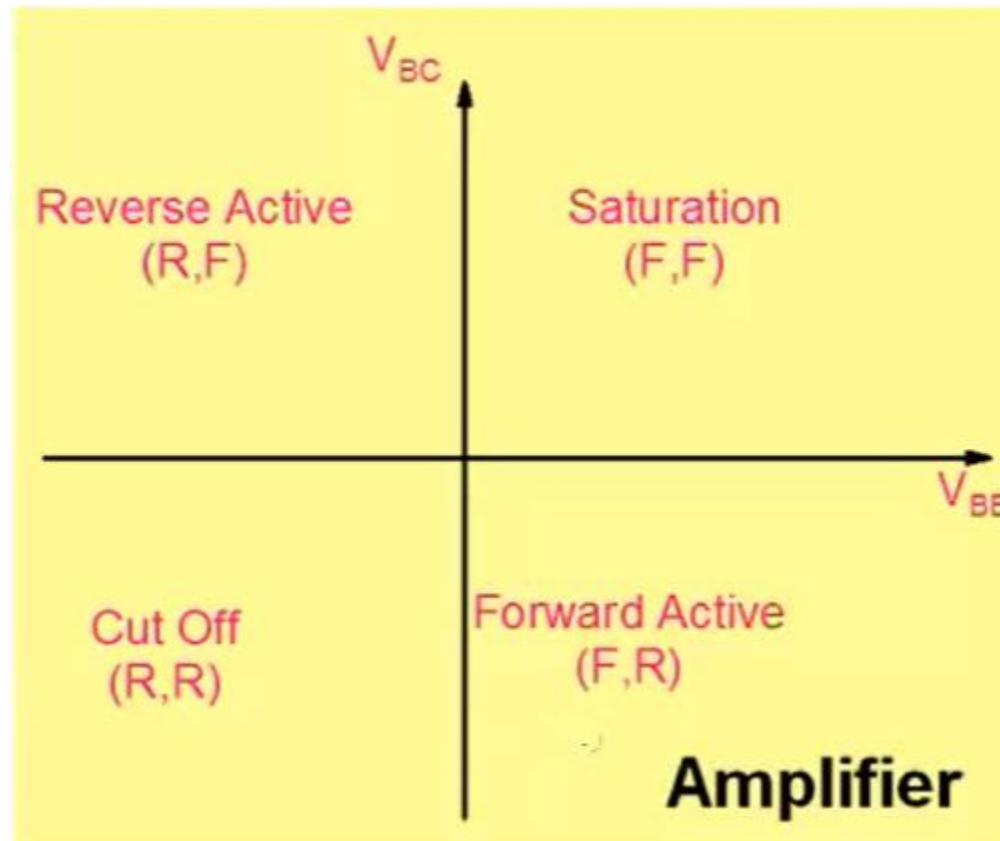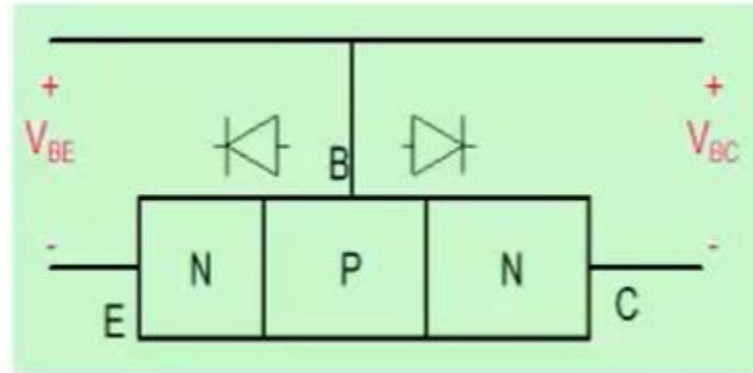

Forward Active Mode: Early Voltage

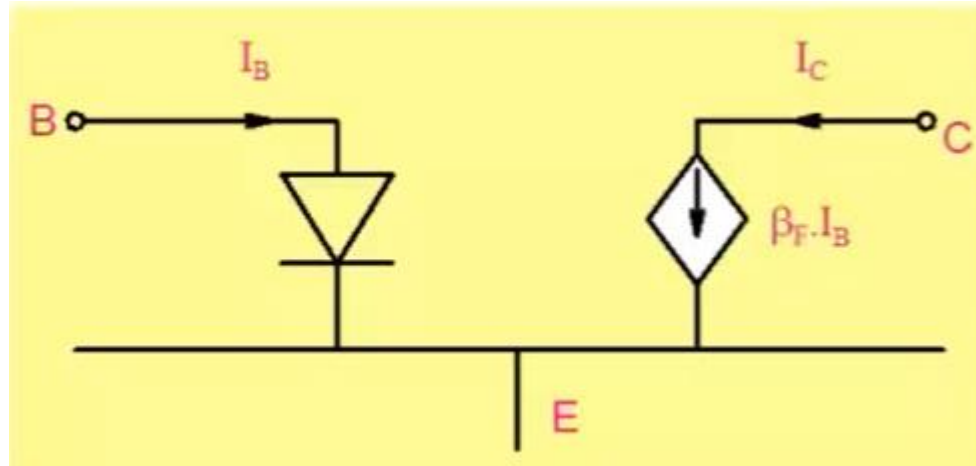

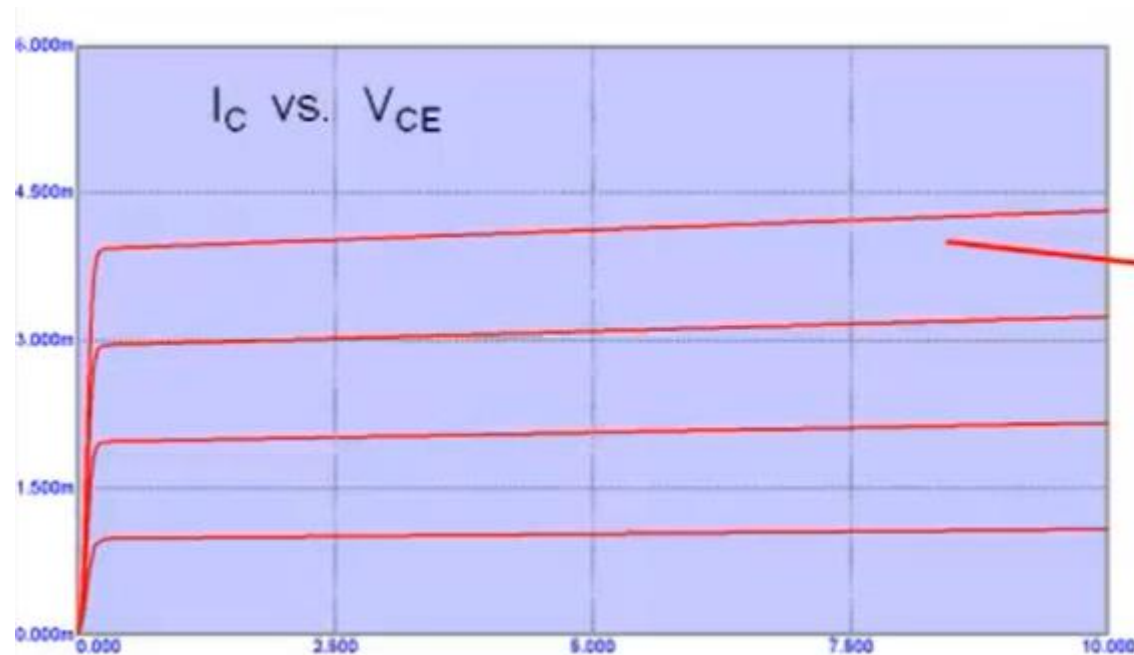
$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$
$$I_B = \frac{I_C}{\beta_F}$$



Current does increase with collector voltage through the increase is small

Early Voltage

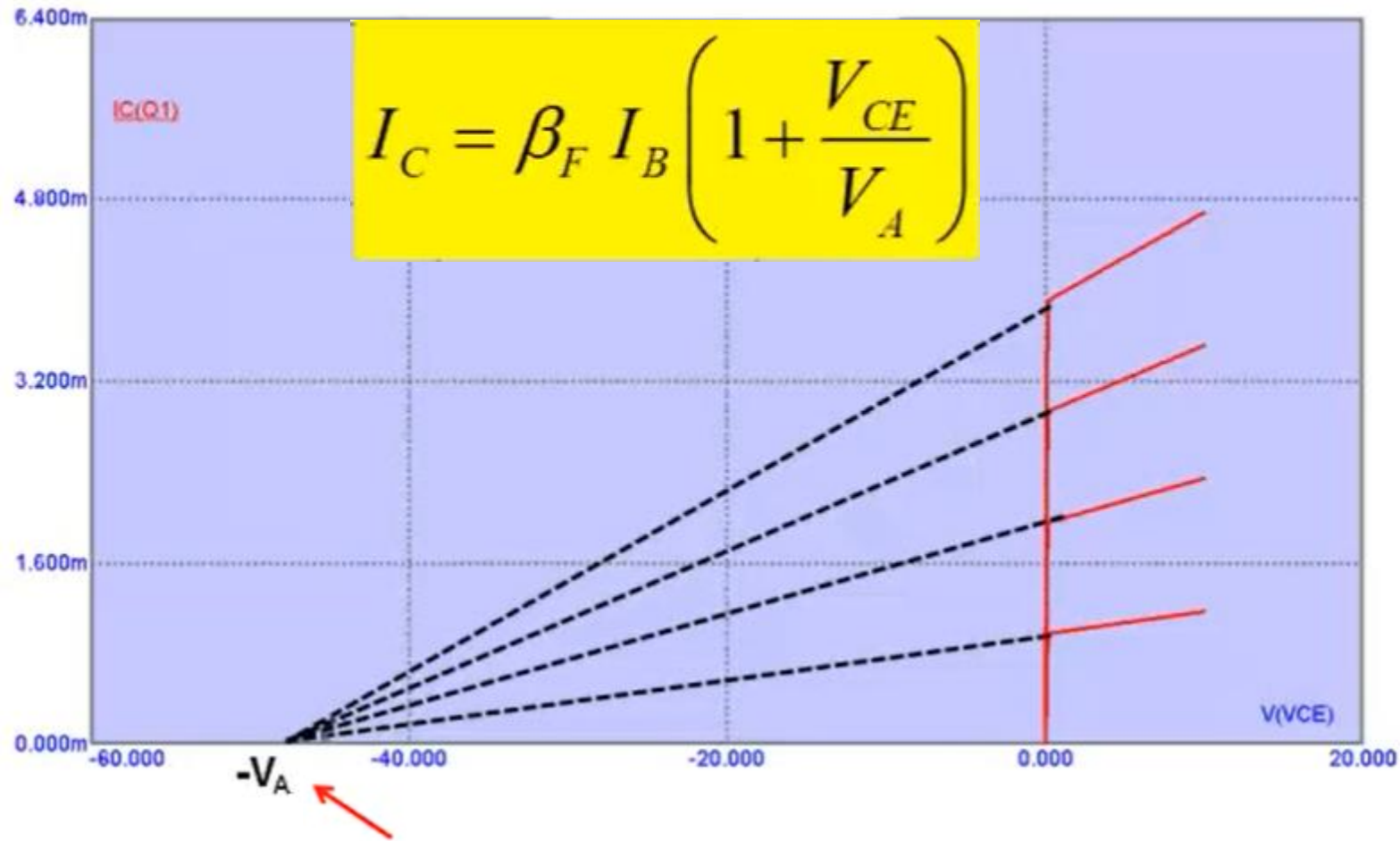

$$I_C = \beta_F I_B \left(1 + \frac{V_{CE}}{V_A} \right)$$

Early Voltage