

# AEC Assignment 3

Sricharan Vinoth Kumar, Roll No: 2024112022

## 1 Region Of Operation

### 1.1

MOSFETs have 3 regions of operation: Cutoff, Saturation and Triode.

1. **Cutoff:** Occurs when  $|V_{GS}| < |V_{TH}|$ , in NMOS and PMOS, Here the channel between the Source and the Drain has not been fully formed yet. So no current flows through the MOSFET, i.e,

$$I_{DS} = 0$$

2. **Triode/Linear:** Occurs in NMOS when,

$$V_{GS} \geq V_{TH} \text{ and } V_{DS} < V_{GS} - V_{TH}$$

and in PMOS when,

$$|V_{GS}| \geq |V_{TH}| \text{ and } |V_{DS}| < |V_{GS}| - |V_{TH}|$$

Here the channel between Source and Drain is fully formed and the MOSFET acts like a voltage dependent variable resistor.

The equation for  $I_{DS}$  is given by,

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2), \quad \text{for NMOS}$$
$$I_{DS} = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (2(V_{SG} - V_{TH})V_{SD} - V_{SD}^2), \quad \text{for PMOS}$$

Where,

$\mu_n$  – Electron Mobility

$\mu_p$  – Hole Mobility

$C_{ox}$  – Gate Oxide Capacitance Per Unit Area

$W$  – Channel Width

$L$  – Channel Length

### 3. **Saturation:** Occurs in NMOS when

$$V_{GS} \geq V_{TH} \text{ and } V_{DS} \geq V_{GS} - V_{TH}$$

and in PMOS when,

$$|V_{GS}| \geq |V_{TH}| \text{ and } |V_{DS}| \geq |V_{GS}| - |V_{TH}|$$

Here the channel has been pinched off at a point before the Drain terminal of the MOSFET. Current flowing in this region is mostly due to carrier injection at the pinch off point. Therefore,  $I_{DS}$  will not depend on  $V_{DS}$  as strongly as in Linear region. The equation for  $I_{DS}$  is given by,

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad \text{for NMOS}$$

$$I_{DS} = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - V_{TH})^2 (1 - \lambda V_{SD}) \quad \text{for PMOS}$$

Where,

$\mu_n$  – Electron Mobility

$\mu_p$  – Hole Mobility

$C_{ox}$  – Gate Oxide Capacitance Per Unit Area

$W$  – Channel Width

$L$  – Channel Length

$\lambda$  – Channel Length Modulation Parameter

## 1.2

### Common Parameters:

It given that  $\mu_n C_{ox} = 300 \mu A/V^2$  and  $\frac{W}{L} = \frac{2\mu}{1\mu} = 2$ . Therefore,

$$\mu_n C_{ox} \frac{W}{L} = 300 \times 10^{-6} \times 2 = 6 \times 10^{-4} A/V^2 \quad (1.2.1)$$

Also, we can use the results and equations mentioned in 1.1 to solve the following questions.

(a) Given:  $V_G = 2V, V_S = 0.5V, V_D = 0.7V, V_{TH} = 1V$

 


Figure 1.2.1: Circuit of 1.2(a)

$$\begin{aligned}
 V_{GS} &= V_G - V_S \\
 &= 2 - 0.5 \\
 &= 1.5V
 \end{aligned}$$

$\Rightarrow V_{GS} > V_{TH} \Rightarrow$  The MOSFET is not in Cutoff

$$\begin{aligned}
 V_{DS} &= V_D - V_S \\
 &= 0.7V - 0.5V \\
 &= 0.2V
 \end{aligned}$$

$$V_{GS} - V_{TH} = 1.5V - 1V = 0.5V$$

$\Rightarrow V_{DS} < V_{GS} - V_{TH} \Rightarrow$  The MOSFET is in **Triode Region**

$$\Rightarrow I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2), \quad \text{from 1.1}$$

$$I_{DS} = \frac{1}{2} \times 6 \times 10^{-4} \times (2(0.5)0.2 - 0.2^2)$$

$$I_{DS} = 3 \times 10^{-4} \times 0.16$$

$$\therefore I_{DS} = 48\mu A$$

(b) Given:  $V_G = 2V, V_S = 0.5V, V_D = 1.5V, V_{TH} = 1V$

 


Figure 1.2.2: Circuit of 1.2(b)

$$\begin{aligned}
 V_{GS} &= V_G - V_S \\
 &= 2 - 0.5 \\
 &= 1.5V
 \end{aligned}$$

$\Rightarrow V_{GS} > V_{TH} \Rightarrow$  The MOSFET is not in Cutoff

$$\begin{aligned}
 V_{DS} &= V_D - V_S \\
 &= 1.5 - 0.5 \\
 &= 1V
 \end{aligned}$$

$$V_{GS} - V_{TH} = 1.5V - 1V = 0.5V$$

$\Rightarrow V_{DS} > V_{GS} - V_{TH} \Rightarrow$  The MOSFET is in **Saturation Region**

$$\Rightarrow I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad \text{from 1.1}$$

$$I_{DS} = \frac{1}{2} \times 6 \times 10^{-4} \times 0.5^2, \text{ (neglecting Channel Length Modulation)}$$

$$I_{DS} = 3 \times 10^{-4} \times 0.25$$

$$\therefore I_{DS} = 75\mu A$$

(c) Given:  $V_G = 2V, V_S = 0.5V$  (Since, source always has the least potential),  $V_D = 1.5V, V_{TH} = 1V$

 


Figure 1.2.3: Circuit of 1.2(c)

Since the parameters are identical to the previous question (1.2(b)), the same results will apply, i.e,

**The MOSFET is operating in Saturation region.**

$$I_{DS} = 75\mu A$$

(d) Given:  $V_G = 2V, V_S = 0V, V_D = 2V, V_{TH} = 1V$

 


Figure 1.2.4: Circuit of 1.2(d)

$$\begin{aligned} V_{GS} &= V_G - V_S \\ &= 2 - 0 = 2V \end{aligned}$$

$$\Rightarrow V_{GS} > V_{TH} \Rightarrow \text{MOSFET is not in Cutoff}$$

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= 2 - 0 \\ &= 2V \end{aligned}$$

$$\begin{aligned} V_{GS} - V_{TH} &= 2 - 1 \\ &= 1V \end{aligned}$$

$$\Rightarrow V_{DS} > V_{GS} - V_{TH} \Rightarrow \text{MOSFET is in **Saturation**}$$

$$\Rightarrow I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad \text{from 1.1}$$

$$I_{DS} = \frac{1}{2} \times 6 \times 10^{-4} \times 1^2, \text{ (Neglecting Channel Length Modulation)}$$

$$\therefore I_{DS} = 300 \mu A$$

(e) Given:  $V_G = 1V, V_S = 0.5V, V_D = 1.5V, V_{TH} = 1V$

 


Figure 1.2.5: Circuit of 1.2(e)

$$\begin{aligned}
 V_{GS} &= V_G - V_S \\
 &= 1 - 0.5 \\
 &= 0.5V \\
 \Rightarrow V_{GS} &< V_{TH} \Rightarrow \text{MOSFET is in **Cutoff**} \\
 \Rightarrow I_{DS} &= 0A
 \end{aligned}$$

### 1.3

 


Figure 1.3.1: Circuit of 1.3

(a) To Show:

For the PMOS in the above configuration to be in Saturation,  $IR \leq |V_{thp}|$

Since Gate Current is Negligible, we can assume,

$$I_{DS} = I \quad (1.3.1)$$

The Source of the PMOS will be at the top, since Source

$$V_{GS} = V_G - V_S$$

By KVL,

$$V_G = 10 - V_{SD} - IR$$

$$V_S = 10 \quad (1.3.2)$$

$$\Rightarrow V_{GS} = (10 - V_{SD} - IR) - (10)$$

$$\Rightarrow V_{GS} = V_{DS} - IR$$

$$IR = V_{DS} - V_{GS}$$

We know that for a PMOS to be in Saturation,

$$\begin{aligned}
 |V_{DS}| &\geq |V_{GS}| - |V_{thp}| \\
 \implies |V_{GS}| - |V_{DS}| &\leq |V_{thp}| \\
 \implies -V_{GS} - (-V_{DS}) &\leq |V_{thp}| \\
 V_{DS} - V_{GS} &\leq |V_{thp}|
 \end{aligned}$$

Applying the result from 1.3.2, we get,

$$\implies IR \leq |V_{thp}|$$

Hence Proved

(b) Given:  $|V_{thp}| = 1V$ ,  $K_p = 0.2mA/V^2$ ,  $I_d = 0.1mA$

To Find:  $V_{SD}$ ,  $V_{SG}$

(i)  $R = 0\Omega$

$$\begin{aligned}
 IR = 0 &\implies IR < |V_{thp}| \\
 \implies \text{MOSFET is in Saturation}
 \end{aligned}$$

We know that, for a MOSFET is Saturation,

$$I_{DS} = -\frac{K_p}{2} (V_{SG} - |V_{TH}|)^2 \quad (1.3.3)$$

$$\implies V_{SG} = |V_{thp}| + \sqrt{\frac{2 \cdot I_{SD}}{K_p}} \quad (1.3.4)$$

$$\begin{aligned}
 V_{SG} &= 1 + \sqrt{\frac{2 \times 0.1 \times 10^{-3}}{0.2 \times 10^{-3}}} \\
 &= 1 + \sqrt{\frac{0.2}{0.2}} \\
 &= 1 + 1 \\
 \implies V_{SG} &= 2V
 \end{aligned}$$

Also from Equations 1.3.2, we know that,

$$\begin{aligned}
 V_{GS} &= V_{DS} - IR \\
 \implies V_{SG} &= V_{SD} \quad (IR = 0) \\
 \implies V_{SD} &= 2V
 \end{aligned}$$

**Therefore, we have  $V_{SG} = 2V$  and  $V_{SD} = 2V$ .**

(ii)  $R = 10k\Omega$

$$\begin{aligned}
 IR &= 0.1 \times 10^{-3} \times 10 \times 10^3 \\
 &= 1V \\
 \Rightarrow IR &= |V_{thp}| \Rightarrow \text{MOSFET is in Saturation, (by Q1.3(a))}
 \end{aligned}$$

From Equation 1.3.4,

$$\begin{aligned}
 V_{SG} &= |V_{thp}| + \sqrt{\frac{2 \cdot I_{SD}}{K_p}} \\
 &= 1 + \sqrt{\frac{0.2}{0.2}} \\
 &= 1 + 1 \\
 \Rightarrow V_{SG} &= 2V
 \end{aligned}$$

From Equations 1.3.2,

$$\begin{aligned}
 V_{GS} &= V_{DS} - IR \\
 -2 &= V_{DS} - 1 \\
 V_{DS} &= -2 + 1 \\
 \Rightarrow V_{SD} &= 1V
 \end{aligned}$$

**Therefore, we have  $V_{SG} = 2V$  and  $V_{SD} = 1V$ .**

(iii)  $R = 100k\Omega$

$$\begin{aligned}
 IR &= 0.1 \times 10^{-3} \times 100 \times 10^3 \\
 &= 10V \\
 \Rightarrow IR &> |V_{thp}| \Rightarrow \text{MOSFET is NOT in Saturation, (by Q1.3(a))}
 \end{aligned}$$

Since current through the MOSFET is not zero, the MOSFET cannot be in Cutoff. Therefore it must be in Linear Region. We know that for Linear Region,

$$\begin{aligned}
 I_{SD} &= \frac{1}{2} K_p (2(V_{SG} - |V_{thp}|)V_{SD} - V_{SD}^2) \\
 \Rightarrow 0.1 \times 10^{-3} &= \frac{1}{2} \times 0.2 \times 10^{-3} \times (2(V_{SG} - 1)V_{SD} - V_{SD}^2) \\
 \Rightarrow 1 &= 2(V_{SG} - 1)V_{SD} - V_{SD}^2
 \end{aligned}$$



From Equations 1.3.2, we know that  $V_{GS} = V_{DS} - IR$ . Substituting this in the Equation, we get,

$$1 = 2(-(V_{DS} - 10) - 1)V_{SD} - V_{SD}^2$$

$$\implies V_{SD}^2 + 18V_{SD} - 1 = 0$$

Solving the Quadratic, we get,

$$V_{SD} = 0.05535 \text{ \& } V_{SD} = -18.05535$$

Since  $V_S > V_D$ , as Source is the terminal with higher voltage in PMOS,  $V_{SD} = 0.05535$  is the only valid solution.

Since  $V_{GS} = V_{DS} - IR$ , we get,

$$\begin{aligned} V_{SG} &= IR + V_{SD} \\ &= 10 + 0.05535 \\ &= 10.05535 \end{aligned}$$

**Therefore, we have  $V_{SG} = 10.05535V$  and  $V_{SD} = 0.05535V$ .**

#### 1.4

 


Figure 1.4.1: Circuit of 1.4

Given:  $V_{thn} = 0.5V$ ,  $\mu_n C_{ox} = 100\mu A/V^2$ ,  $\mu_n C_{ox} = 100\mu A/V^2$ ,  $\frac{W}{L} = \frac{1.8\mu}{0.18\mu}$

$$\begin{aligned}
 K_n &= \mu_n C_{ox} \frac{W}{L} \\
 &= 100 \times 10^{-6} \times \frac{1.8\mu}{0.18\mu} \\
 &= 10^{-4} \times 10 \\
 \therefore K_n &= 10^{-3} A/V^2
 \end{aligned}$$

(a) To determine Region Of Operation,

$$\begin{aligned}
 V_S &= 0V \\
 V_G &= 0.8V \\
 V_{GS} &= V_G - V_S = 0.8V \\
 \implies V_{GS} &> V_{thn}
 \end{aligned}$$

$\implies$  MOSFET is not in Cutoff

$$\begin{aligned}
 V_{GS} - V_{TH} &= 0.8 - 0.5 \\
 &= 0.3V
 \end{aligned}$$

Assume the MOSFET is in Saturation. So the current across the MOSFET will be given by,

$$\begin{aligned}
 I_{DS} &= \frac{K_n}{2} (V_{GS} - V_{TH})^2 \\
 I_{DS} &= \frac{10^{-3}}{2} (0.3)^2 \\
 I_{DS} &= 0.045 \times 10^{-3} \\
 I_{DS} &= 45\mu A
 \end{aligned}$$

If we use KVL from V1 to ground,

$$\begin{aligned}
 1.8V - I_{DS}R - V_{DS} &= 0 \\
 V_{DS} &= 1.8 - 3000 \times 45 \times 10^{-6} \\
 &= 1.8 - 0.135 \\
 V_{DS} &= 1.665 > V_{GS} - V_{thp}
 \end{aligned}$$

Since the condition for Saturation is satisfied, we can confirm that the MOSFET is indeed in **Saturation region**.

- (b) From the previous question, biasing current is found out to be  $45\mu A$ . The transconductance is given by,

$$\begin{aligned} g_m &= \frac{2I_{DS}}{V_{GS} - V_{thn}} \\ &= \frac{2 \times 45 \times 10^{-6}}{0.8 - 0.5} \\ &= 3 \times 10^{-4} S \end{aligned}$$

- (c) For the MOSFET to be in Saturation,  $V_{GS}$  must follow 2 conditions

- (i)  $V_{GS} \geq V_{thn}$   
(ii)  $V_{DS} \geq V_{GS} - V_{thn}$

In Condition (i),

$$\begin{aligned} V_{GS} &\geq V_{thn} \\ \implies V_{GS} &\geq 0.5V \end{aligned}$$

In Condition (ii)

$$V_{DS} \geq V_{GS} - V_{thn}$$

Applying KVL from V1 to ground,

$$\begin{aligned} 1.8V - I_{DS}R - V_{DS} &= 0 \\ V_{DS} &= 1.8 - I_{DS}R \end{aligned}$$

We know that

$$\begin{aligned} I_{DS} &= \frac{K_n}{2} (V_{GS} - V_{TH})^2 \\ \implies V_{DS} &= 1.8 - 3000\left(\frac{K_n}{2}\right)(V_{GS} - V_{thn})^2 \\ \implies 1.8 - 3000\left(\frac{K_n}{2}\right)(V_{GS} - V_{thn})^2 &\geq V_{GS} - V_{thn} \end{aligned} \tag{1.4.1}$$

In the above inequality, to find point of equality,

$$\begin{aligned} 1.8 - 3000\left(\frac{K_n}{2}\right)(V_{GS} - V_{thn})^2 &= V_{GS} - V_{thn} \\ 1.8 - 3000\left(\frac{K_n}{2}\right)(V_{GS} - V_{thn})^2 - (V_{GS} - V_{thn}) &= 0 \\ 1.8 - 3000(0.5 \times 10^{-3})(V_{GS} - V_{thn})^2 - (V_{GS} - V_{thn}) &= 0 \\ 1.8 - 1.5(V_{GS} - V_{thn})^2 - (V_{GS} - V_{thn}) &= 0 \end{aligned}$$

Considering this as a quadratic in  $V_{GS} - V_{thn}$  (i.e,  $V_{DSAT}$ ), upon solving, we get,

$$\begin{aligned} V_{GS} - V_{thn} &= -1.478 \quad \& \quad V_{GS} - V_{thn} = 0.811 \\ \implies V_{GS} &= -0.978 \quad \& \quad V_{GS} = 1.311 \end{aligned}$$

Using these in the inequality obtained in 1.4.1, we get that for the inequality to hold,

$$V_{GS} \in [-0.978, 1.311] \quad (1.4.2)$$

Combining 1.4.2 with Condition (i), we get that for the MOSFET to be in Saturation, we need,

$$V_{GS} \in [0.5, 1.311]$$

Range =  $1.311 - 0.5 = 0.811V$ , Lower Limit =  $0.5V$ , Upper Limit,  $1.311V$

## 2 Small Signal Model And Impedances

### 2.1

The Small Signal Models of a NMOS and a PMOS are:

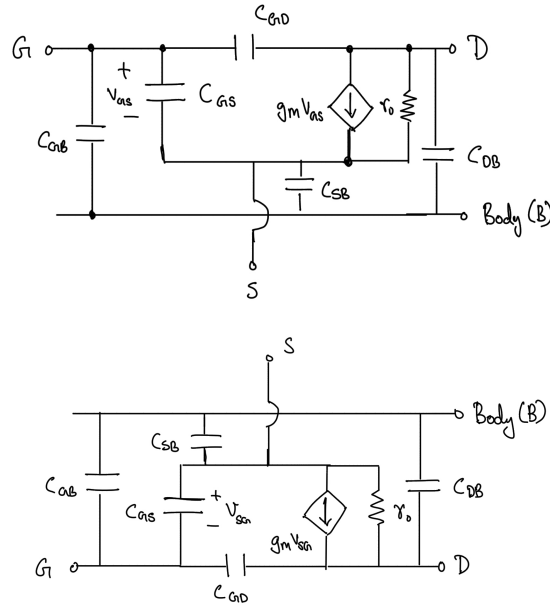


Figure 2.1.1: Small Signal Model of NMOS (top) and PMOS (bottom)

## 2.2

Let  $v_{in}$  be the input test voltage, and  $i_{in}$  be the current at the input terminal. Then the input impedance  $z_{in}$  is given by,

$$z_{in} = \frac{v_{in}}{i_{in}} \quad (2.2.1)$$

(i)

 


Figure 2.2.1: Circuit of 2.2(i)

Grounding the Source and Drain terminals, the equivalent small signal circuit for the same will be as Figure 2.2.2

 


Figure 2.2.2: Equivalent Circuit of 2.2(i)

Looking at the circuit we can see that  $i_{in}$  flows into an open terminal. Therefore, by KCL,  $i_{in}$  must be zero.

$$\therefore z_{in} \rightarrow \infty$$

(ii)

Grounding the Source and Gate terminals, the equivalent small signal circuit for the same will be as Figure 2.2.4

 


Figure 2.2.3: Circuit of 2.2(ii)

 


Figure 2.2.4: Equivalent Circuit of 2.2(ii)

From the equivalent circuit, we can see that,

$$\begin{aligned}
 i_{in} &= i_x + i_y, \text{ By KCL} \\
 v_g &= 0 \\
 v_s &= 0 \\
 \Rightarrow v_{gs} &= 0 \\
 \Rightarrow g_m v_{gs} &= 0 \\
 \Rightarrow i_x &= 0 \\
 \Rightarrow i_{in} &= i_y = \frac{v_{in}}{r_o} \\
 \Rightarrow z_{in} &= r_o
 \end{aligned}$$

Therefore,  $z_{in} = r_o$ .

(iii)

Grounding the Drain and Gate terminals, the equivalent small signal circuit for the same will be as Figure 2.2.6

 


Figure 2.2.5: Circuit of 2.2(iii)

 


Figure 2.2.6: Equivalent Circuit of 2.2(iii)

From the equivalent circuit, we can see that,

$$\begin{aligned}
 i_{in} &= i_x + i_y \\
 v_g &= 0 \\
 v_s &= v_{in} \\
 \Rightarrow v_{gs} &= -v_{in} \\
 \Rightarrow g_m v_{gs} &= -g_m v_{in} \\
 i_x &= -g_m v_{gs} \\
 \Rightarrow i_x &= g_m v_{in} \\
 i_y &= \frac{v_{in}}{r_o} \\
 \Rightarrow i_{in} &= g_m v_{in} + \frac{v_{in}}{r_o} \\
 \Rightarrow z_{in} &= \frac{1}{g_m + \frac{1}{r_o}}
 \end{aligned}$$

Therefore,  $z_{in} = \frac{1}{g_m + \frac{1}{r_o}}$

(iv)

 


Figure 2.2.7: Circuit of 2.2(iv)

Grounding the Drain and Source terminals, the equivalent small signal circuit for the same will be as Figure 2.2.8

 


Figure 2.2.8: Equivalent Circuit of 2.2(iv)

Looking at the circuit we can see that  $i_{in}$  flows into an open terminal. Therefore, by KCL,  $i_{in}$  must be zero.

$$\therefore z_{in} \rightarrow \infty$$

(v)

 


Figure 2.2.9: Circuit of 2.2(v)

Grounding the Drain and Gate terminals, the equivalent small signal circuit for



 


Figure 2.2.10: Equivalent Circuit of 2.2(v)

the same will be as Figure 2.2.10

From the equivalent circuit we can see that,

$$\begin{aligned}
 i_{in} &= i_x + i_y \\
 v_s &= v_{in} \\
 v_g &= 0 \\
 \Rightarrow v_{sg} &= v_{in} \\
 i_x &= g_m v_{sg} \\
 \Rightarrow i_x &= g_m v_{in} \\
 i_y &= \frac{v_{in}}{r_o} \\
 \Rightarrow i_{in} &= g_m v_{in} + \frac{v_{in}}{r_o} \\
 \Rightarrow z_{in} &= \frac{1}{g_m + \frac{1}{r_o}}
 \end{aligned}$$

(vi)

 


Figure 2.2.11: Circuit of 2.2(vi)

Grounding the Source and Gate terminals, the equivalent small signal circuit for the same will be as Figure 2.2.12

 


Figure 2.2.12: Equivalent Circuit of 2.2(vi)

From the equivalent circuit we can see that.

$$\begin{aligned}
 i_{in} &= i_x + i_y \\
 v_s &= 0 \\
 v_g &= 0 \\
 \Rightarrow v_{sg} &= 0 \\
 \Rightarrow g_m v_{sg} &= 0 \\
 \Rightarrow i_y &= 0 \\
 \Rightarrow i_{in} &= i_x = \frac{v_{in}}{r_o} \\
 \Rightarrow z_{in} &= r_o
 \end{aligned}$$

(vii)

 


Figure 2.2.13: Circuit of 2.2(vii)

Grounding the Source terminal, the equivalent small signal circuit for the same will be as Figure 2.2.14

 


Figure 2.2.14: Equivalent Circuit of 2.2(vii)

From the equivalent circuit we can see that.

$$i_{in} = i_x + i_y + i_z$$

Since  $i_x$  flows into an open terminal, it is zero.

$$\begin{aligned} v_g &= v_{in} \\ v_s &= 0 \\ \Rightarrow v_{gs} &= v_{in} \\ i_y &= g_m v_{gs} = g_m v_{in} \\ i_z &= \frac{v_{in}}{r_o} \\ \Rightarrow i_{in} &= 0 + g_m v_{in} + \frac{v_{in}}{r_o} \\ \Rightarrow z_{in} &= \frac{1}{g_m + \frac{1}{r_o}} \end{aligned}$$

(viii)



Figure 2.2.15: Circuit of 2.2(viii)

Grounding the Drain terminal, the equivalent small signal circuit for the same

 


Figure 2.2.16: Equivalent Circuit of 2.2(viii)

will be as Figure 2.2.16

From the equivalent circuit we can see that.

$$\begin{aligned}
 i_{in} &= i_x + i_y \\
 v_g &= 0 \\
 v_s &= v_{in} \\
 \Rightarrow v_{gs} &= -v_{in} \\
 i_x &= -g_m v_{gs} = g_m v_{in} \\
 i_y &= \frac{v_{in}}{r_o} \\
 i_{in} &= g_m v_{in} + \frac{v_{in}}{r_o} \\
 \Rightarrow z_{in} &= \frac{1}{g_m + \frac{1}{r_o}}
 \end{aligned}$$

(ix)

 


Figure 2.2.17: Circuit of 2.2(ix)

Grounding the Gate and the Resistor terminals, the equivalent small signal circuit for the same will be as Figure 2.2.18

 


Figure 2.2.18: Equivalent Circuit of 2.2(ix)

From the equivalent circuit we can see that.

$$\begin{aligned}
 i_{in} &= i_x + i_y \\
 v_g &= 0 \\
 v_s &= i_{in} R_s \\
 \Rightarrow v_{gs} &= -i_{in} R_s \\
 i_x &= g_m v_{gs} = -g_m i_{in} R_s \\
 i_y &= \frac{v_{in}}{r_o} \\
 \Rightarrow i_{in} &= -g_m i_{in} R_s + \frac{v_{in}}{r_o} \\
 i_{in} (1 + g_m R_s) &= \frac{v_{in}}{r_o} \\
 \Rightarrow z_{in} &= r_o (1 + g_m R_s)
 \end{aligned}$$

(x)

 


Figure 2.2.19: Circuit of 2.2(x)

Grounding the Gate and the Drain terminals, the equivalent small signal circuit for the same will be as Figure 2.2.20

 


Figure 2.2.20: Equivalent Circuit of 2.2(x)

From the equivalent circuit we can see that.

$$\begin{aligned}
 i_{in} &= i_x + i_y \\
 v_g &= 0 \\
 v_s &= v_{in} - i_{in} R_s \\
 \Rightarrow v_{gs} &= i_{in} R_s - v_{in} \\
 i_x &= -g_m v_{gs} = g_m (v_{in} - i_{in} R_s) \\
 i_y &= \frac{v_{in} - i_{in} R_s}{r_o} \\
 \Rightarrow i_{in} &= g_m (v_{in} - i_{in} R_s) + \frac{v_{in} - i_{in} R_s}{r_o} \\
 i_{in} \left( 1 + g_m R_s + \frac{R_s}{r_o} \right) &= v_{in} \left( g_m + \frac{1}{r_o} \right) \\
 \Rightarrow z_{in} &= \frac{1 + g_m R_s + \frac{R_s}{r_o}}{g_m + \frac{1}{r_o}}
 \end{aligned}$$

### 3 LTSpice Simulation

#### 3.1

Plot of  $I_{DS}$  vs  $V_{DS}$  at multiple values of  $V_{GS}$  is given by Figure 3.1.2

Name: Sritharan Vinoth Kumar  
Rno: 2024112022

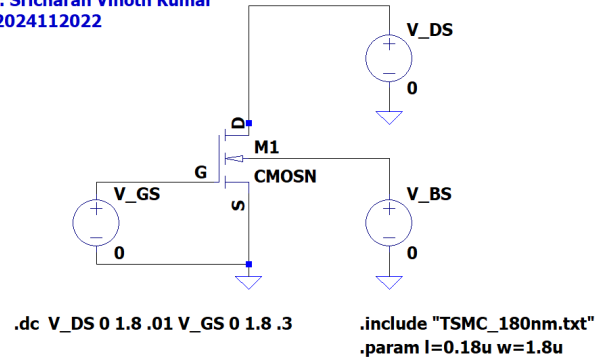


Figure 3.1.1: LTSpice Schematic

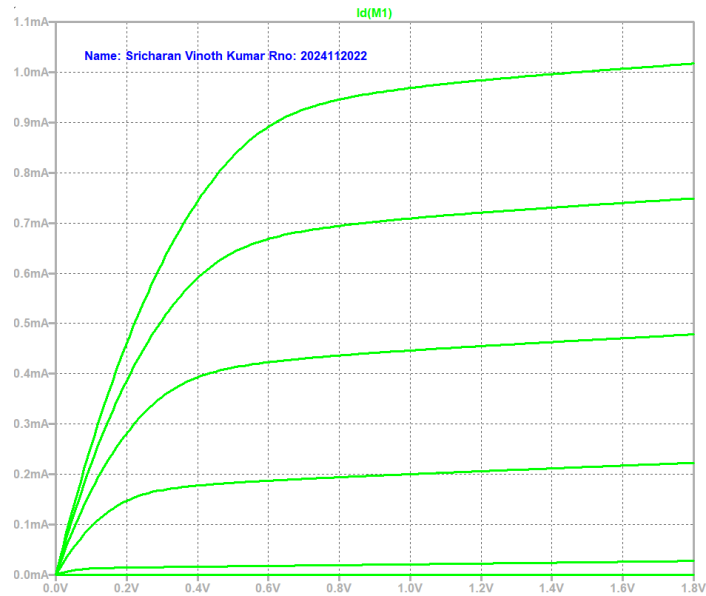


Figure 3.1.2: Plot of  $I_{DS}$  vs  $V_{DS}$ . X axis represents  $V_{DS}$  and Y axis represents  $I_{DS}$ . Each line represents a value of  $V_{GS}$ . Higher the value of  $V_{GS}$ , higher the value of  $I_{DS}$

## 3.2

Name: Sricharan Vinoth Kumar  
Roll No: 2024112022

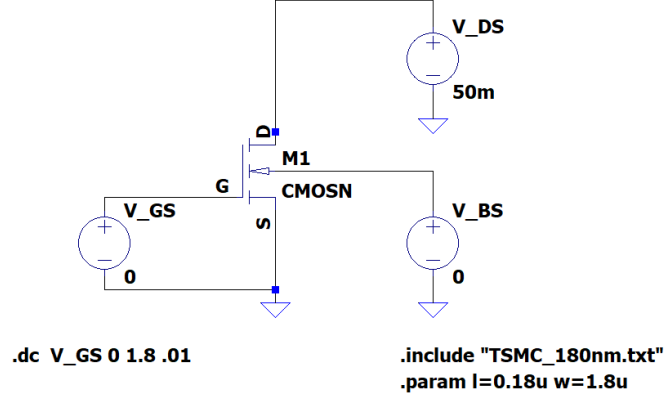


Figure 3.2.1: LTSpice Schematic

For the plot in Figure 3.2.2, the following parameters were used:

- $V_{DS} = 50mV$
- $V_{BS} = 0V$
- $\frac{W}{L} = \frac{1.8u}{0.18u}$

We know that  $V_{TH}$  is the voltage at which the channel is formed and the MOSFET starts conducting. In the context of the plot, it must be the point where the value of  $I_{DS}$  starts to become non-zero. We can approximate that point as  $411.368mV$ , as shown in Figure 3.2.3

To calculate  $\mu_n C_{ox} \frac{W}{L}$ , we take the point of highest slope, given by Figure 3.2.4, which is  $(707.888mV, 25.066\mu A)$

Since  $V_{DS}$  is small, we assume the MOSFET to be in Triode region, Therefore,

$$\begin{aligned}
 I_{DS} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2) \\
 \Rightarrow \mu_n C_{ox} &= \frac{2I_{DS}}{\frac{W}{L} (2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2)} \\
 \Rightarrow \mu_n C_{ox} &= \frac{2 \times 25.066 \times 10^{-6}}{10 \times (2(0.7078 - 0.4113)0.05 - (0.05)^2)}
 \end{aligned}$$

On solving, we get,

$$\mu_n C_{ox} = 0.00018464825 = 184.648 \mu A/V^2$$



 


Figure 3.2.2: Plot of  $I_{DS}$  vs  $V_{GS}$ . X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ .

The obtained value is reasonably close to the actual value (roughly  $240\mu A/V^2$ )

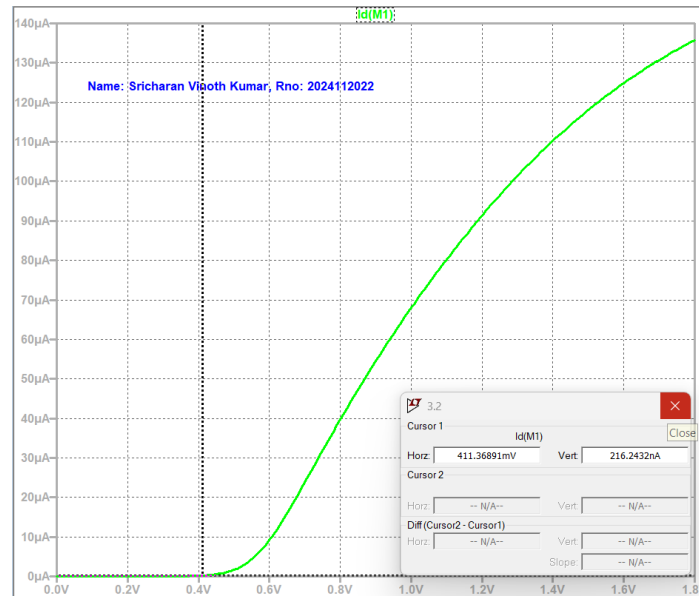


Figure 3.2.3: Plot of  $I_{DS}$  vs  $V_{GS}$  with  $V_{TH}$  approximation. X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ .

 


Figure 3.2.4: Plot of  $I_{DS}$  vs  $V_{GS}$  with point of maximum slope. X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ .

For  $V_{DS} = 1.8V$ , we get the plot shown in Figure 3.2.5

 


Figure 3.2.5: Plot of  $I_{DS}$  vs  $V_{GS}$  at  $V_{DS} = 1.8V$ . X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ .

To find  $V_{TH}$ , using the same logic as before, i.e, find the point at which  $I_{DS}$  starts becoming non-zero, we get  $V_{TH} = 369.605mV$ , as per Figure 3.2.6

*Note: That specific point was chosen since it had a similar current value to the point considered for  $V_{TH}$  in the  $V_{DS} = 50mV$  case, (approximately  $220nA$ ), for the sake of uniformity.*

We see that  $V_{TH}$  has decreased, when compared to the  $V_{DS} = 50mV$  case. This can be attributed to the phenomena of Drain-Induced Barrier Lowering.

#### Drain-Induced Barrier Lowering:

When drain voltage increases, the threshold voltage for channel formation decreases, enabling channel formation at an earlier stage of  $V_{GS}$ . This occurs because a high drain voltage attracts charge carriers towards the Channel region, increasing charge density and making it easier to form the channel, which explains our observations.

 


Figure 3.2.6: Plot of  $I_{DS}$  vs  $V_{GS}$  at  $V_{DS} = 1.8V$ , with  $V_{TH}$  approximation. X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ .

### 3.3

For NMOS, taking  $V_{DS} = 1V$ ,

Name: Sricharan Vinoth Kumar  
Roll No: 2024112022

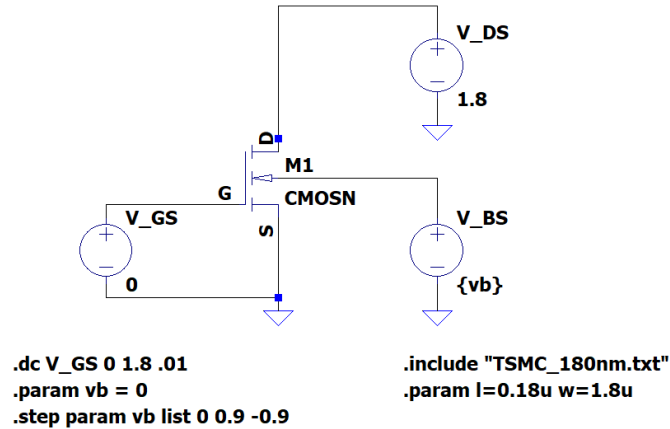


Figure 3.3.1: LTSpice Schematic

If we plot  $I_{DS}$  vs  $V_{GS}$  for different values of  $V_{BS}$ , we get the plot obtained in Figure 3.3.2

In the previous question, we took  $V_{TH}$  as the point in the plot where  $I_{DS}$  starts becoming non zero. Applying the same logic here, we get  $V_{TH}$  values as,

- (a)  $V_{TH} = 453.13225mV$  at  $V_{BS} = 0V$
- (b)  $V_{TH} = 311.13689mV$  at  $V_{BS} = 0.9V$
- (c)  $V_{TH} = 659.86079mV$  at  $V_{BS} = -0.9V$

from Figure 3.3.3.

*Note: These points was chosen such that they had similar corresponding current values (approximately  $1.9\mu A$ ), for the sake of uniformity.*

**We see that  $V_{TH}$  decreases with increase in  $V_{BS}$**

 


Figure 3.3.2: Plot of  $I_{DS}$  vs  $V_{GS}$  at different values of  $V_{BS}$  mentioned in the plot. X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ .

 


Figure 3.3.3: Plot of  $I_{DS}$  vs  $V_{GS}$  at different values of  $V_{BS}$  mentioned in the plot, with  $V_{TH}$  Measurement. X axis represents  $V_{GS}$  and Y axis represents  $I_{DS}$ . (Top Image, for  $V_{BS} = 0V$  and  $V_{BS} = -0.9V$ , Bottom Image for  $V_{BS} = -0.9V$ )

For PMOS, taking  $V_{SD} = 1V$ ,

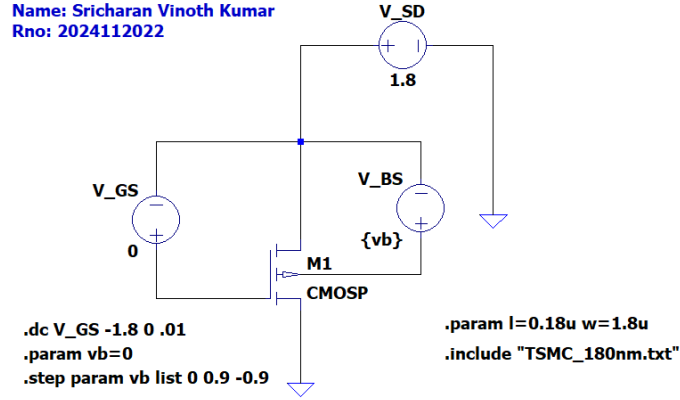


Figure 3.3.4: LTSpice Schematic

If we plot  $I_{DS}$  vs  $V_{GS}$  for different values of  $V_{BS}$ , we get the plot obtained in Figure 3.3.5

 


Figure 3.3.5: Plot of  $I_{SD}$  vs  $V_{GS}$  at different values of  $V_{BS}$  mentioned in the plot. X axis represents  $V_{GS}$  and Y axis represents  $I_{SD}$ .

*Note: In 3.3.5, we are plotting  $I_{SD}$ , since  $I_{DS}$  is negative. So we are using the negative of  $I_{DS}$  within LTSpice to find  $I_{SD}$ , hence the negative sign in the plot label.*

We are taking  $V_{TH}$  as the point in the plot where  $I_{DS}$  starts becoming zero. We get the values as,



- (a)  $V_{TH} = -505.00582mV$  at  $V_{BS} = 0V$   
 (b)  $V_{TH} = -733.41094mV$  at  $V_{BS} = 0.9V$   
 (c)  $V_{TH} = -331.08265mV$  at  $V_{BS} = -0.9V$

from Figure 3.3.6.

*Note: These points was chosen such that they had similar corresponding current values (approximately  $1.9\mu A$ ), for the sake of uniformity.*

**We see that  $V_{TH}$  decreases with increase in  $V_{BS}$  and  $|V_{TH}|$  increases with increase in  $V_{BS}$**

The 2 results obtained, from NMOS and PMOS, can be summarized as:

$V_{TH}$  decreases with increase in  $V_{BS}$

This result can be attributed to body effect.

#### Body Effect:

An increase in  $V_{BS}$  causes  $V_{TH}$  to fall. This phenomena is expressed mathematically by the equation,

$$\begin{aligned} V_{th} &= V_{th0} + \gamma \left( \sqrt{V_{SB} + \phi_f} - \sqrt{\phi_f} \right), \text{ for NMOS} \\ V_{th} &= V_{th0} + \gamma \left( \sqrt{|V_{SB} + \phi_f|} - \sqrt{\phi_f} \right), \text{ for PMOS} \end{aligned} \quad (3.3.1)$$

Where,

- $V_{th}$  = Threshold Voltage
- $V_{th0}$  = Threshold voltage when  $V_{SB} = 0$ .
- $\gamma$  = Body effect coefficient.
- $\phi_f$  = Fermi potential.
- $V_{SB} = V_S - V_B$  (Source-to-Bulk voltage).

From the equation we see that  $V_{th} \propto \sqrt{V_{SB}}$  approximately, which explains our observations.

 


Figure 3.3.6: Plot of  $I_{SD}$  vs  $V_{GS}$  at different values of  $V_{BS}$  mentioned in the plot, with  $V_{TH}$  Measurement. X axis represents  $V_{GS}$  and Y axis represents  $I_{SD}$ . (Top Image, for  $V_{BS} = 0V$  and  $V_{BS} = -0.9V$ , Bottom Image for  $V_{BS} = 0.9V$ )