
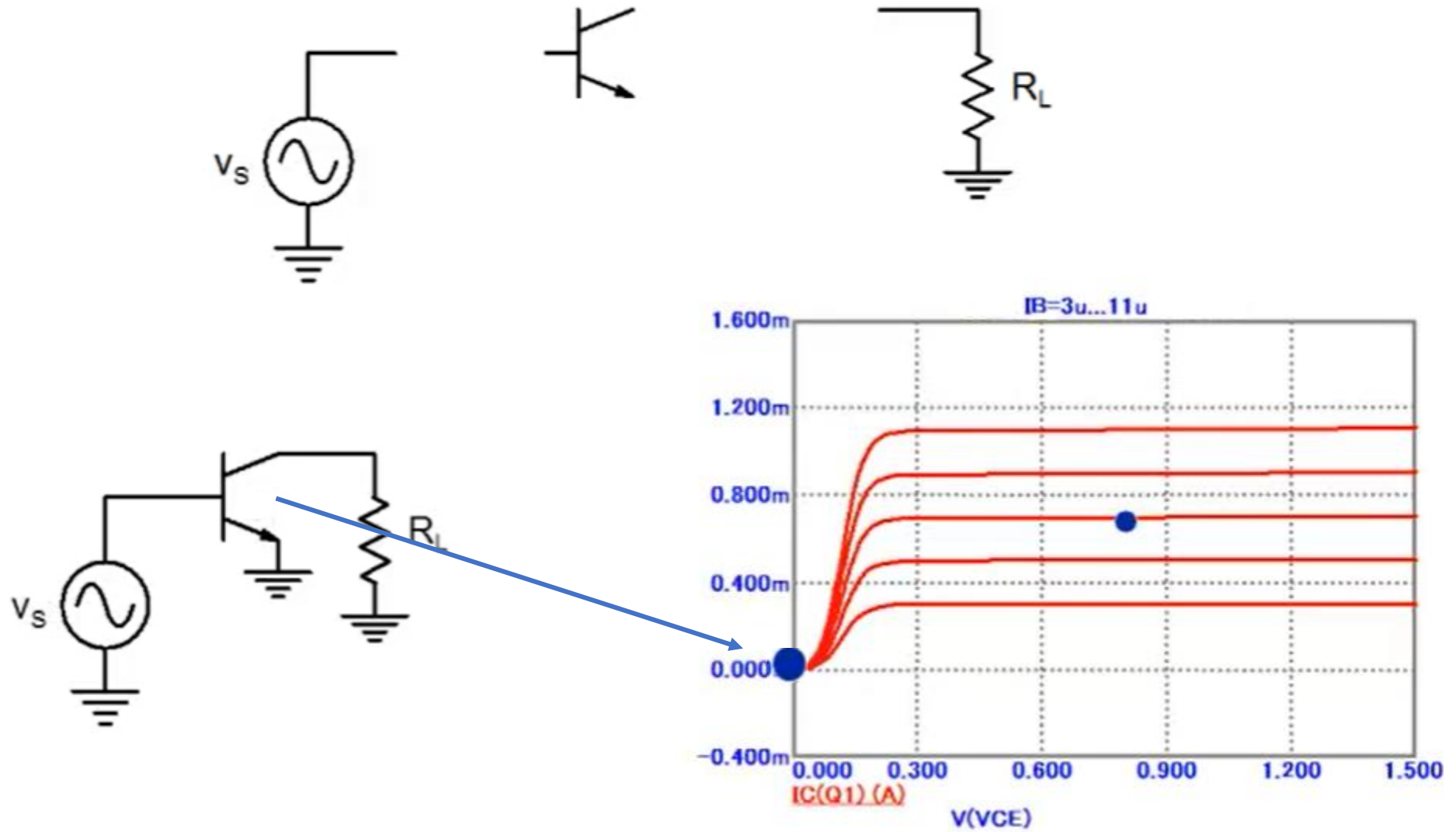


BJT Amplifier Biasing


Biasing

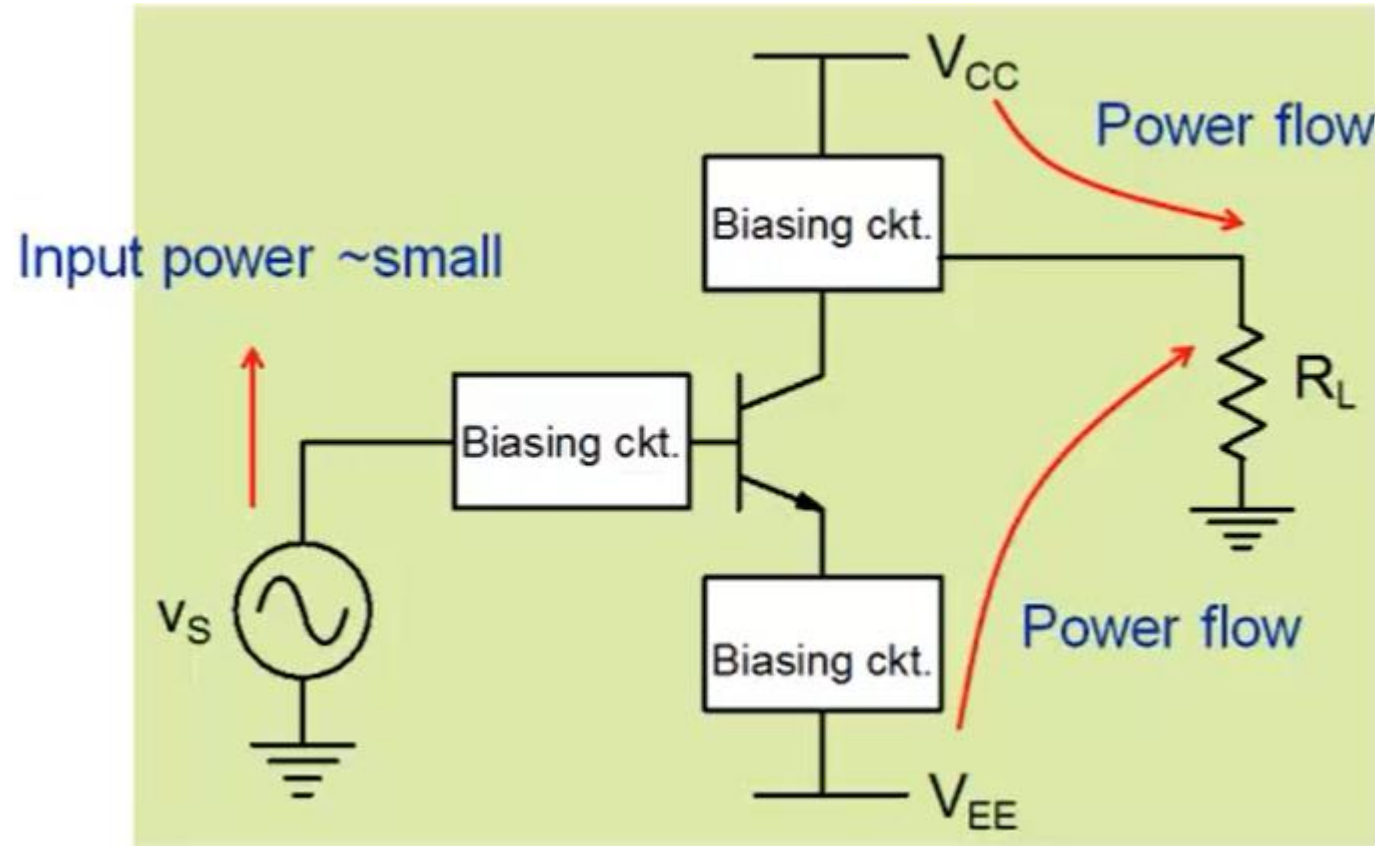




Good Biasing circuit: Bias point is stable against variations in temperature, current gain β , supply voltage etc, power efficient, low cost

Variations to watch out for

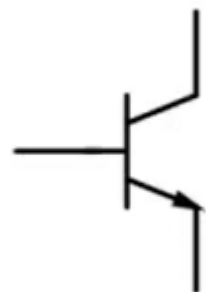


(1)
$$\frac{dV_{BE}}{dT} \cong -2mV/^{\circ}C$$


(2)

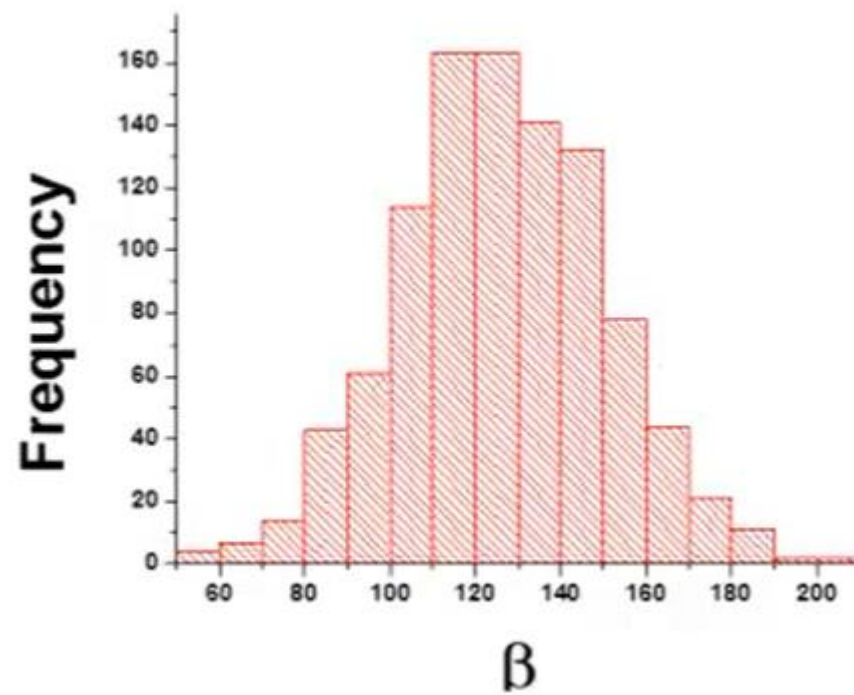

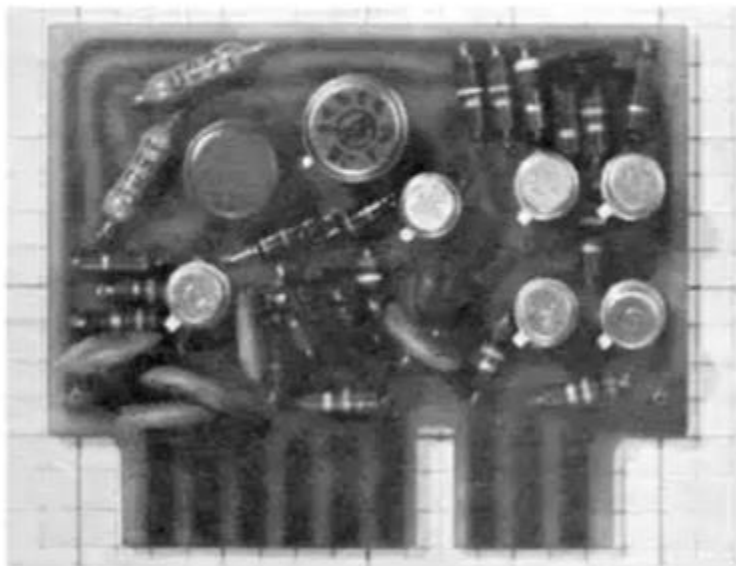Different biasing circuit for discrete and monolithic (IC) circuit implementation



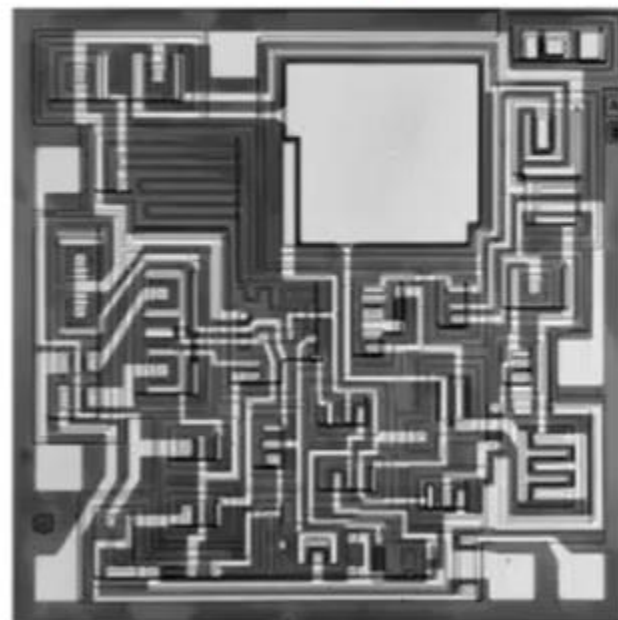
Resistors and capacitors are 'cheap' and transistors are relatively more expensive.



Higher value resistors ($M\Omega$) are expensive and capacitors in pF range only are possible. Passive components are expensive, while transistors are cheap !







A good biasing circuit for discrete implementation

Bias circuit has 4R, 3C, 0Tr.

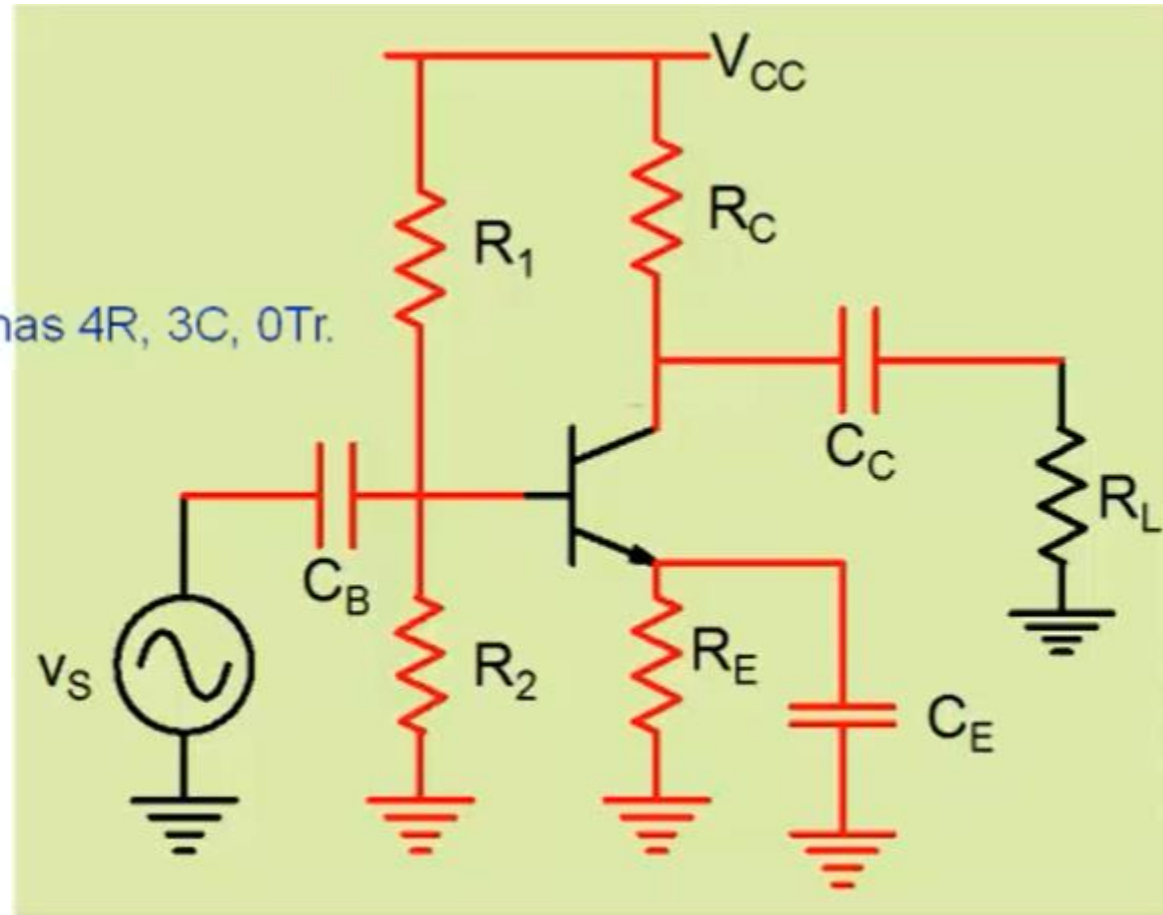


Every Circuit is a solution to one or more set of problems !

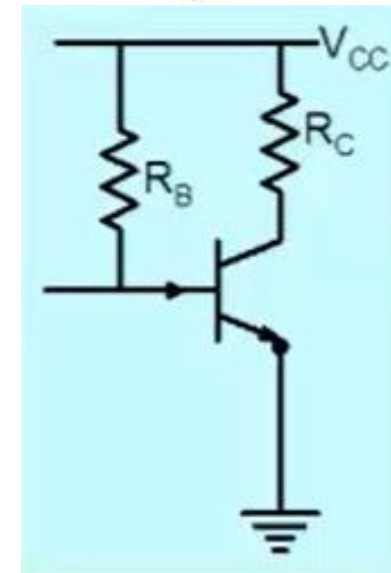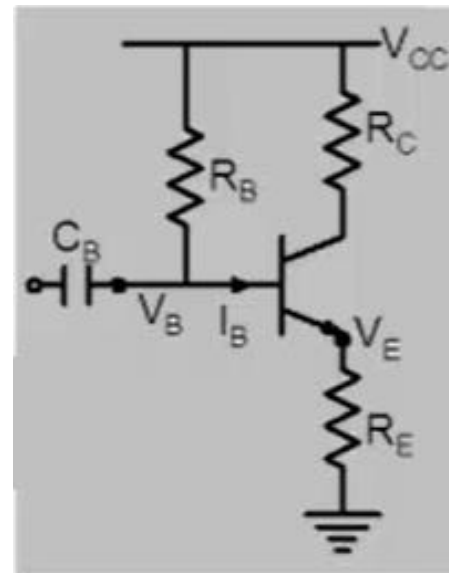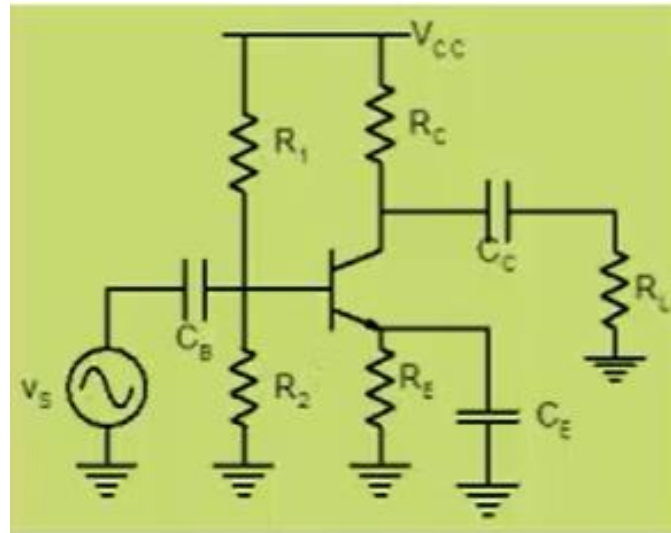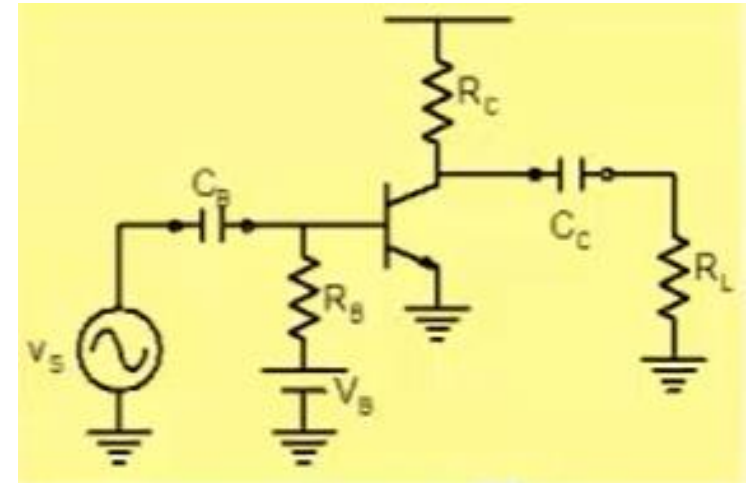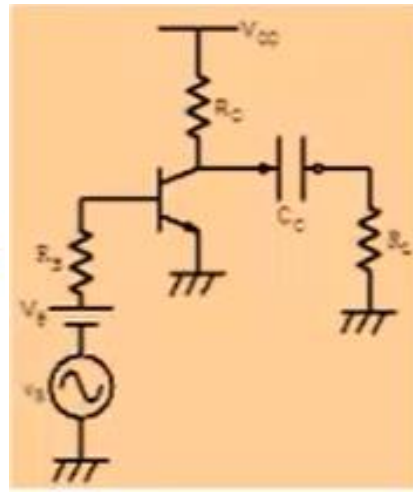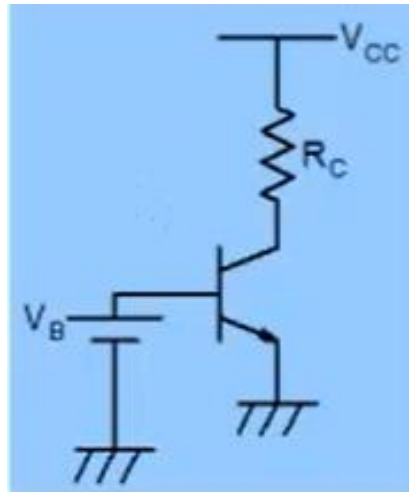
Evolution of circuit from simple to complex



BJT amp-1

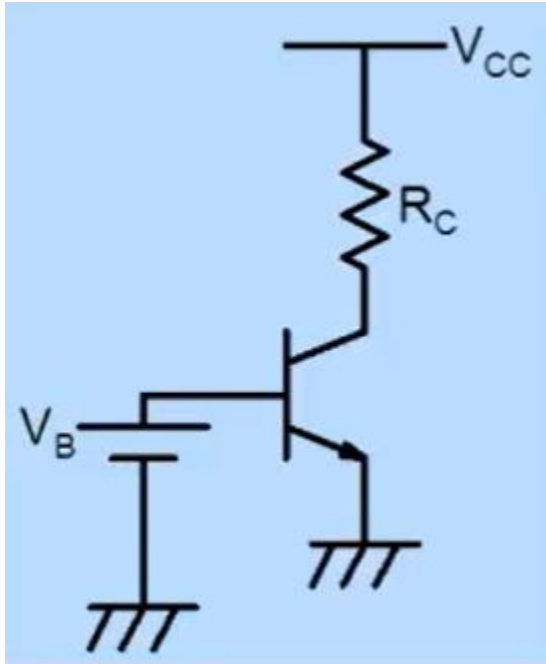

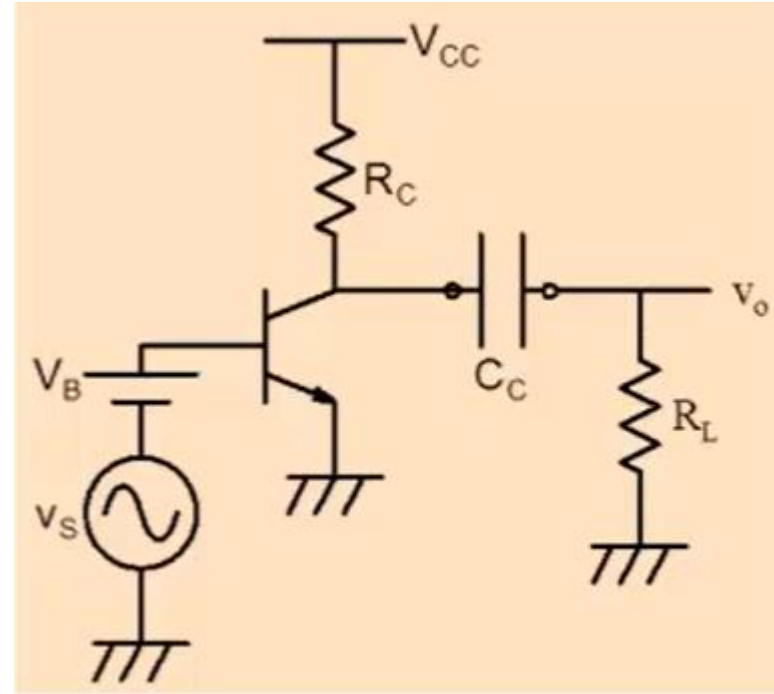Bias the Transistor in Forward Active Mode



Apply the signal at the base and Connect the load


$$I_C \cong I_S \times \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$\Delta I_C \cong I_S \times \exp\left(\frac{V_{BE}}{V_T}\right) \times \frac{\Delta V_{BE}}{V_T}$$

$$\left(\frac{\Delta I_C}{I_C}\right) = \left(\frac{\Delta V_B}{V_B}\right) \times \left(\frac{V_{BE}}{V_T}\right)$$

Biassing is very sensitive to the biasing voltage and temperature

BJT amp-2

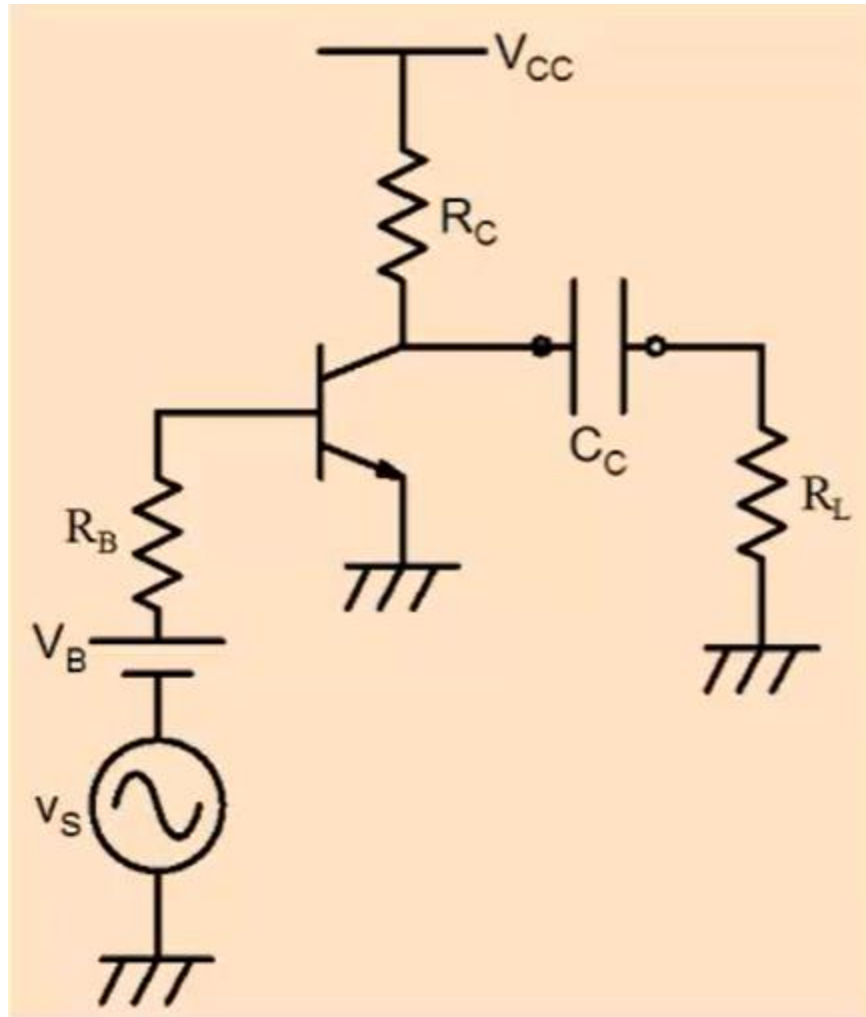

$$I_B = \frac{V_B - V_{BE}}{R_B}$$

$$I_C = \beta \times I_B$$

$$\frac{\Delta I_C}{I_C} = \frac{-\Delta V_{BE} + \Delta V_B}{V_B - V_{BE}}$$


$$\frac{dV_{BE}}{dT} = -2\text{mV}/^\circ\text{C}$$

$$\Delta V_{BE} = 100\text{ mV}$$


$$V_B - V_{BE} \gg 100\text{ mV}$$

$$V_B - V_{BE} = I_B R_B \geq 1\text{ Volt}$$

Why use a capacitor at the output?

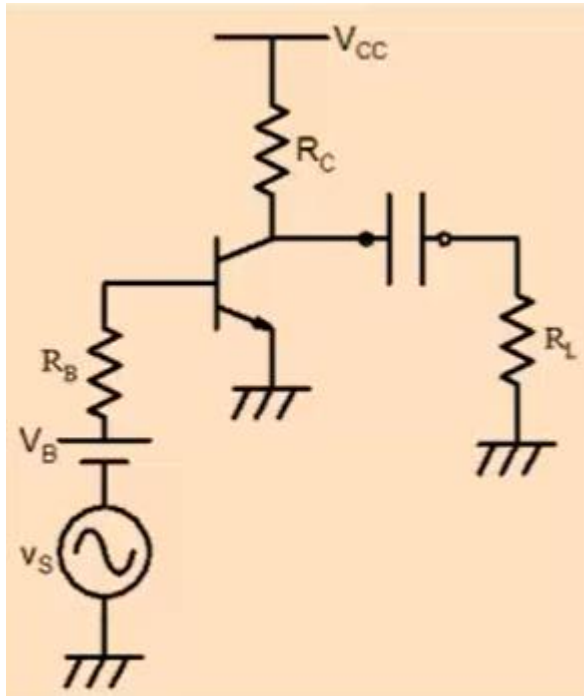


$$V_{CE} = V_{CC} - I_C R_C$$

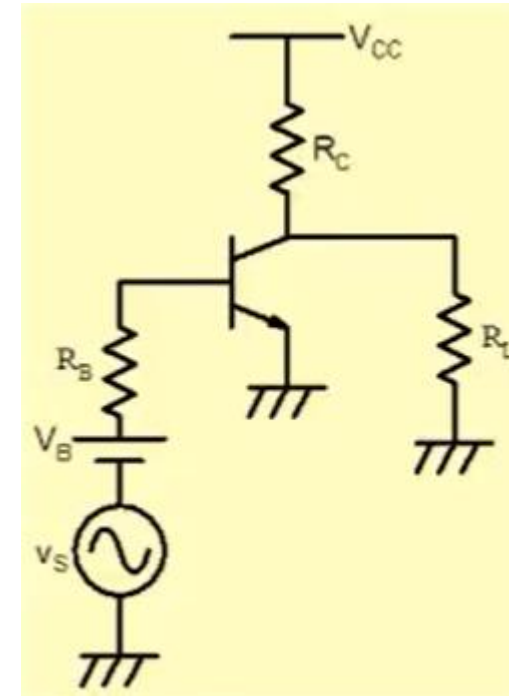

$$V_{CE} = \frac{V_{CC} - I_C R_C}{1 + R_C / R_L}$$

It may become difficult to obtain the desired value of V_{CE} and bias point becomes load dependent.

Example-1

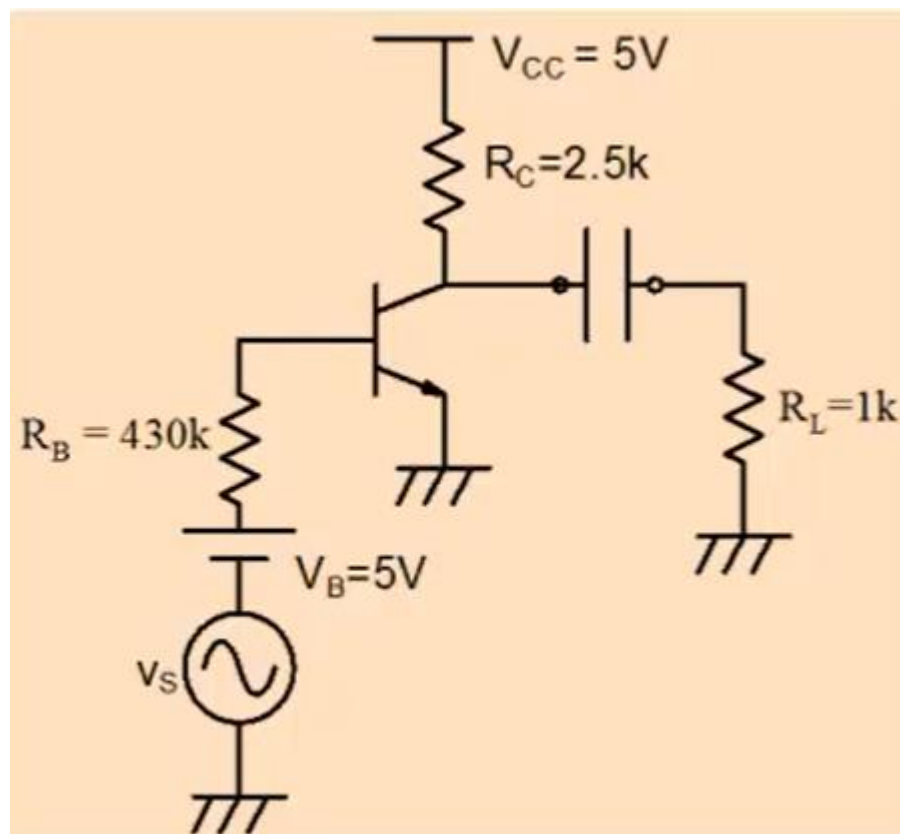

Bias or quiescent (Q) Point :

$$I_{CQ} = 1mA; \quad V_{CEQ} = 2.5V$$

Design:


$$I_B = \frac{V_B - V_{BE}}{R_B}; \quad I_C = \beta \times I_B$$

$$V_{CE} = V_{CC} - I_C \times R_C$$


$$I_B R_B > 1V$$





$$R_B = 430k\Omega; \quad R_C = 2.5k\Omega$$

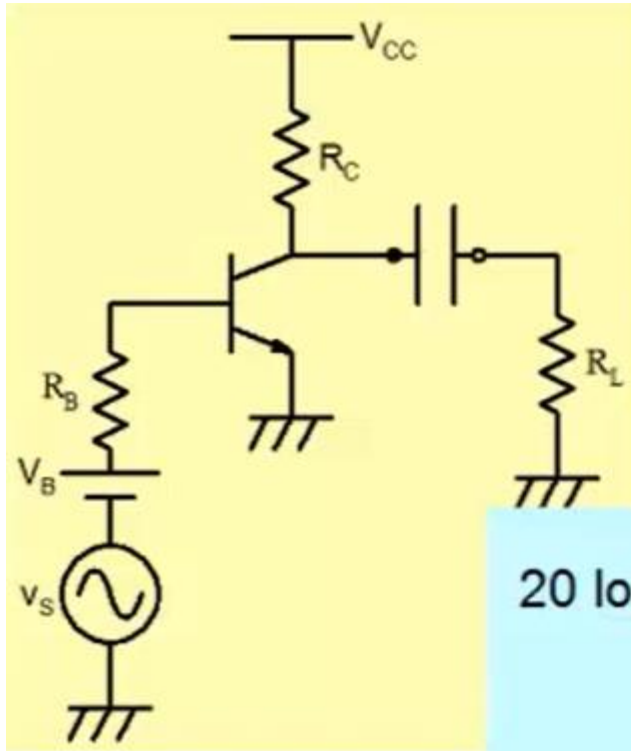Small Signal Analysis (Mid Frequency Range)




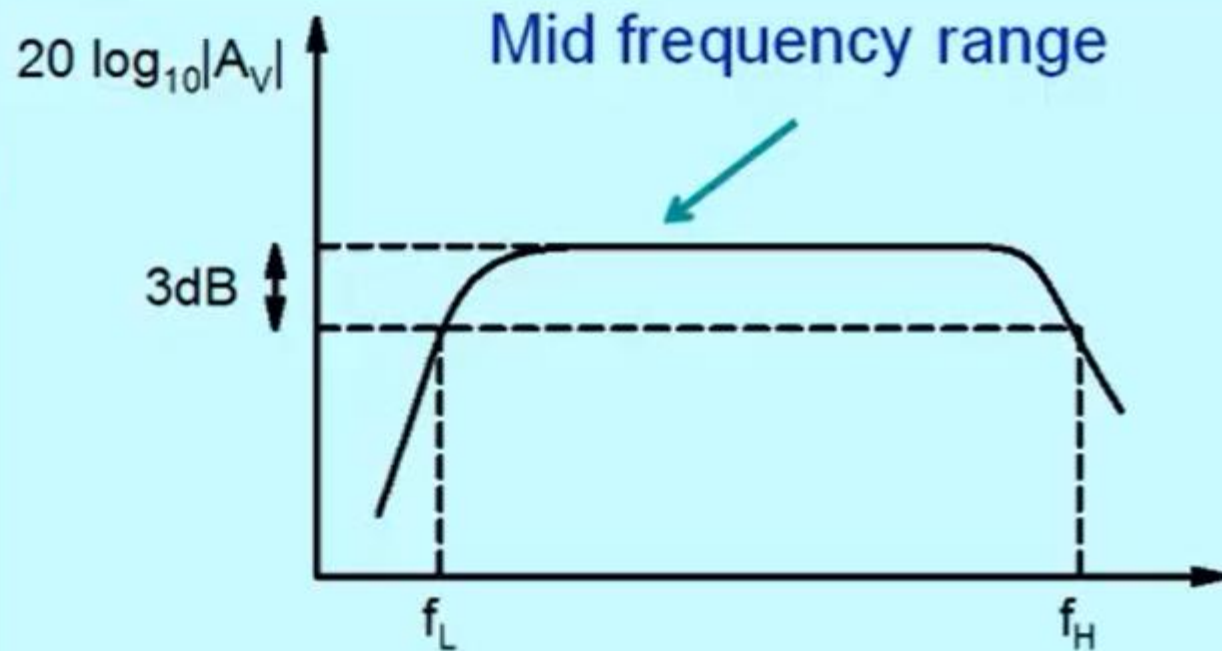Frequency is high enough for all coupling capacitors to be assumed as short but low enough for all internal transistor capacitances to be considered as open.



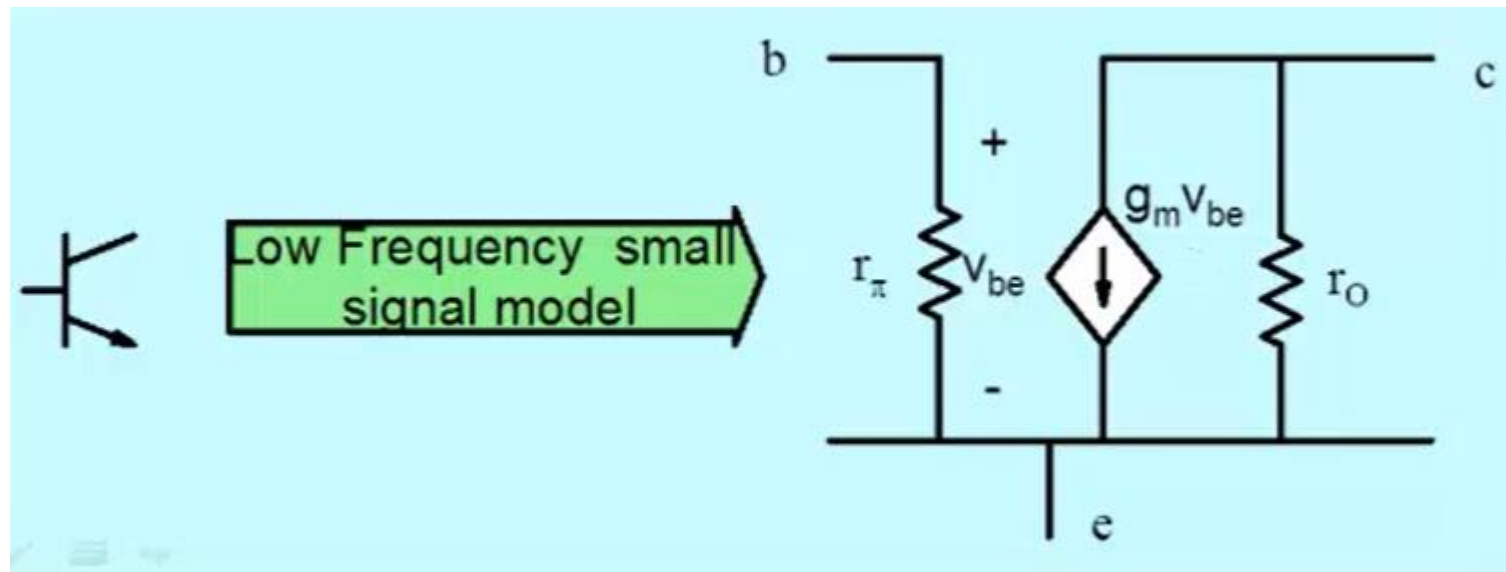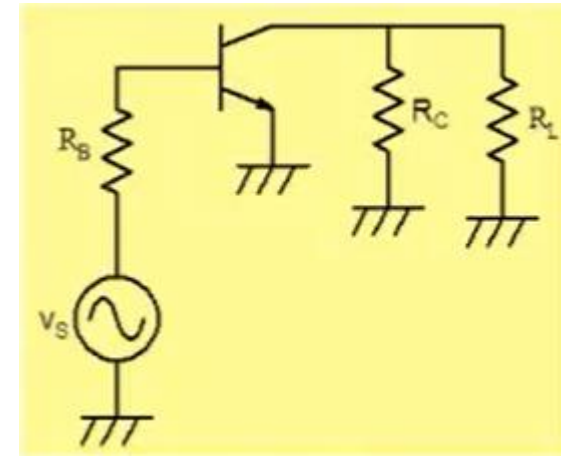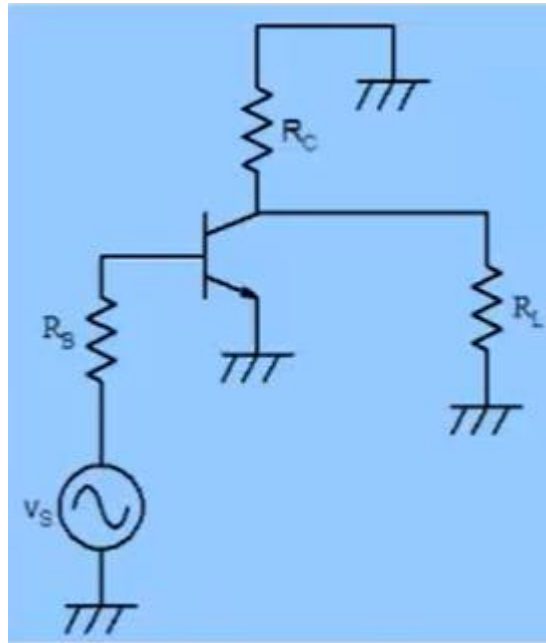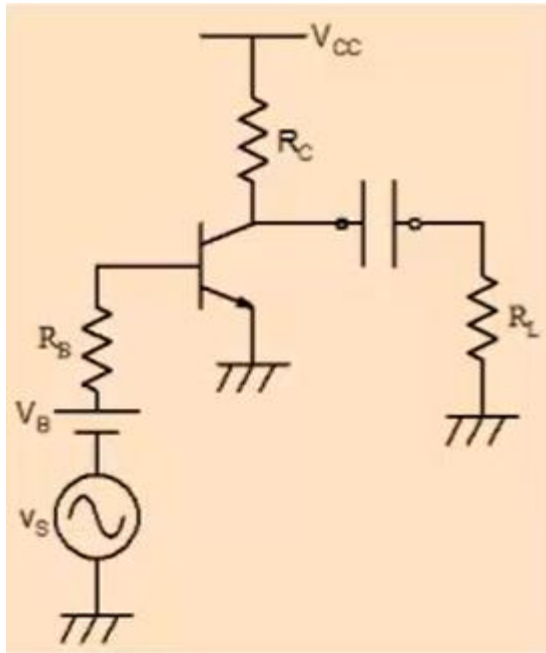

Small Signal Analysis

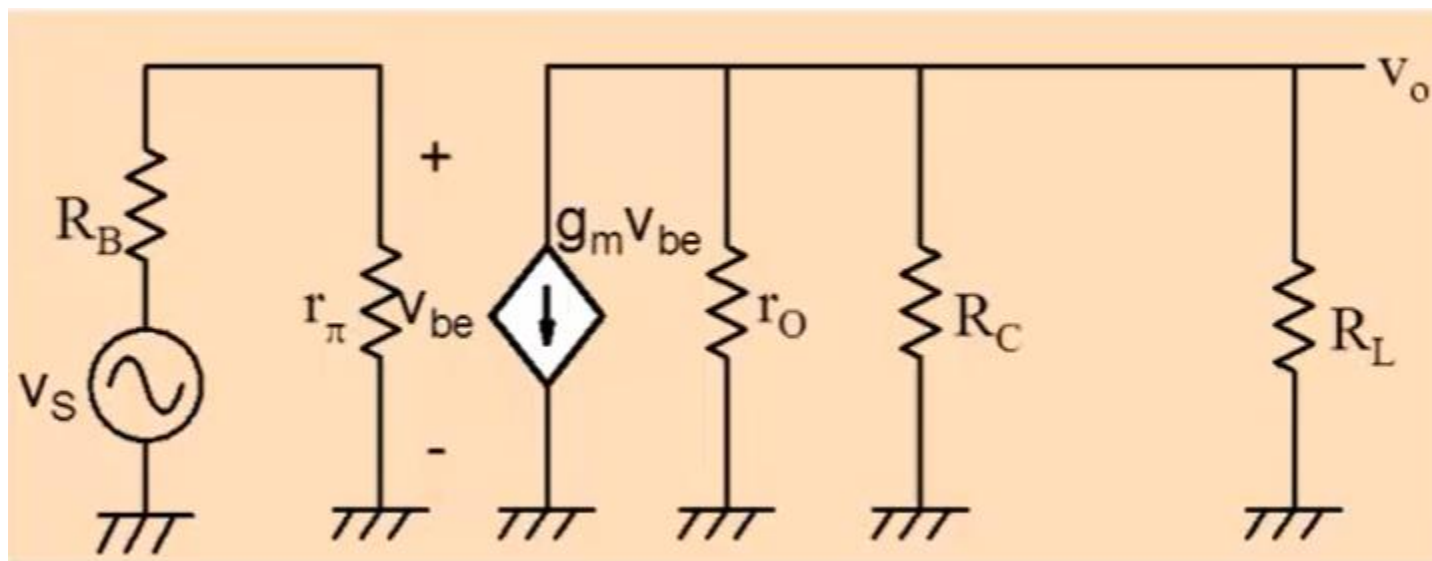


$$v_{be} = \frac{r_\pi}{r_\pi + R_B} v_s$$

$$v_o = - g_m v_{be} \times (r_o \parallel R_C \parallel R_L)$$

$$A_v = - \left(\frac{r_\pi}{r_\pi + R_B} \right) g_m \times (r_o \parallel R_C \parallel R_L)$$

Example-1

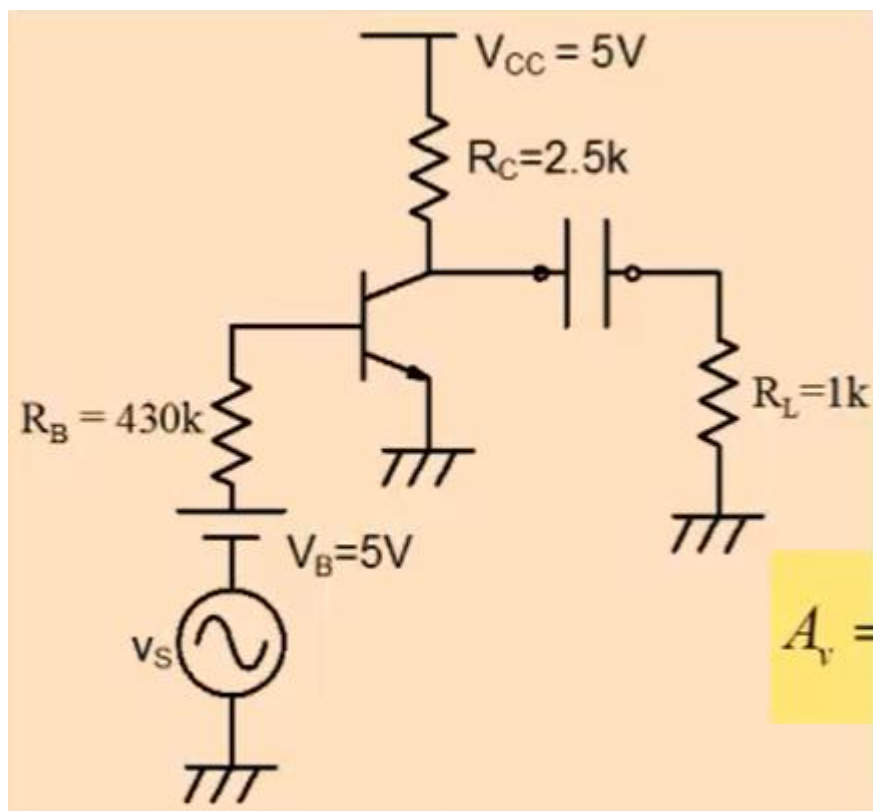


$$I_{CQ} = 1mA; \quad V_{CEQ} = 2.5V$$

$$g_m = 38mS; \quad r_\pi = 2.6k\Omega; \quad r_o = 100k\Omega$$

$$A_v = - \left(\frac{r_\pi}{r_\pi + R_B} \right) \{ g_m \times (r_o \parallel R_C \parallel R_L) \}$$

$$A_v = (6 \times 10^{-3}) \times 27.2 = 0.164$$

Problem


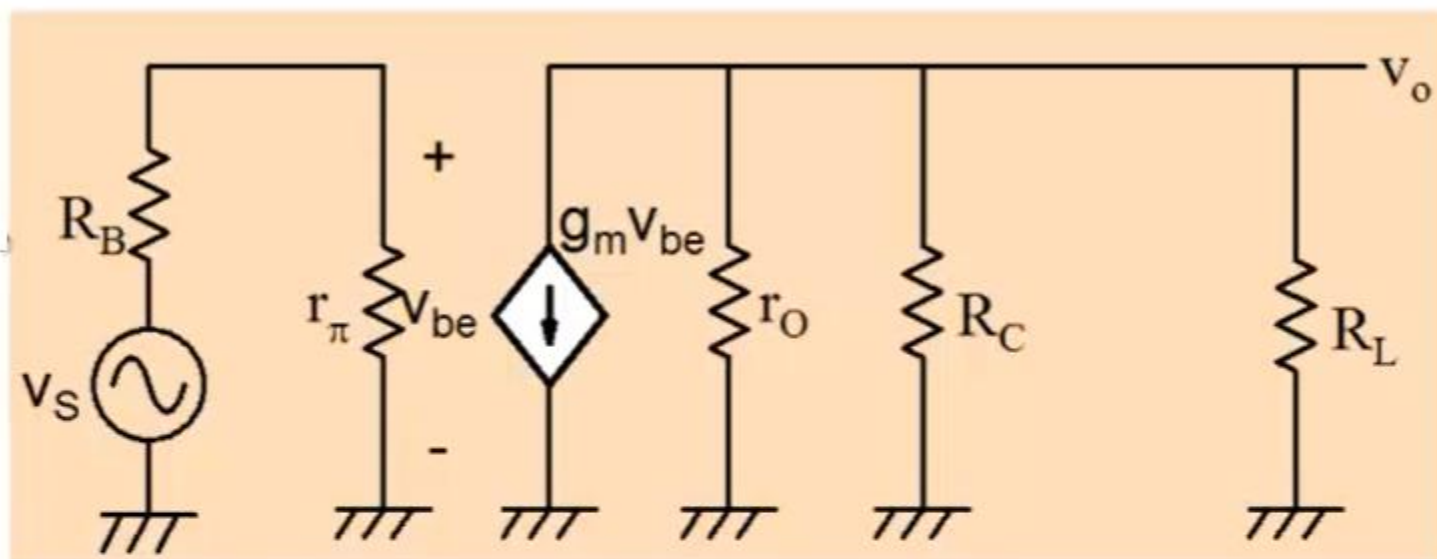


$$A_V \cong \left(\frac{r_\pi}{r_\pi + R_B} \right) g_m R_L$$

$$\left(\frac{r_\pi}{r_\pi + R_B} \right) = \frac{V_T / I_B}{(V_T / I_B) + R_B} = \frac{V_T}{V_T + I_B R_B}$$

A large fraction of input gets dropped across R_B



Another Problem

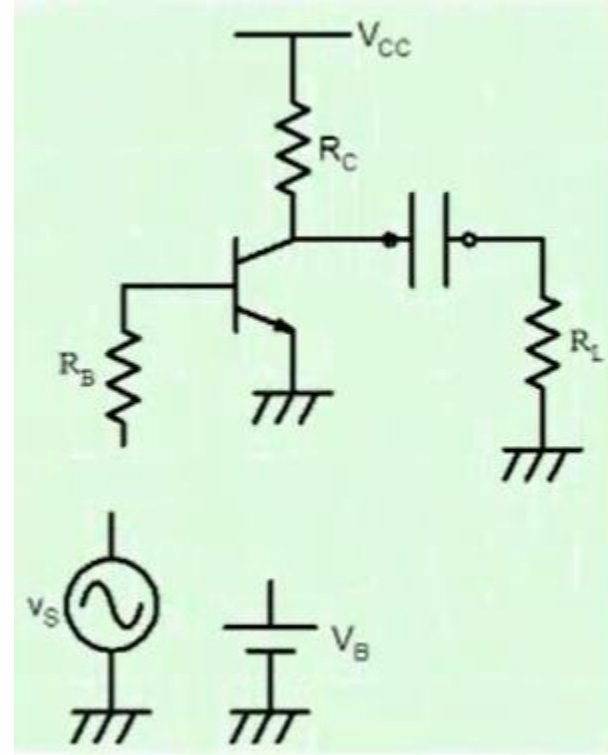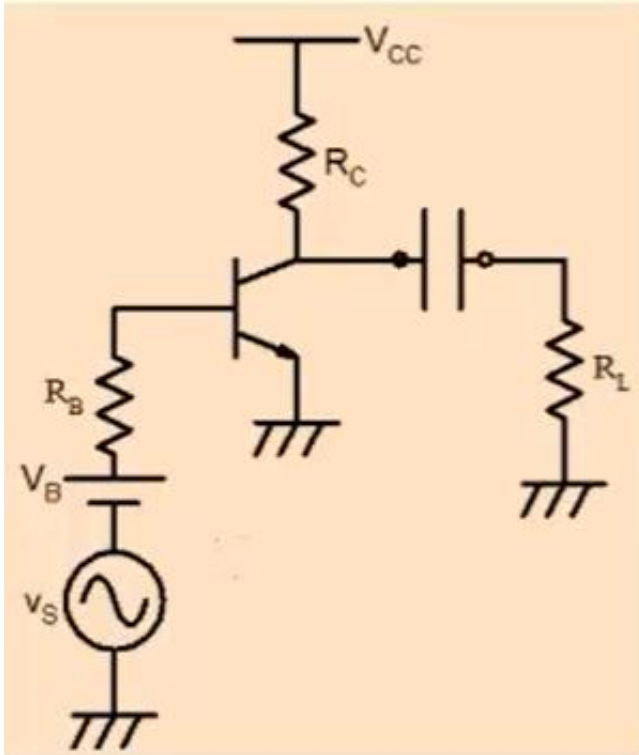



How do we connect v_S and V_B in series when one terminal of both is ground?

Solution

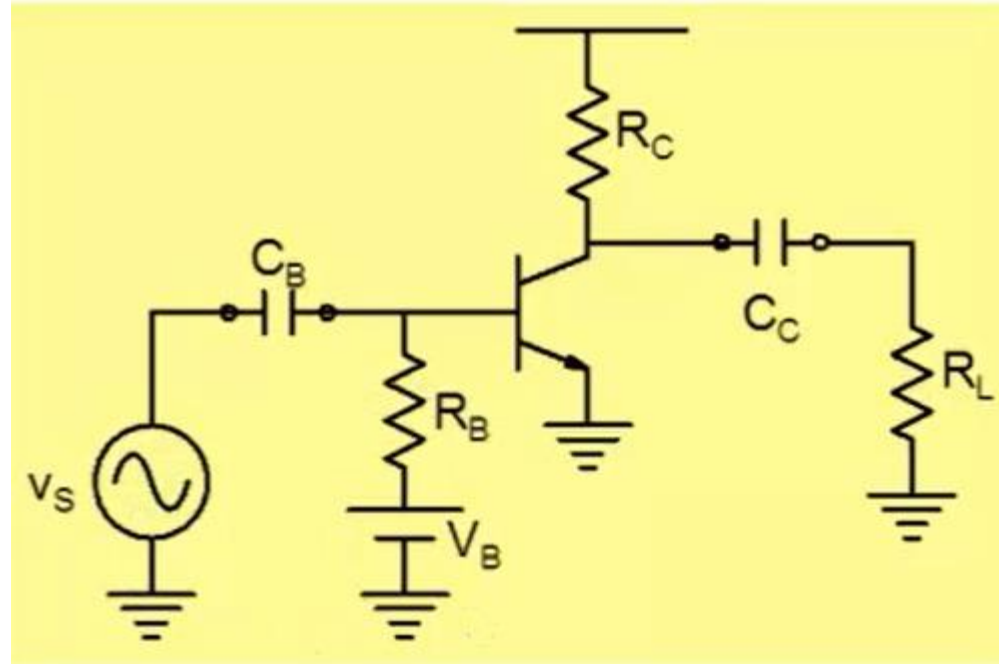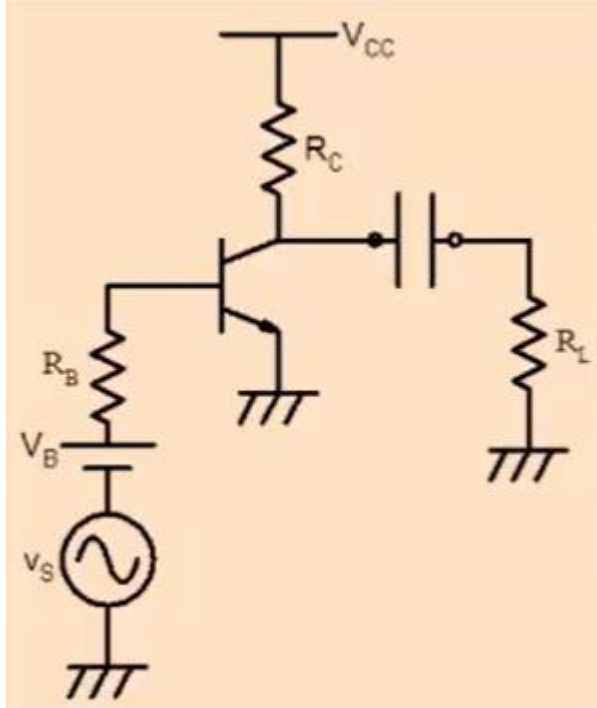Bypass resistance R_B from the path of the input signal



Small Signal Model

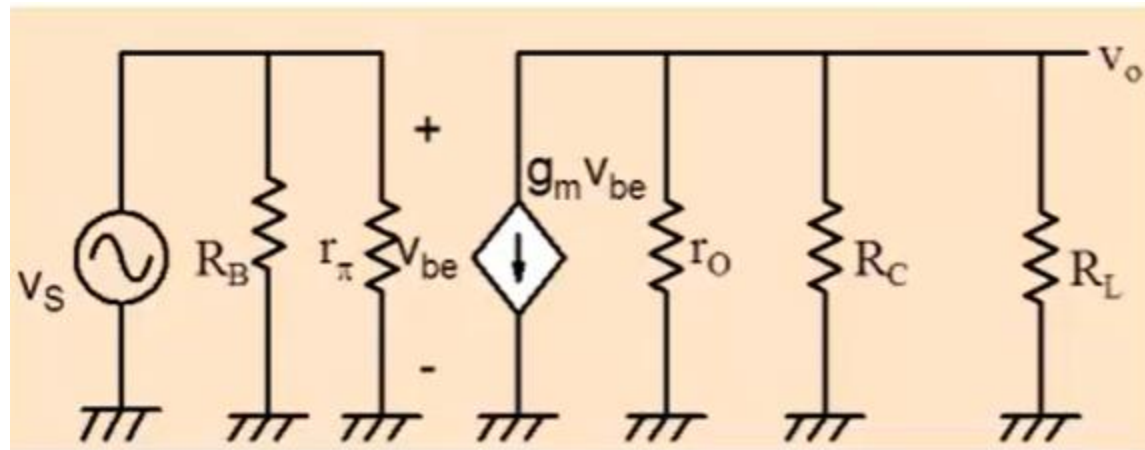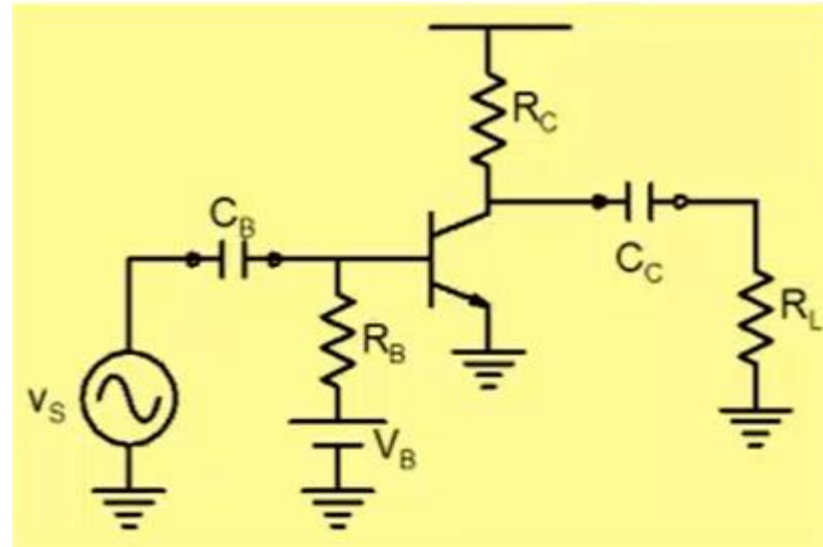

$$A_v = -g_m \times r_o \parallel R_C \parallel R_L$$

$$\cong -g_m \times R_C \parallel R_L$$

$$g_m \times R_C = \frac{I_C \times R_C}{V_T}$$