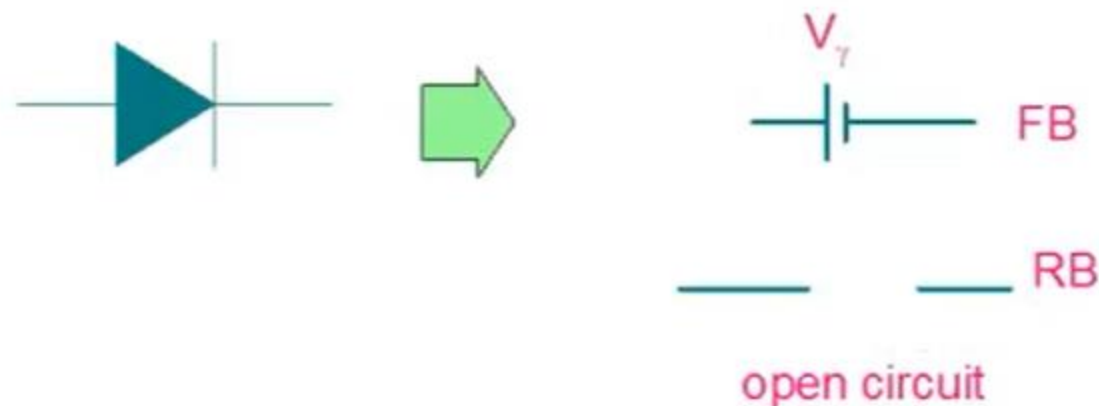



**For hand analysis of circuits, we need
simpler models!**

- Analysis using a **non-linear** diode model is relatively difficult and time consuming.
- It also does not give a symbolic expression that can provide insight and help in the design of the circuit.

Need **SIMPLER** and **LINEAR** Device Models



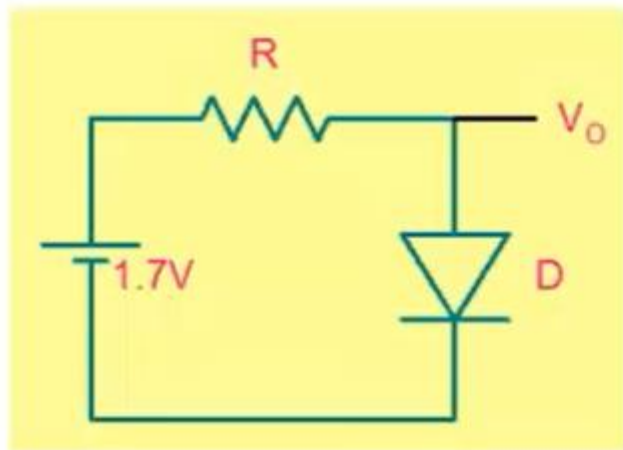What should we take as diode drop?.....0.7V?



$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$


$$I_S = 2 \times 10^{-15} \text{ A}$$


$$V_T = kT / q \cong 26 \text{ mV} \text{ at } T = 300\text{K}$$

$$R: 10\Omega \rightarrow 1M\Omega$$

Simple 0.7V model would predict:


$$I = \frac{1}{R}$$

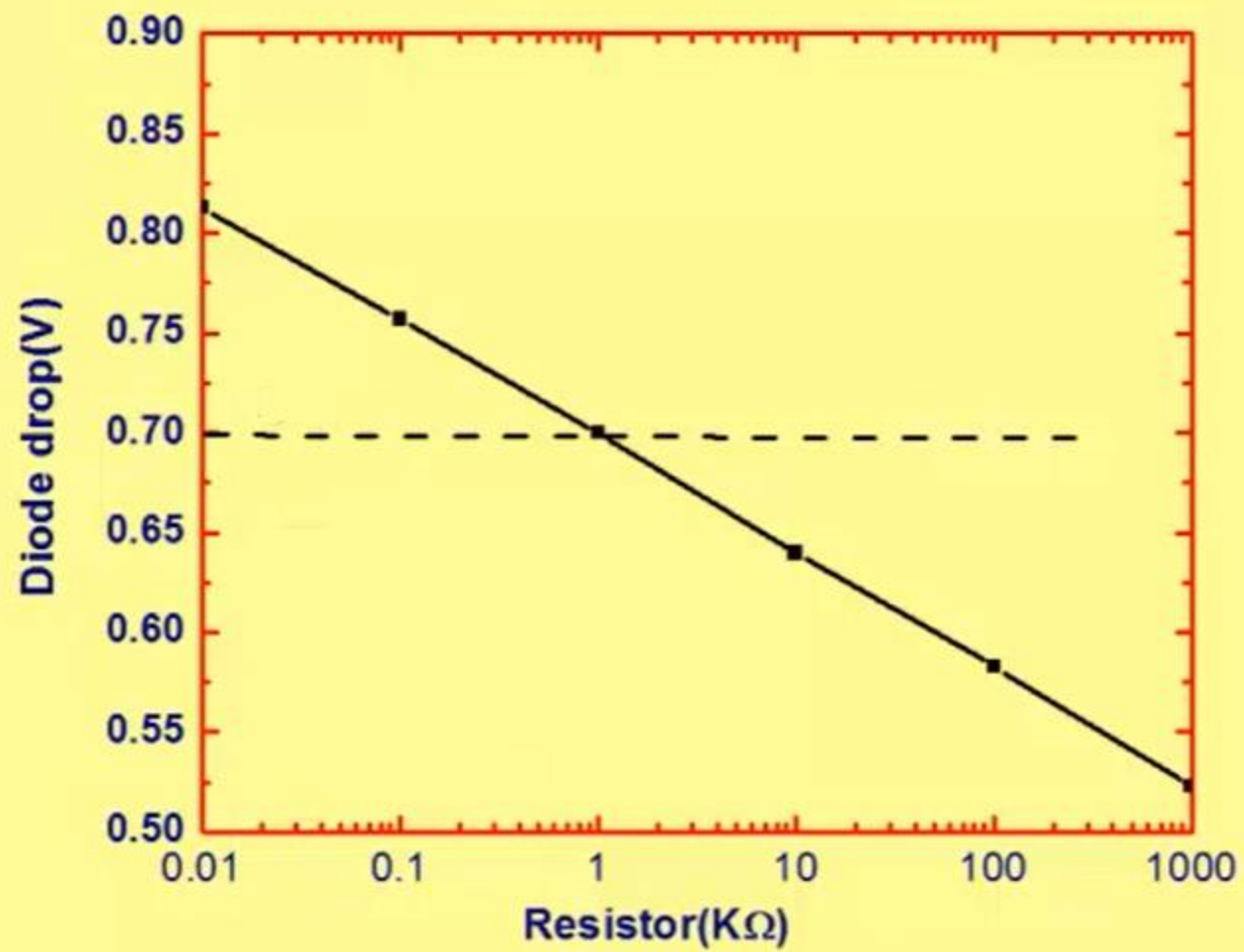

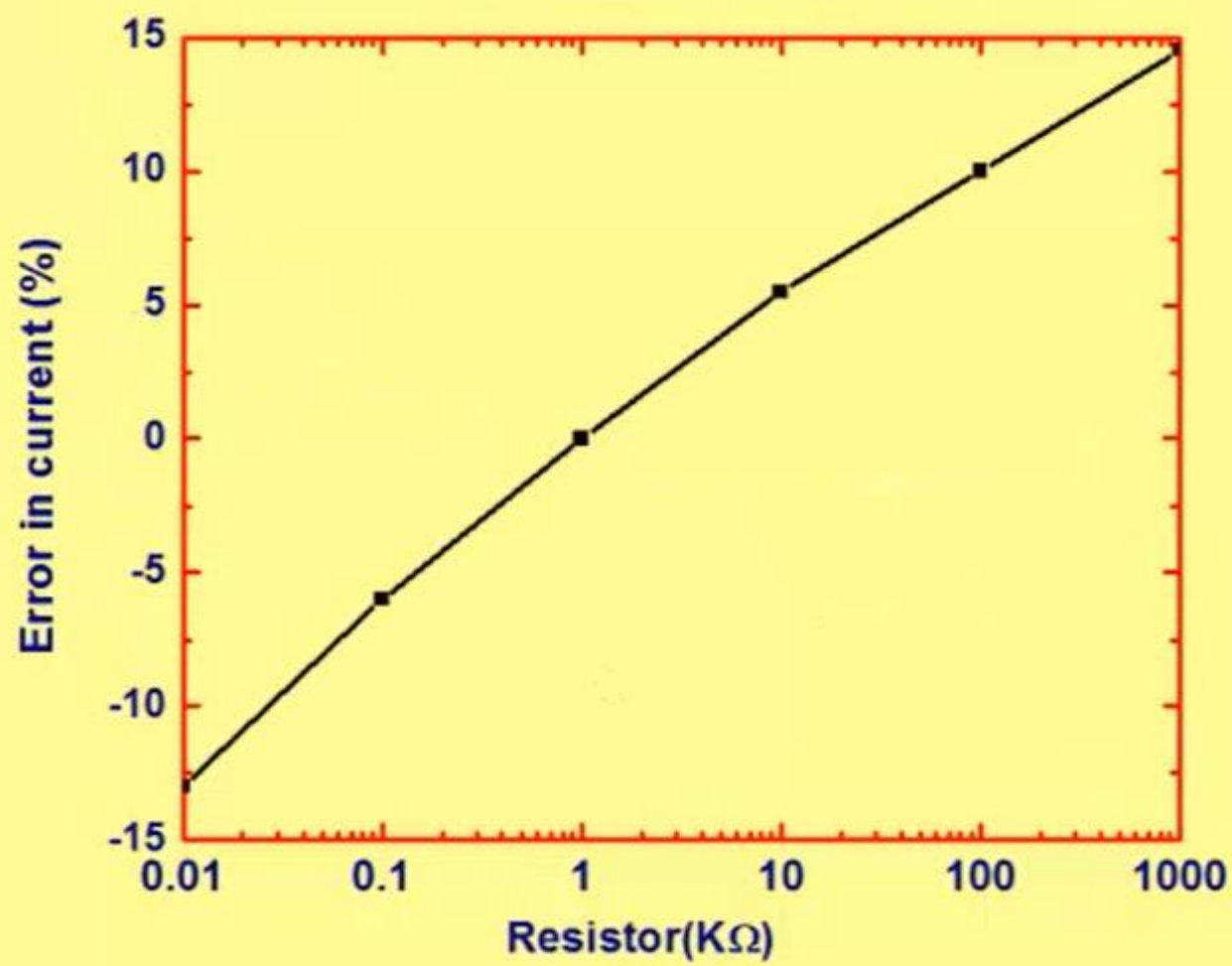


(100mA - 1 μ A)

Different Diode: ~1N4148

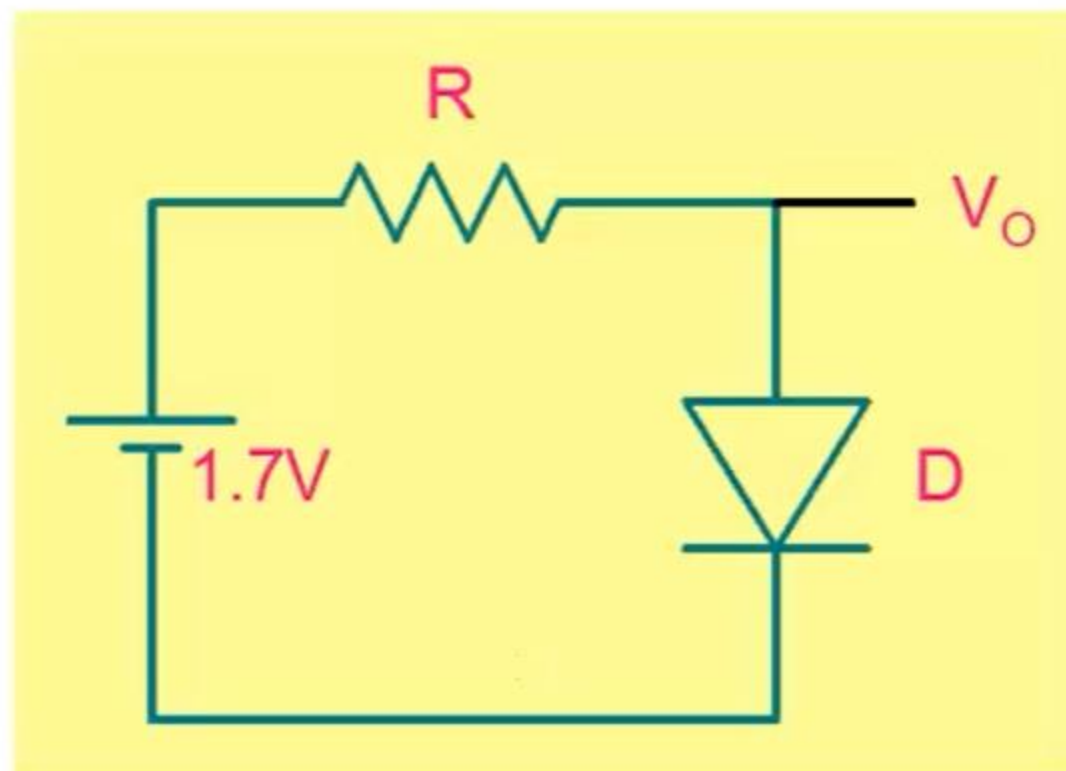


$$I = I_S \times \left\{ \exp\left(\frac{V}{nV_T} \right) - 1 \right\}$$
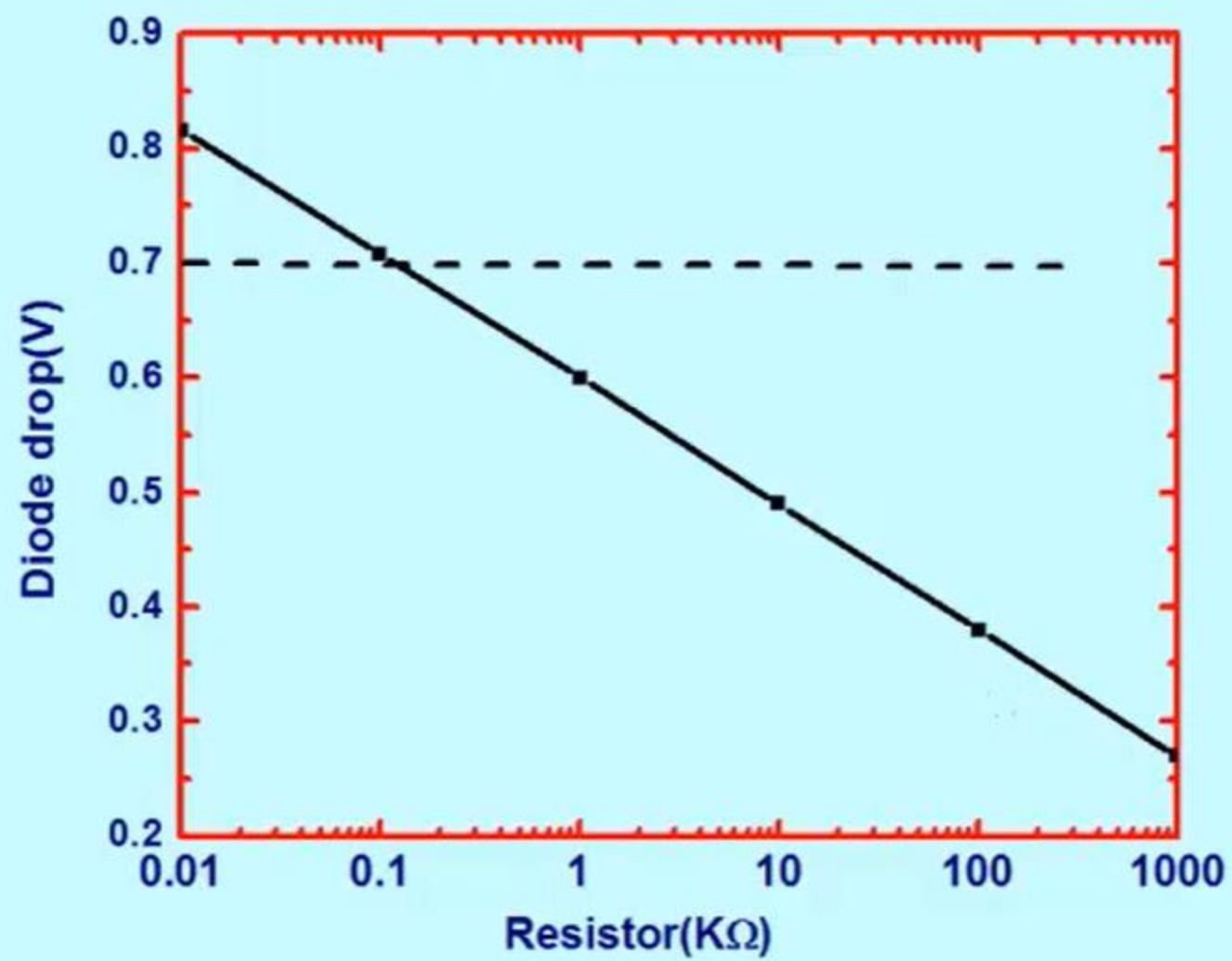
$$I_S = 5.9 \times 10^{-9} \text{ A} ; n = 1.91$$



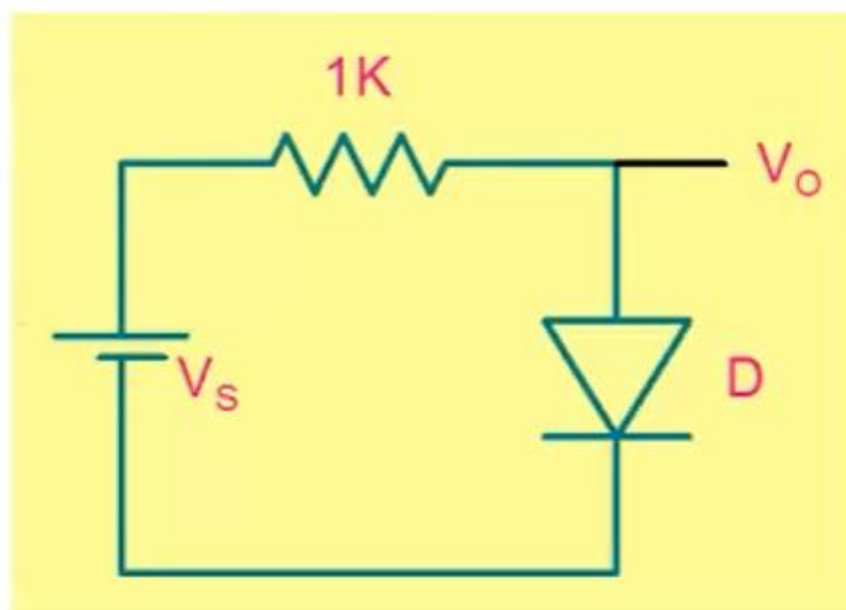Constant diode voltage approximation becomes worse as applied voltage approaches the diode drop !



$$I = \frac{V_S - V_D}{R}$$


$$\Delta I = -\frac{\Delta V_D}{R}$$

$$\frac{\Delta I}{I} = -\left(\frac{\Delta V_D}{V_S - V_D}\right)$$


As V_S approaches $V_D \rightarrow \left(\frac{\Delta I}{I}\right)$ increases

Error was ~9% with 1.7 V but 63% with 0.8V supply

A better Diode Model

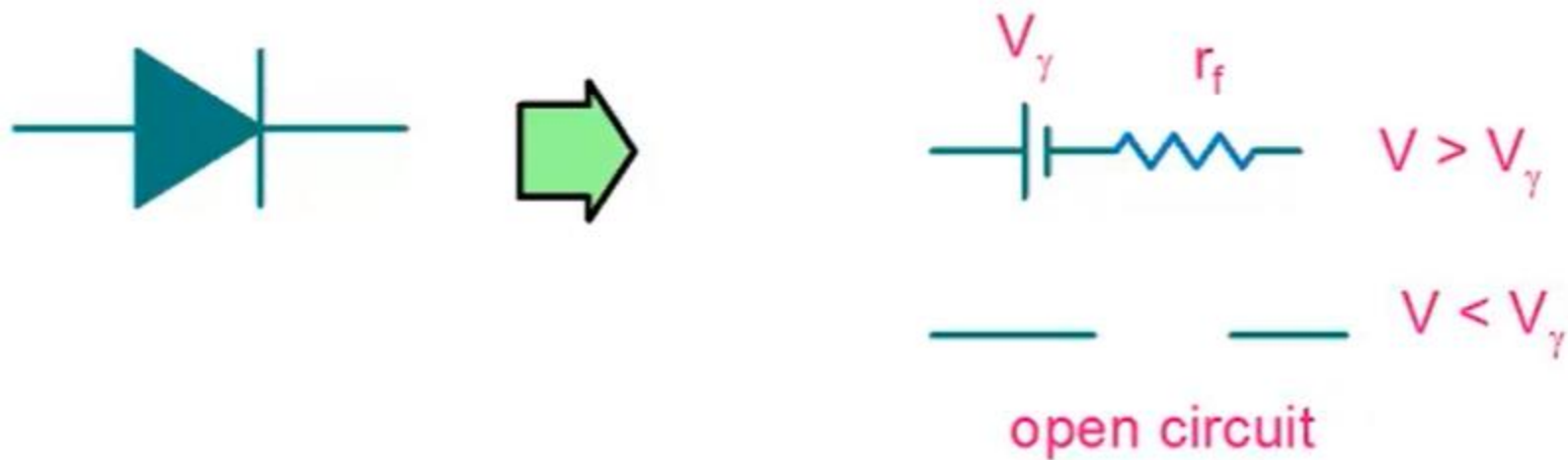

Piece-Wise Linear Model

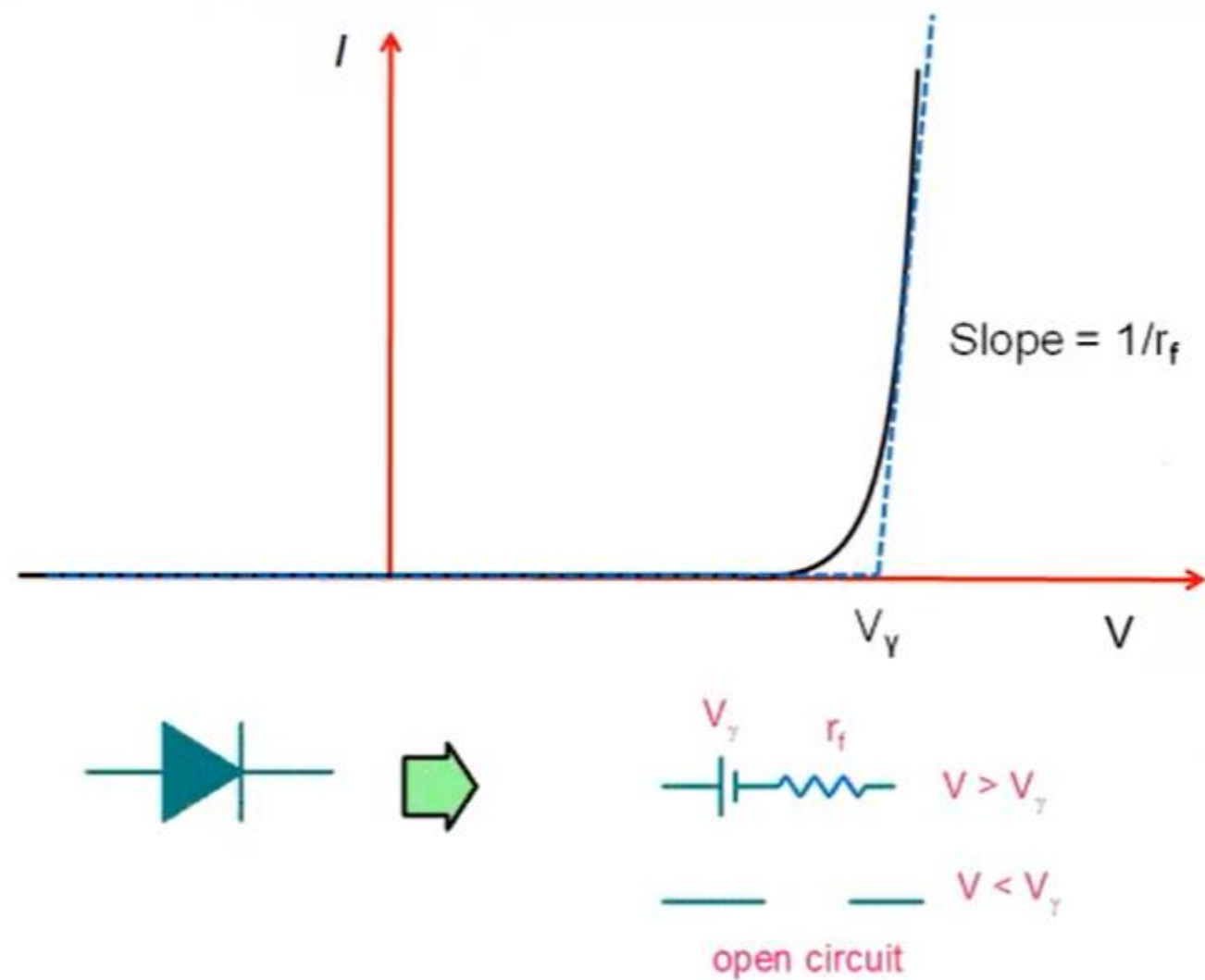



V_Y is called cut-in or turn-on voltage and depends on nature of diode and range of current considered

$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T}\right) - 1 \right\}$$

$$I_S = 2 \times 10^{-15} \text{ A}$$

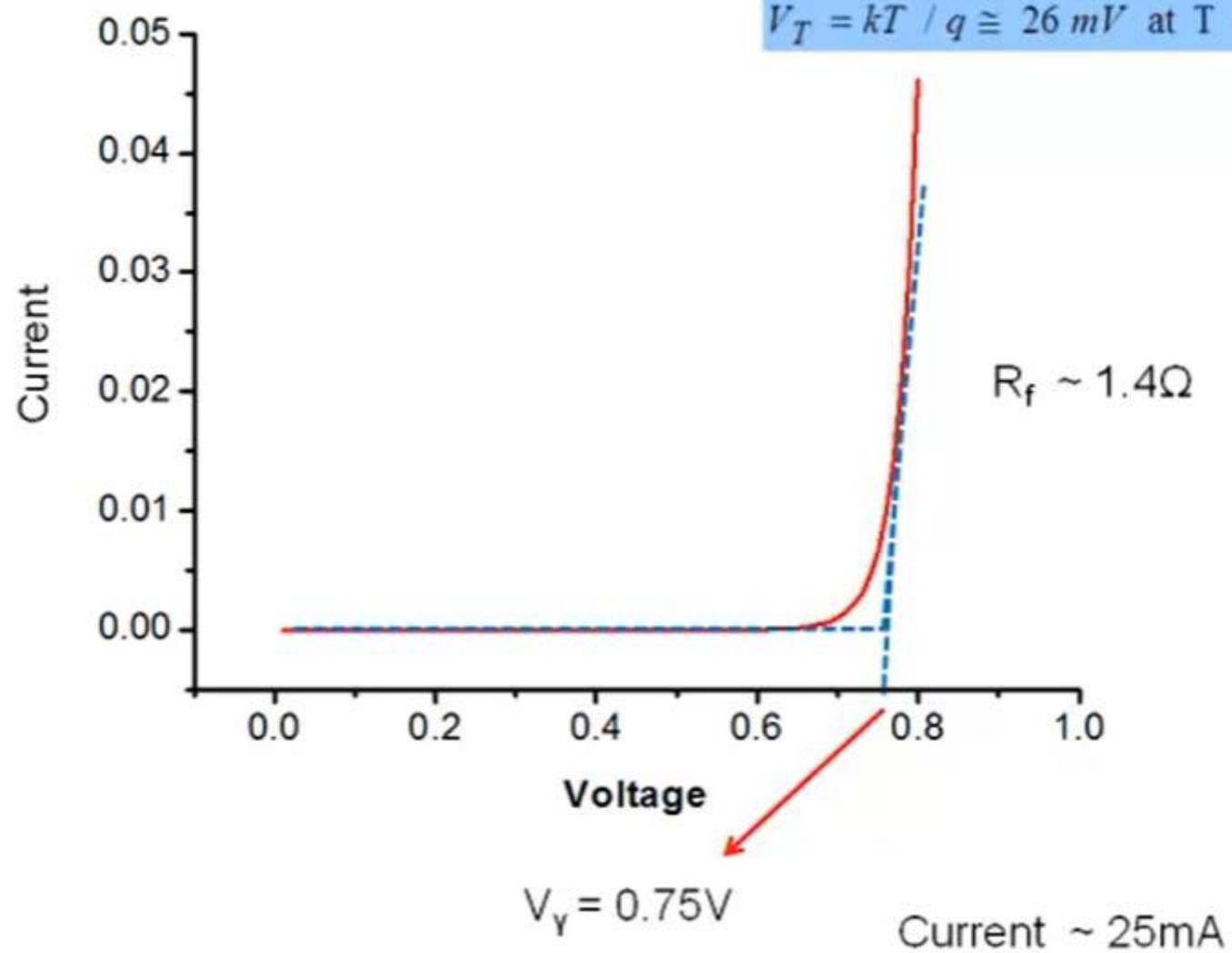
$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$



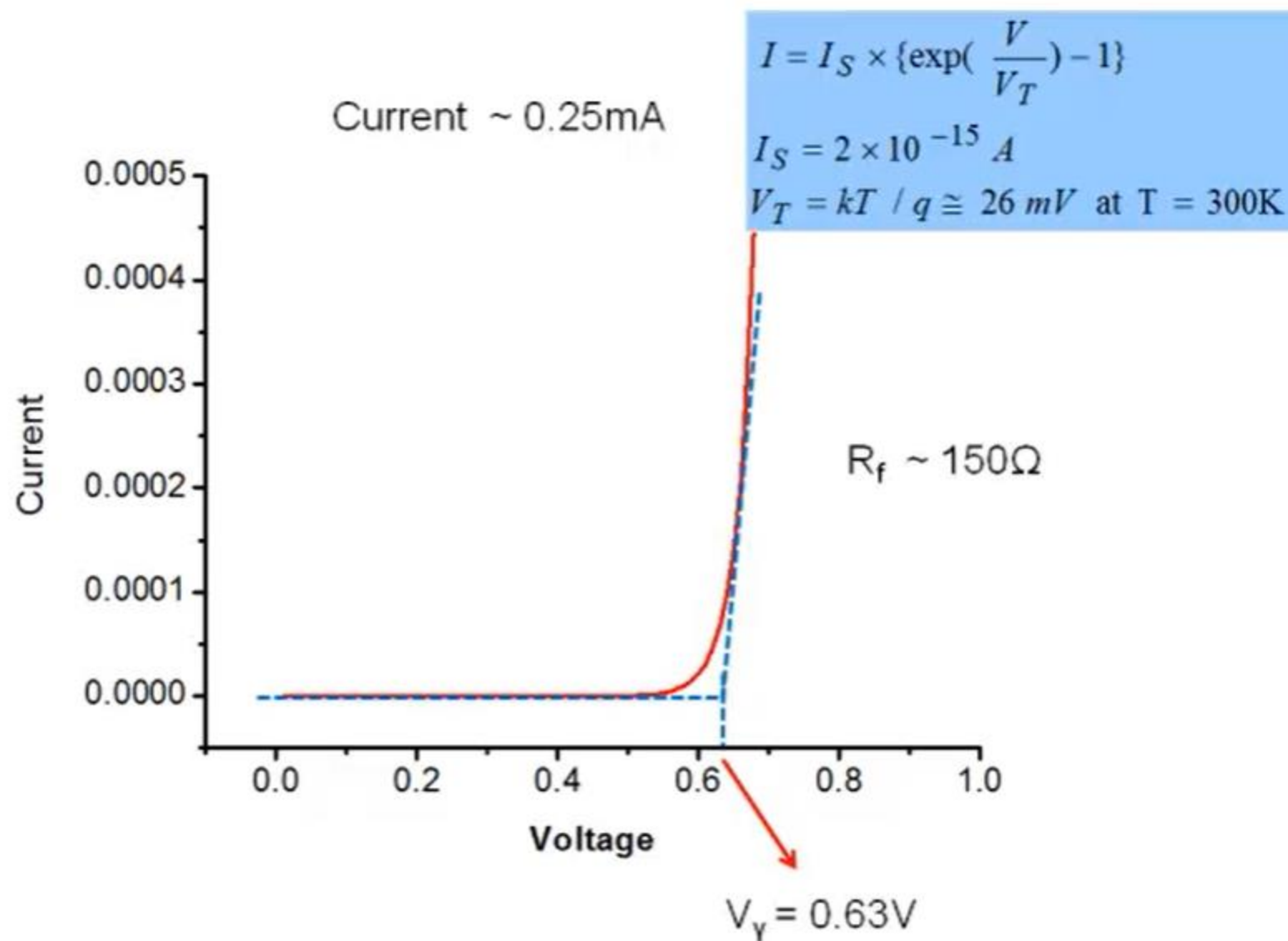


For most of our analysis, we will take $V_Y = 0.7V$ and $r_f \sim 10\Omega$

Even Simpler Diode Models

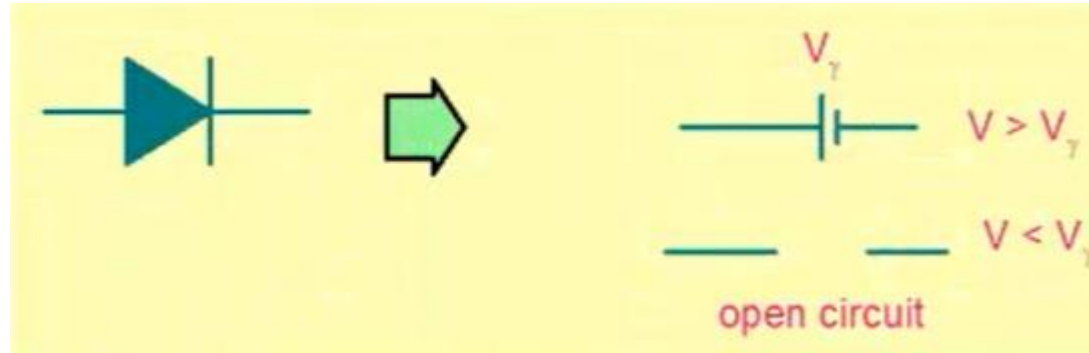


Ideal diode model

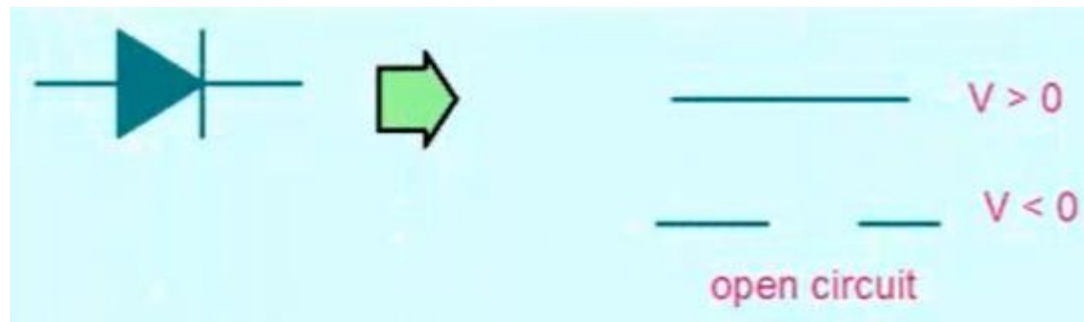


Diode Models

Simplicity


Accuracy

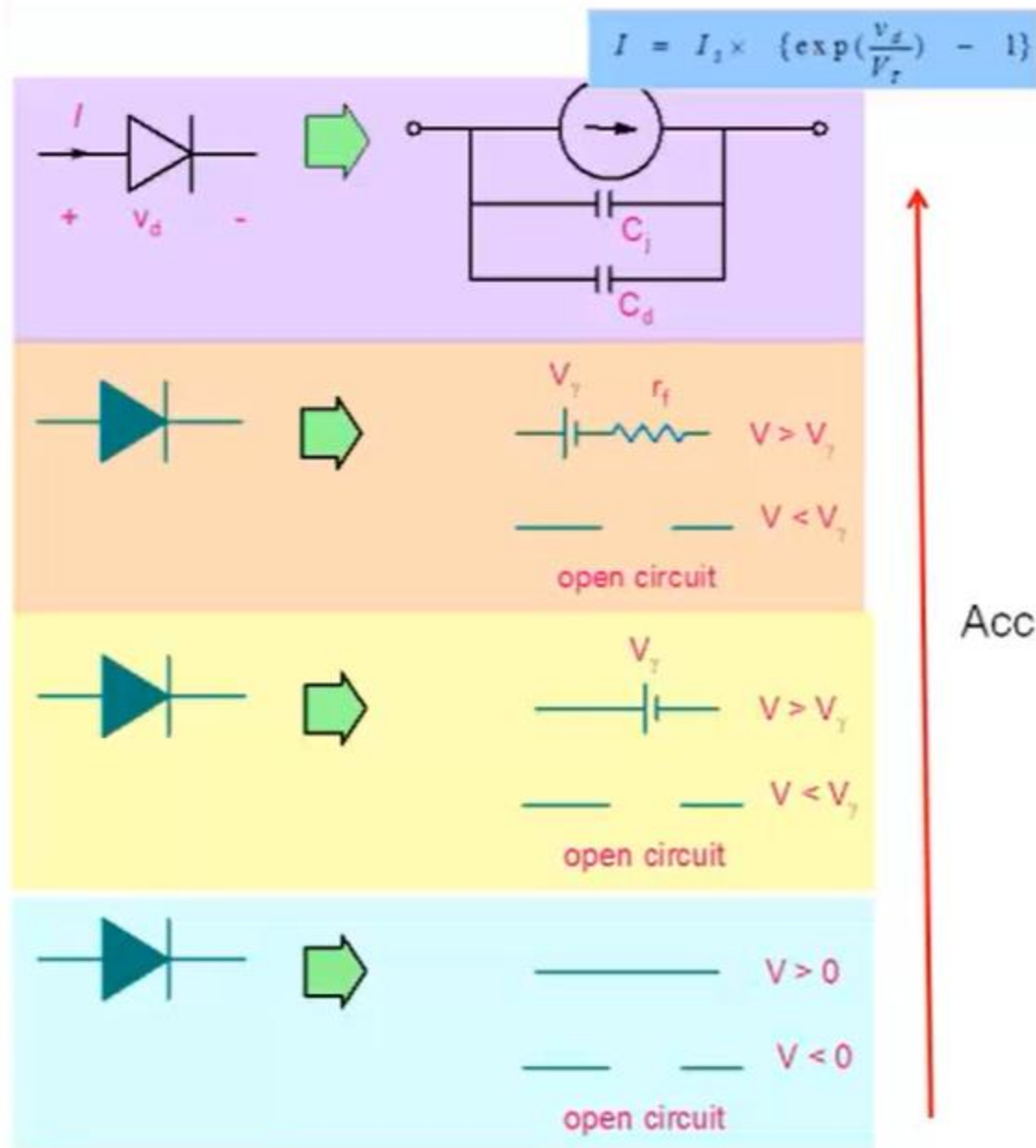

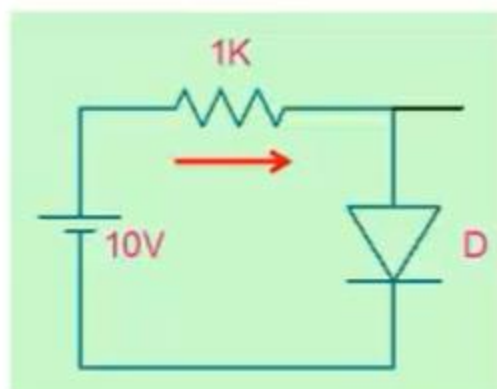Use the simplest model that will yield results with desired accuracy



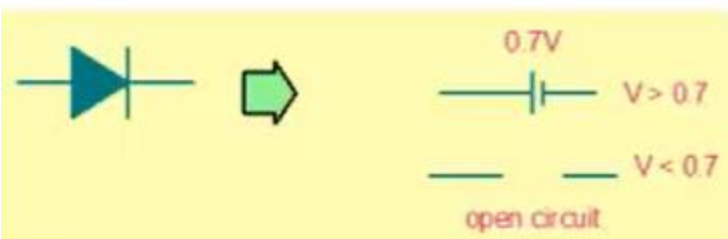
$$I = 10 / 10^3 = 10 \text{ mA} \quad 8.2\%$$




$$I = (10 - 0.7) / 10^3 = 9.3 \text{ mA}$$

0.65%

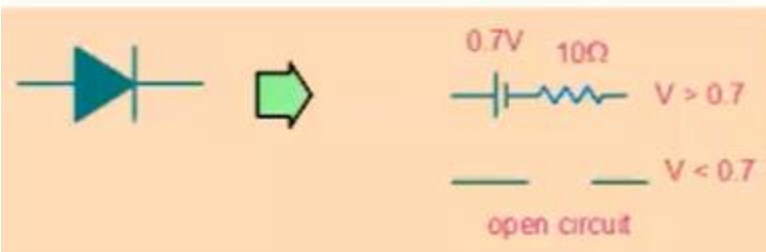


$$I = (10 - 0.7) / (10^3 + 10) = 9.208 \text{ mA}$$

-0.34%

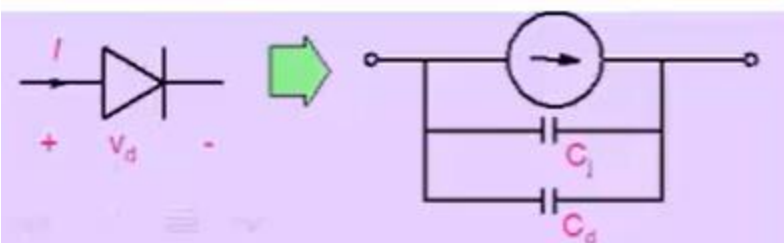


$$I = 9.24 \text{ mA}$$

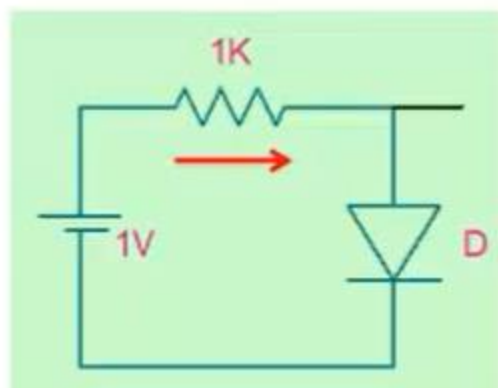Use the simplest model that will yield results with desired accuracy




$$I = 1 / 10^3 = 1 \text{ mA}$$

~200%

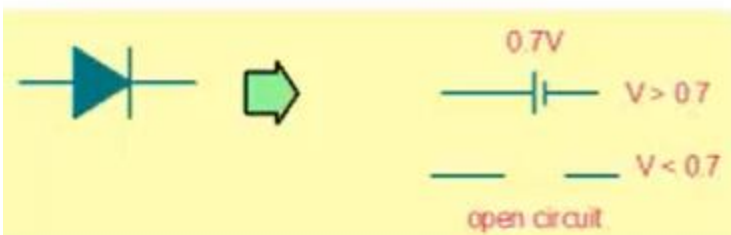


$$I = (1 - 0.7) / 10^3 = 0.3 \text{ mA}$$

-8.8%

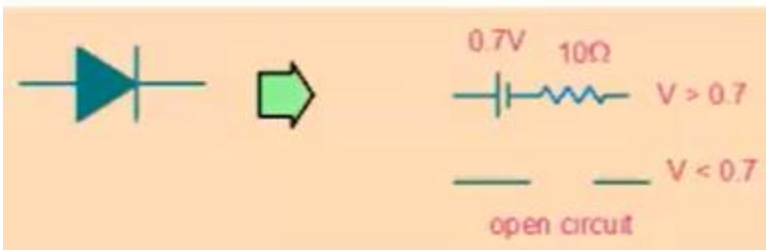

$$I = (1 - 0.7) / (10^3 + 10) = 0.297 \text{ mA}$$

-9.7%

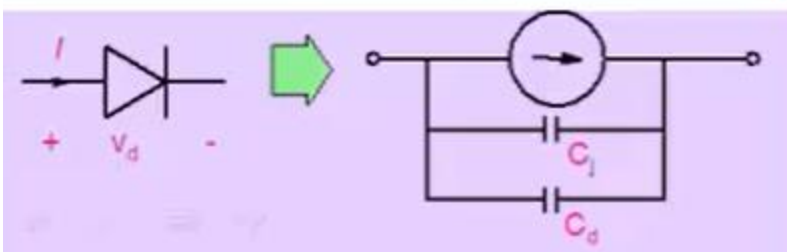

$$I = 0.329 \text{ mA}$$

Small Signal Model

Diode: Small Signal Model (dc or low frequency)

Forward Bias

$$I_d = I_s e^{\frac{V_d}{nV_T}}$$

$$I_D + i_d = I_s e^{\frac{V_D + v_d}{nV_T}}$$

$$i_d = I_D \left(e^{\frac{v_d}{nV_T}} - 1 \right)$$


$$i_d = I_D \left(\frac{v_d}{nV_T} + \frac{v_d^2}{2(nV_T)^2} + \dots \right)$$

Small signal approx : $\frac{v_d}{nV_T} \ll 1$

$$i_d = I_D \left(\frac{v_d}{nV_T} + \frac{v_d^2}{2(nV_T)^2} + \dots \right)$$

$$i_d \cong \left(\frac{I_D}{nV_T} \right) v_d$$
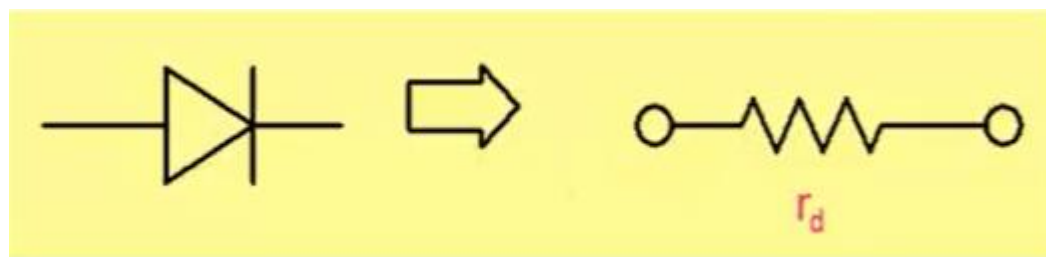
$$i_d = \frac{v_d}{r_d} ; r_d = \frac{nV_T}{I_D}$$



Temperature dependence of diode characteristics

$$I_D = I_S \times \left\{ \exp\left(\frac{V_d}{V_T}\right) - 1 \right\}$$

$$V_T = \frac{kT}{q}$$

$$I_S \propto n_i^2 \propto e^{-\frac{E_g}{kT}}$$

Reverse saturation current increases with temperature. For forward bias, even though V_T increases, current still increases because of greater influence of I_S


For a diode in forward bias at a fixed current I_O : $v_D = V_T \times \ln(I_O/I_S + 1)$

For Silicon diodes, v_D decreases at the rate of $\sim -2\text{mV}/^\circ\text{C}$

If the diode voltage is 0.7 at 27°C , then at 100°C it would be only :

$$0.7 - 2 \times 10^{-3} \times (100 - 27) = 0.554\text{V}$$

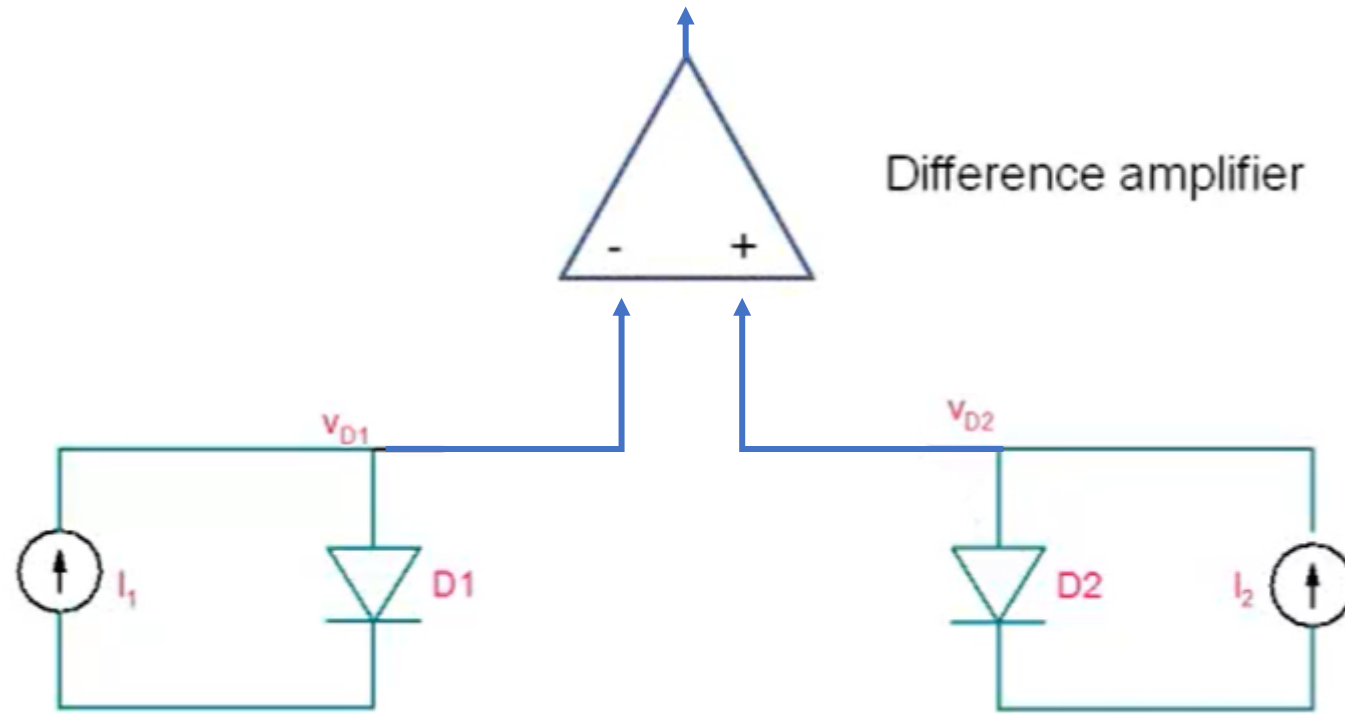Measurement of temperature using a pn junction diode



$$v_{D1} = V_T \times \ln(I_1/I_S + 1)$$

$$v_{D2} = V_T \times \ln(I_2/I_S + 1)$$

$$v_o = C \times (v_{D2} - v_{D1})$$

$$v_o = \left(C \times \frac{k}{q} \times \ln\left(\frac{I_2}{I_1}\right) \right) \times T$$